

# CMSC 313 Lecture 16

- **Postulates & Theorems of Boolean Algebra**
- **Semiconductors**
- **CMOS Logic Gates**

# Last Time

- Overview of second half of this course
- Logic gates & symbols
- Equivalence of Boolean functions, truth tables, Boolean formulas and combinational circuits
- Universality of NAND gates

# Postulates of Boolean Algebra

---

- **Commutative:**  $AB = BA, \quad A + B = B + A$
- **Associative:**  $(AB)C = A(BC), \quad (A + B) + C = A + (B + C)$
- **Distributive:**  $A(B + C) = AB + AC, \quad A + BC = (A + B)(A + C)$
- **Identity:** there exists 0 and 1 such that for all  $A$ ,

$$1A = A \quad \text{and} \quad 0 + A = A.$$

- **Complement:** for all  $A$ , there exists  $\bar{A}$  such that

$$A\bar{A} = 0 \quad \text{and} \quad A + \bar{A} = 1$$

where 0 and 1 are the identity elements.

## Some Theorems of Boolean Algebra

---

- **Zero and One:**  $0A = 0$ ,  $1 + A = 1$
- **Idempotence:**  $AA = A$ ,  $A + A = A$
- **Involution:**  $\overline{\overline{A}} = A$
- **DeMorgan's:**  $\overline{AB} = \overline{A} + \overline{B}$ ,  $\overline{A + B} = \overline{A}\overline{B}$
- **Absorption:**  $A(A + B) = A$ ,  $A + AB = A$
- **Consensus:**  $AB + \overline{A}C + BC = AB + \overline{A}C$ ,  
 $(A + B)(\overline{A} + C)(B + C) = (A + B)(\overline{A} + C)$

# Theorems are derived from the postulates

---

- Idempotence:

$A = A1$	identity, commutative
$= A(A + \overline{A})$	complement
$= AA + A\overline{A}$	distributive
$= AA + 0$	complement
$= AA$	commutative, identity
$A = 0 + A$	identity
$= (A\overline{A}) + A$	complement
$= (A + A)(\overline{A} + A)$	distributive
$= (A + A)1$	commutative, complement
$= A + A$	commutative, identity

## Theorems are derived from the postulates

---

- Zero and One:

$0A$	$= (A\bar{A})A$	complement
	$= A(A\bar{A})$	commutative
	$= (AA)\bar{A}$	associative
	$= A\bar{A}$	idempotent
	$= 0$	complement
$1 + A$	$= (A + \bar{A}) + A$	complement
	$= A + (A + \bar{A})$	commutative
	$= (A + A) + \bar{A}$	associative
	$= A + \bar{A}$	idempotent
	$= 1$	complement

## Theorems are derived from the postulates

---

- Absorption:

$$\begin{aligned} A + AB &= A1 + AB && \text{identity, commutative} \\ &= A(1 + B) && \text{distributive} \\ &= A1 && \text{one} \\ &= A && \text{commutative, identity} \end{aligned}$$

$$\begin{aligned} A(A + B) &= AA + AB && \text{distributive} \\ &= A + AB && \text{idempotent} \\ &= A && \text{absorption} \end{aligned}$$

## Proof by truth table?

---

- Absorption:  $A + AB = A$

$A$	$B$	$AB$	$A + AB$
0	0	0	0
0	1	0	0
1	0	0	1
1	1	1	1

- Proof by truth table only applies to 0-1 Boolean Algebra.
- Proof by derivation from postulates holds for any Boolean Algebra.



## A Boolean Algebra with 8 elements

---

- Elements are the subsets of  $\{a, b, c\}$ :

$$\emptyset, \{a\}, \{b\}, \{c\}, \{a, b\}, \{a, c\}, \{b, c\}, \{a, b, c\}$$

- Operations:  $AB \rightarrow A \cap B$ ,  $A + B \rightarrow A \cup B$ .
- Union and intersection are commutative and associative.
- Union distributes over intersection:  $A \cup (B \cap C) = (A \cup B) \cap (A \cup C)$ .
- Intersection distributes over union:  $A \cap (B \cup C) = (A \cap B) \cup (A \cap C)$ .
- Identity:  $0 = \emptyset$ ,  $1 = \{a, b, c\}$ ,  $\{a, b, c\} \cap A = A$  and  $\emptyset \cup A = A$ .
- Complement:  $\bar{A} = \{a, b, c\} - A$ ,  $A \cap \bar{A} = \emptyset$  and  $A \cup \bar{A} = \{a, b, c\}$ .
- All postulates hold. Therefore, all derived theorems also hold.

## Simplifying MAJ3

---

- Simplify MAJ3 using the postulates and theorems of Boolean Algebra

$$\text{MAJ3}(A, B, C)$$

$$= \overline{A}BC + A\overline{B}C + AB\overline{C} + ABC \quad \text{SOP form}$$

$$= \overline{A}BC + A\overline{B}C + AB\overline{C} + ABC + ABC + ABC \quad \text{idempotent}$$

$$= \overline{A}BC + ABC + A\overline{B}C + ABC + AB\overline{C} + ABC \quad \text{commutative}$$

$$= (\overline{A} + A)BC + (\overline{B} + B)AC + (\overline{C} + C)AB \quad \text{distributive}$$


$$= 1BC + 1AC + 1AB \quad \text{complement}$$

$$= BC + AC + AB \quad \text{identity}$$

- Resulting circuit uses fewer gates.

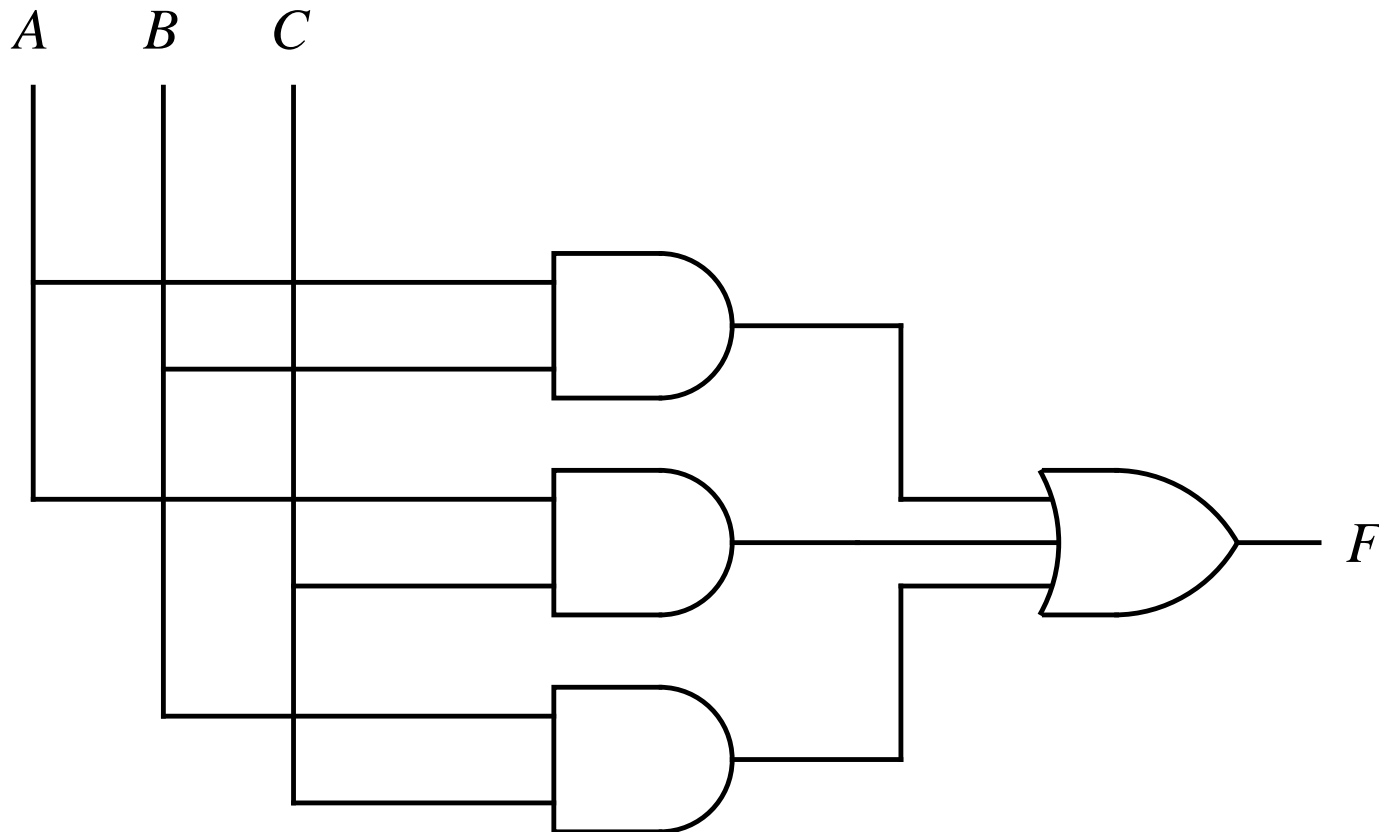
# The Algebraic Method

- This majority circuit is functionally equivalent to the previous majority circuit, but this one is in its minimal two-level form:


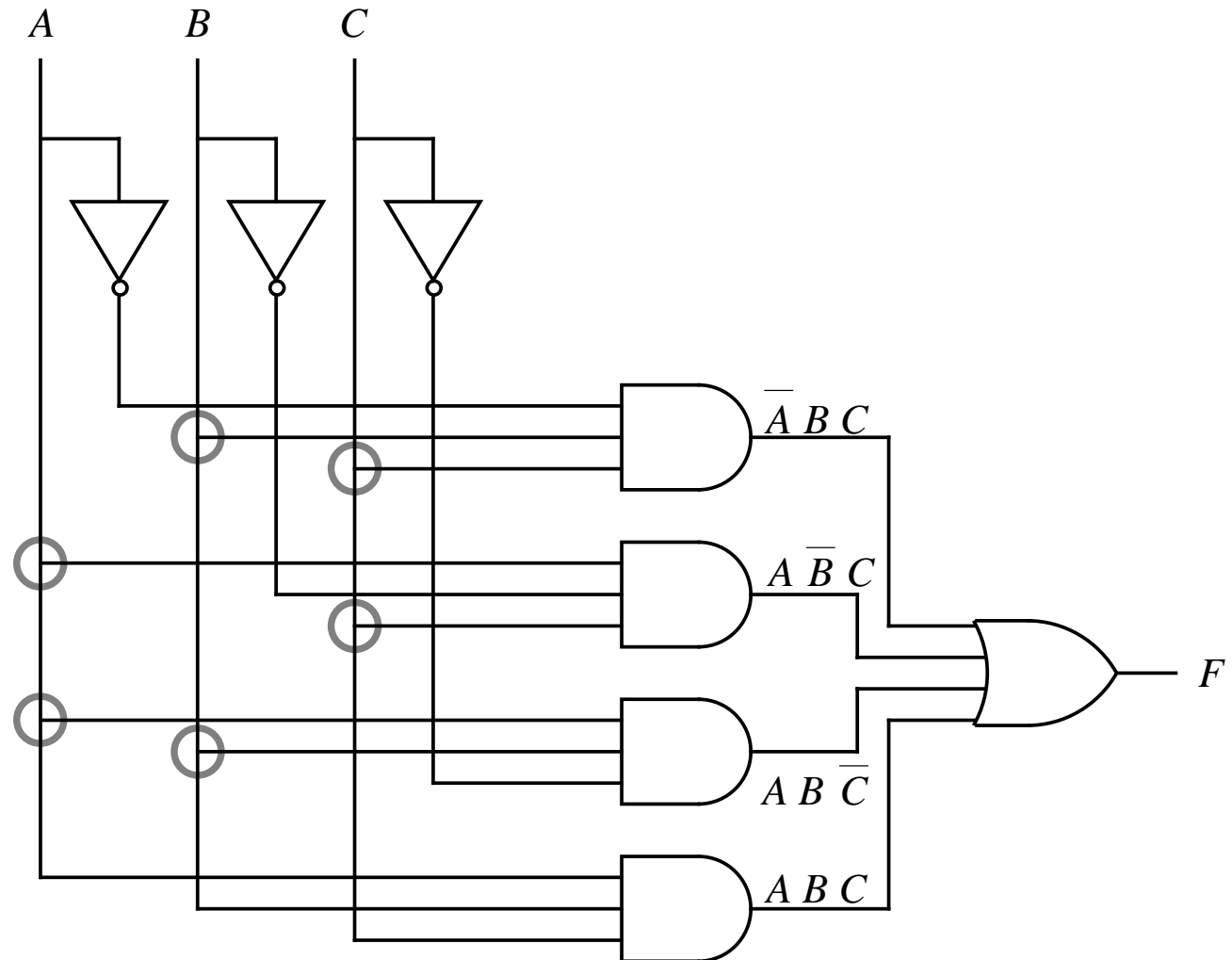
# AND-OR Implementation of Majority


- Gate count is 8, gate input count is 19.



**How do we make gates???**
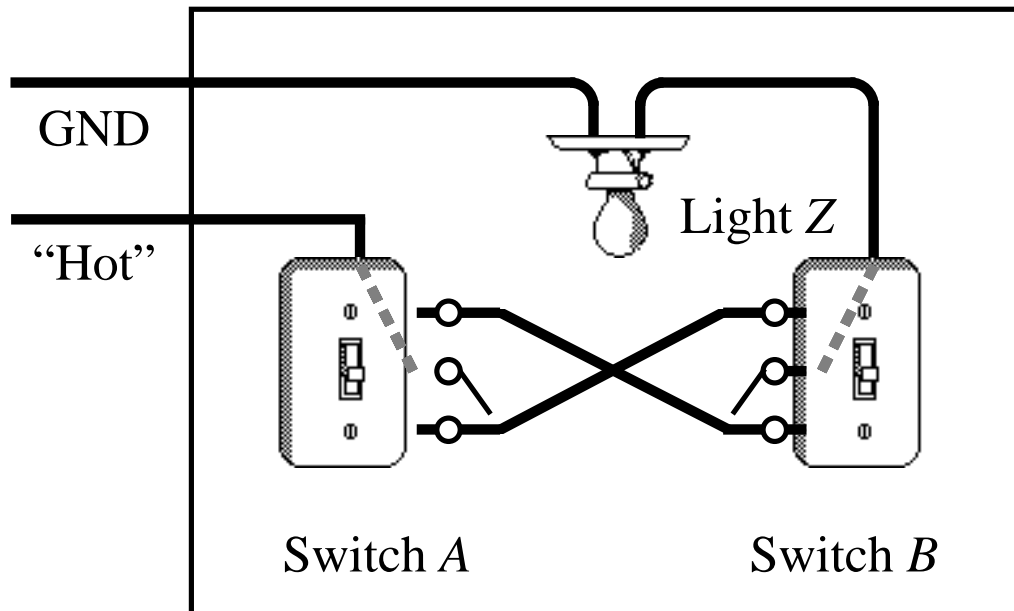
# A Truth Table



- Developed in 1854 by George Boole.
- Further developed by Claude Shannon (Bell Labs).
- Outputs are computed for all possible input combinations (how many input combinations are there?)
- Consider a room with two light switches. How must they work?



Inputs		Output
A	B	Z
0	0	0
0	1	1
1	0	1
1	1	0

# Electrically Operated Switch

- **Example: a relay**

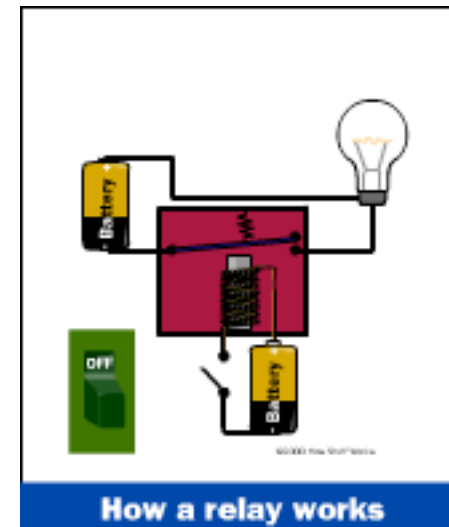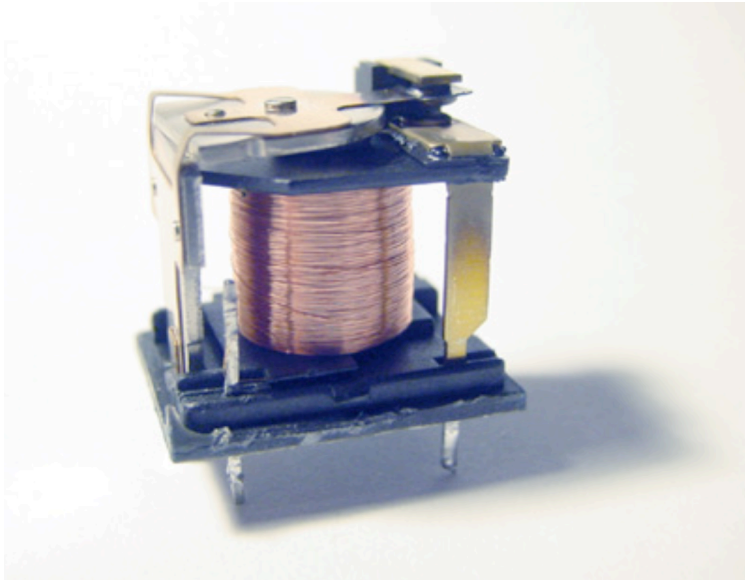

source: <http://www.howstuffworks.com/relay.htm>


# Semiconductors



- **Electrical properties of silicon**
- **Doping: adding impurities to silicon**
- **Diodes and the P-N junction**
- **Field-effect transistors**


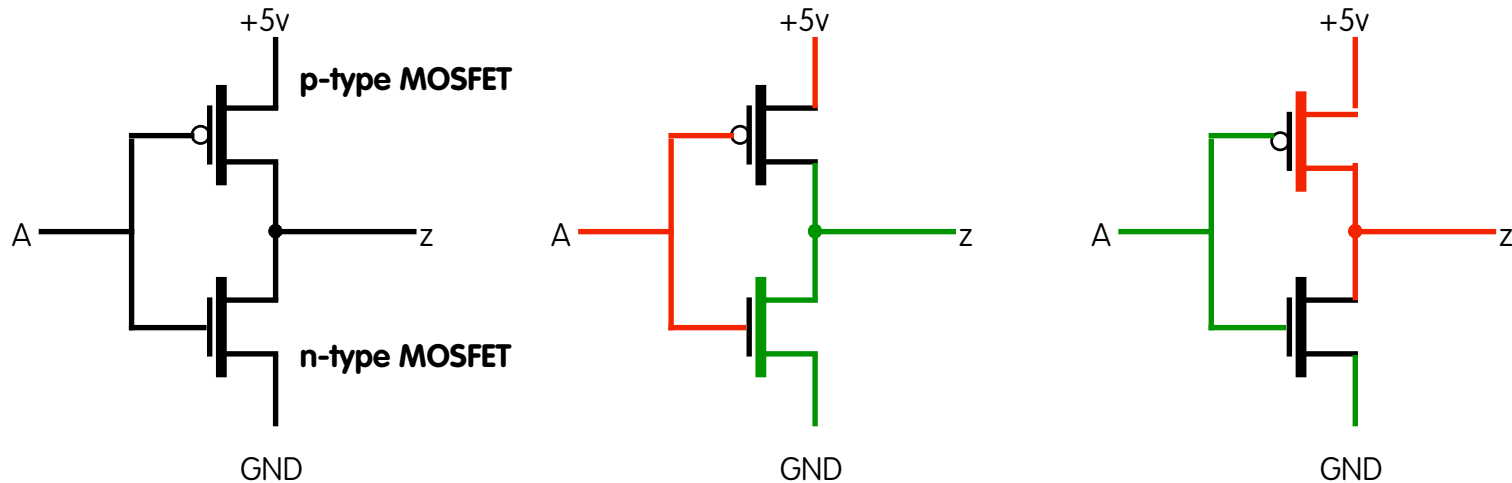
# An Inverter using MOSFET




- **CMOS** = complementary metal oxide semiconductor
- **P-type transistor conducts when gate is low**
- **N-type transistor conducts when gate is high**





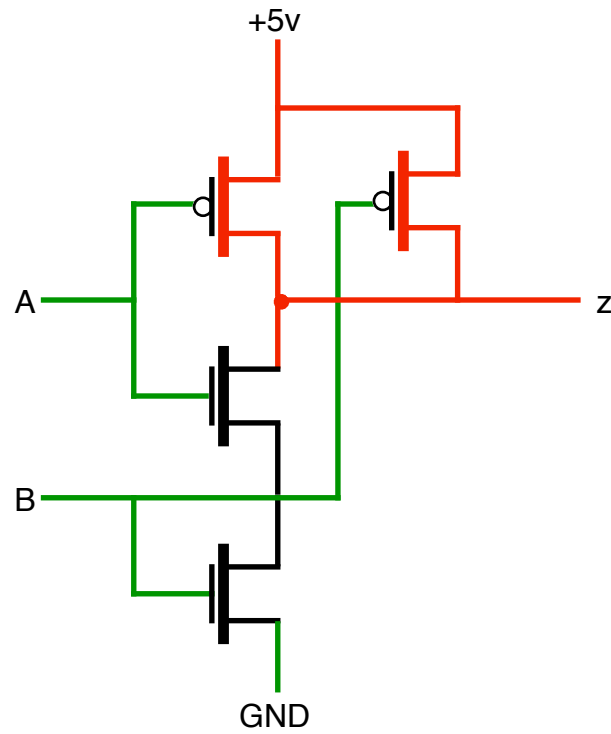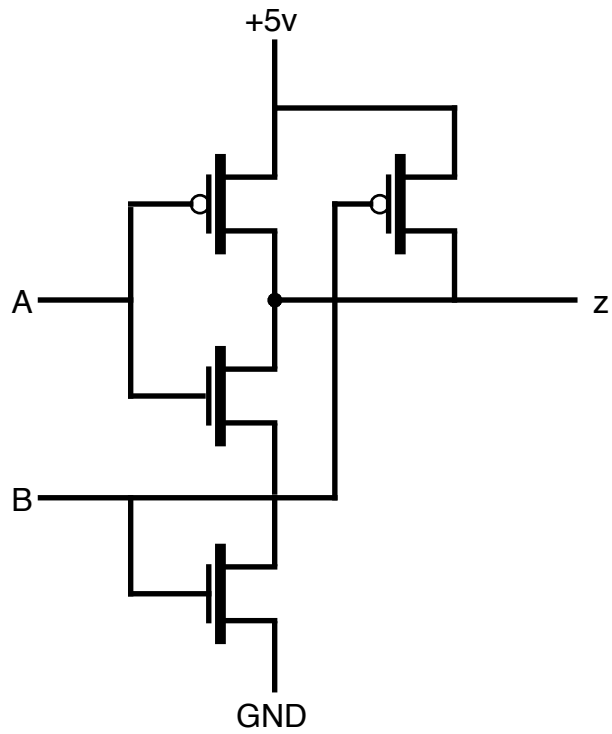

## NAND GATE




A	B	z
0	0	1
0	1	1
1	0	1
1	1	0

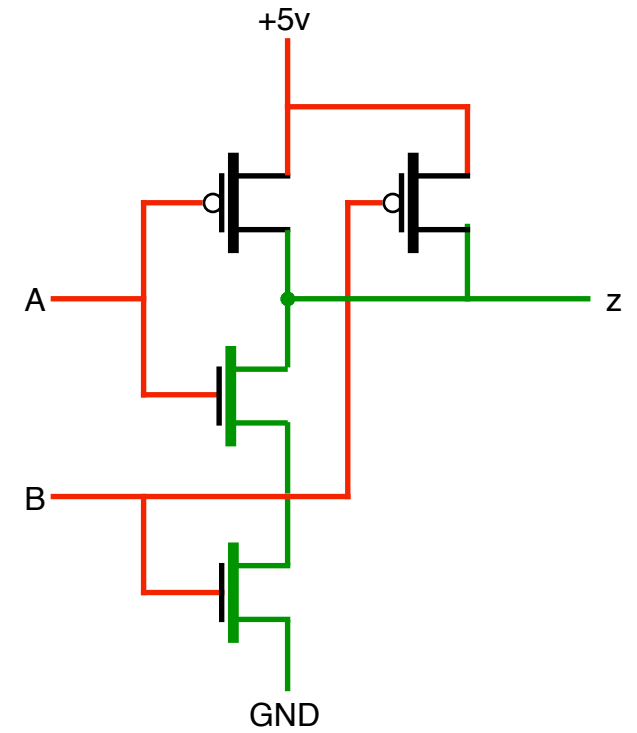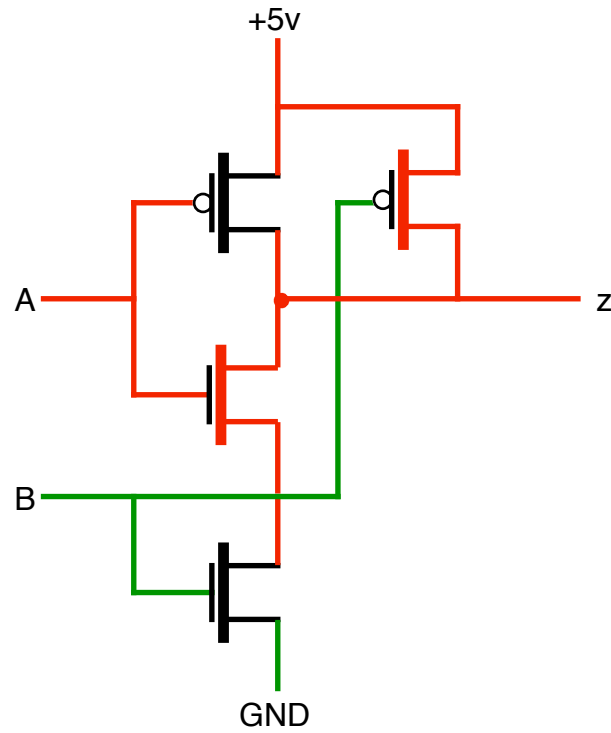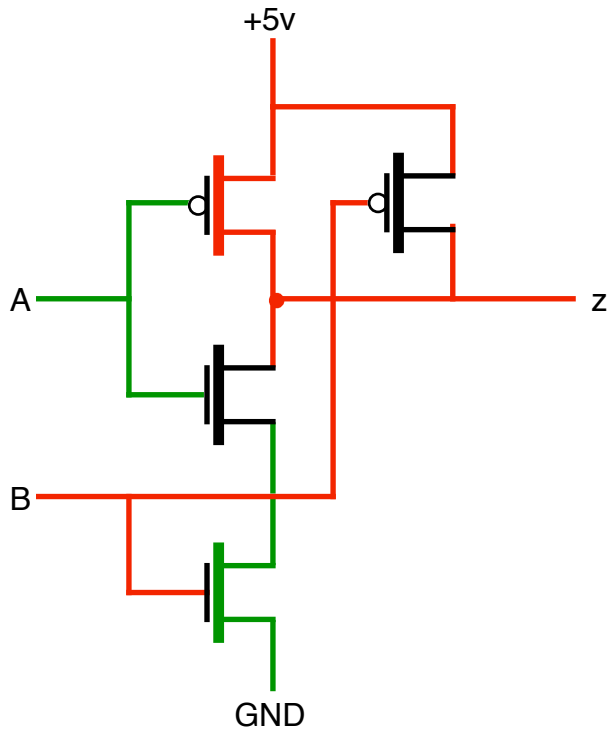

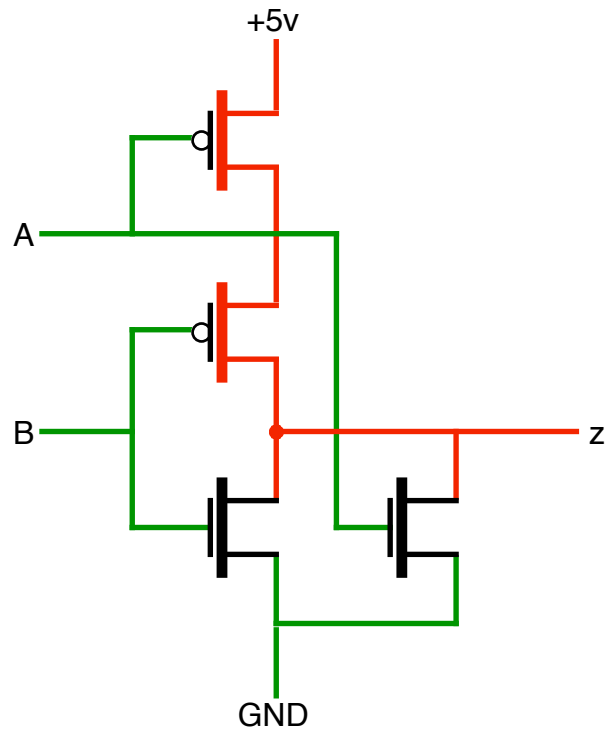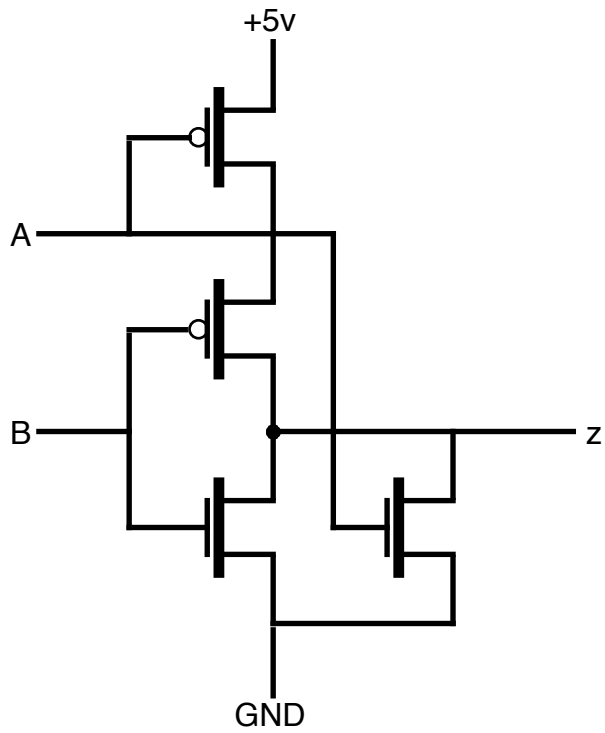

## NOR GATE

A	B	z
0	0	1
0	1	0
1	0	0
1	1	0

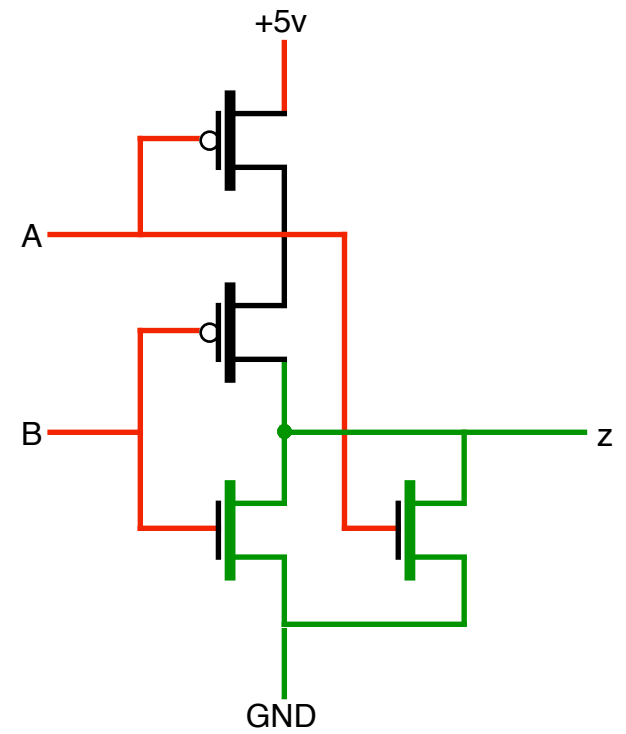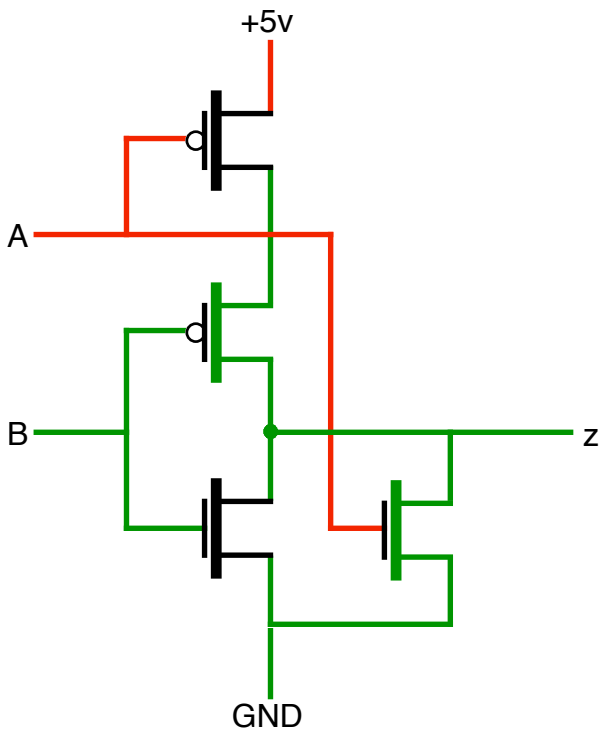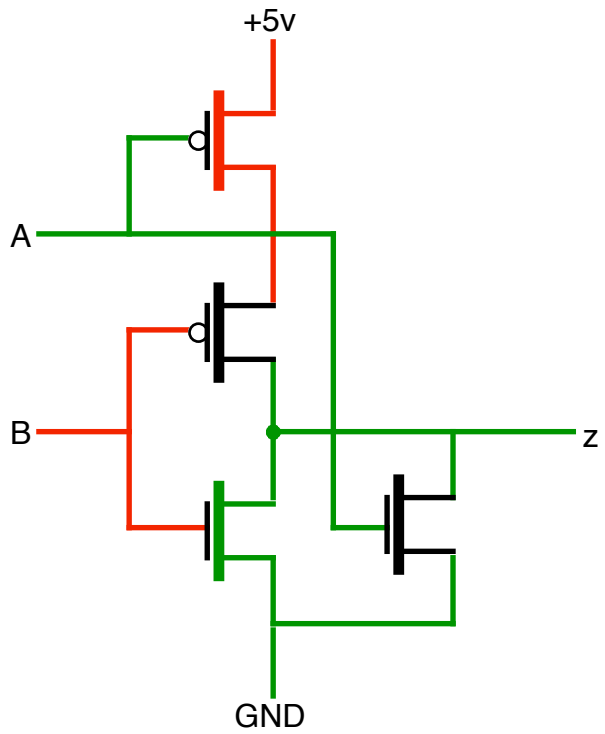


# CMOS Logic vs Bipolar Logic


- **MOSFET transistors are easier to miniaturize**
- **CMOS logic has lower current drain**
- **CMOS logic is easier to manufacture**

**Due: October 30, 2003**

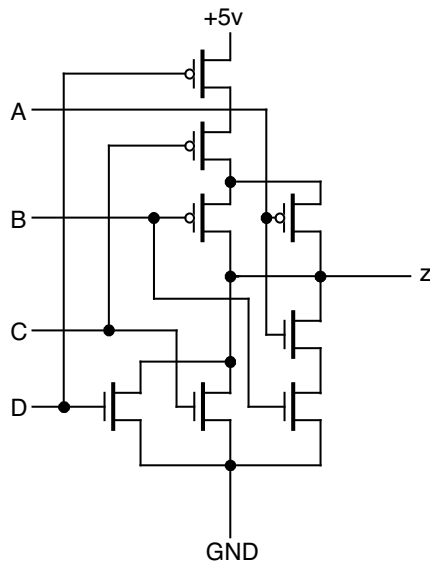1. (20 points) Draw schematics for the following functions using AND, OR and NOT gates. (Do not simplify the formulas.)
  - (a)  $X(Y + Z)$
  - (b)  $\overline{X + YZ}$
  - (c)  $\overline{X(Y + Z)}$
  - (d)  $W(X + YZ)$
  
2. (10 points) Question A.3, page 493, Murdocca & Heuring
  
3. (10 points) Prove the Consensus Theorem  $AB + \overline{A}C + BC = AB + \overline{A}C$  using the postulates and theorems of Boolean algebra (except the Consensus Theorem itself) in Table A-1 (p. 451). *Hint: use absorption creatively.*
  
4. (40 points) For each CMOS circuit below,
  - (a) Provide a truth table for the circuit's function.
  - (b) For diagram (a), write down the Sum-of-Products (SOP) Boolean formula for the truth table. For diagram (b), write down the Product-of-Sums (POS) Boolean formula.
  - (c) Simplify the SOP or POS formula using the postulates and theorems of Boolean Algebra (p. 451). *Show all work.*
  - (d) Draw the logic diagram of the simplified formula using AND, OR, NAND, NOR and NOT gates.



(a)

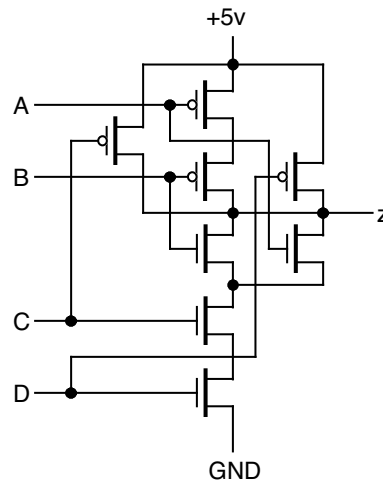

(b)

# Next time

- **Circuits for Addition**