

CMSC 313 Lecture 17

- **Focus Groups**

- ◇ Need good sample of all types of CS students
- ◇ Mon 11/17 & Thu 11/20, 12:30p-2:00p & 6:00p-7:30p

- **Announcement: in-class lab Thu 10/30**

- **Homework 3 Questions**

- **Circuits for Addition**

- **Midterm Exam returned**


Due: October 30, 2003

1. (20 points) Draw schematics for the following functions using AND, OR and NOT gates. (Do not simplify the formulas.)
 - (a) $X(Y + Z)$
 - (b) $\overline{X + YZ}$
 - (c) $\overline{X(Y + Z)}$
 - (d) $W(X + YZ)$


2. (10 points) Question A.3, page 493, Murdocca & Heuring

3. (10 points) Prove the Consensus Theorem $AB + \overline{A}C + BC = AB + \overline{A}C$ using the postulates and theorems of Boolean algebra (except the Consensus Theorem itself) in Table A-1 (p. 451). *Hint: use absorption creatively.*

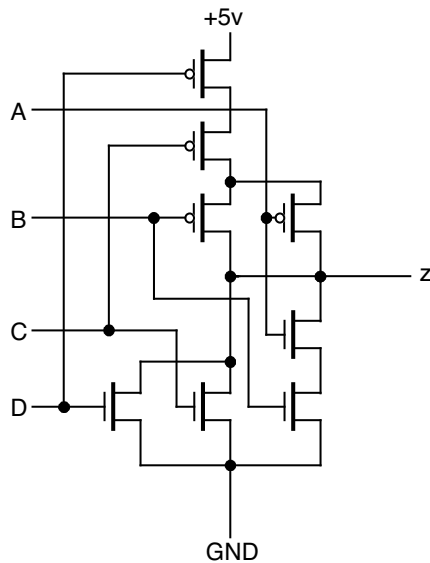4. (40 points) For each CMOS circuit below,
 - (a) Provide a truth table for the circuit's function.
 - (b) For diagram (a), write down the Sum-of-Products (SOP) Boolean formula for the truth table. For diagram (b), write down the Product-of-Sums (POS) Boolean formula.
 - (c) Simplify the SOP or POS formula using the postulates and theorems of Boolean Algebra (p. 451). *Show all work.*
 - (d) Draw the logic diagram of the simplified formula using AND, OR, NAND, NOR and NOT gates.



(a)

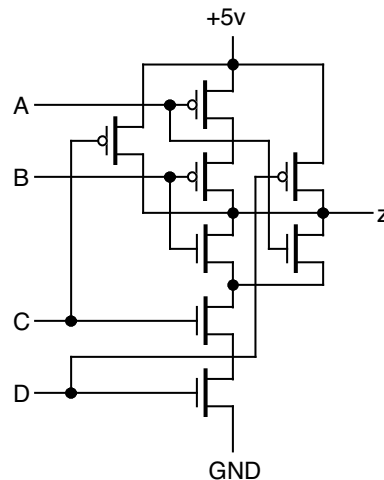

(b)

Last Time

- **Postulates & Theorems of Boolean Algebra**
- **Periodic Table & Semiconductors**
- **P-N junction**
- **Field-Effect Transistors**
- **CMOS Logic Gates**

Half Adder

- **Inputs:** A and B
- **Outputs:** S = lower bit of $A + B$, c_{out} = carry bit

A	B	S	c_{out}
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

- Using Sum-of-Products: $S = \overline{A}B + A\overline{B}$, $c_{\text{out}} = AB$.
- Alternatively, we could use XOR: $S = A \oplus B$.

Full Adder


- **Inputs:** A , B and c_{in}
- **Outputs:** S = lower bit of $A + B$, c_{out} = carry bit

A	B	c_{in}	S	c_{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

- $S = \overline{A}\overline{B}C + \overline{A}B\overline{C} + A\overline{B}\overline{C} + ABC = A \oplus B \oplus C.$
- $c_{out} = \text{MAJ3} = AB + BC + AC.$


Ripple Carry Adder

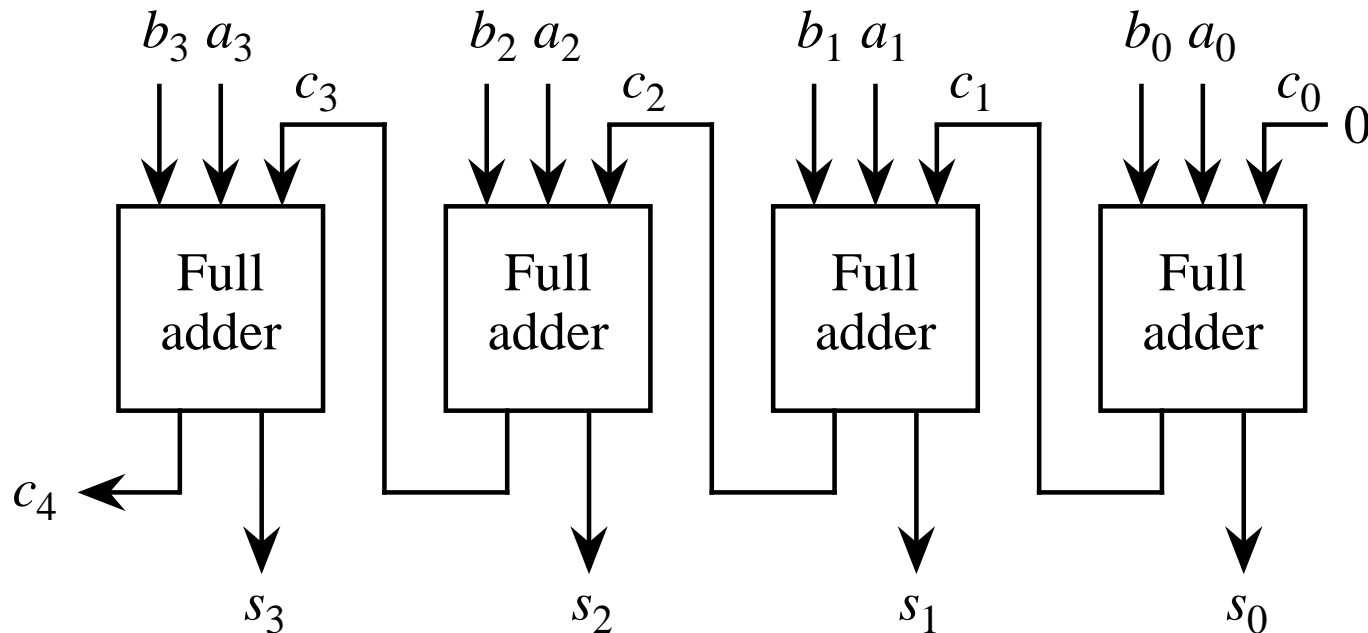- Two binary numbers A and B are added from right to left, creating a sum and a carry at the outputs of each full adder for each bit position.



Constructing Larger Adders

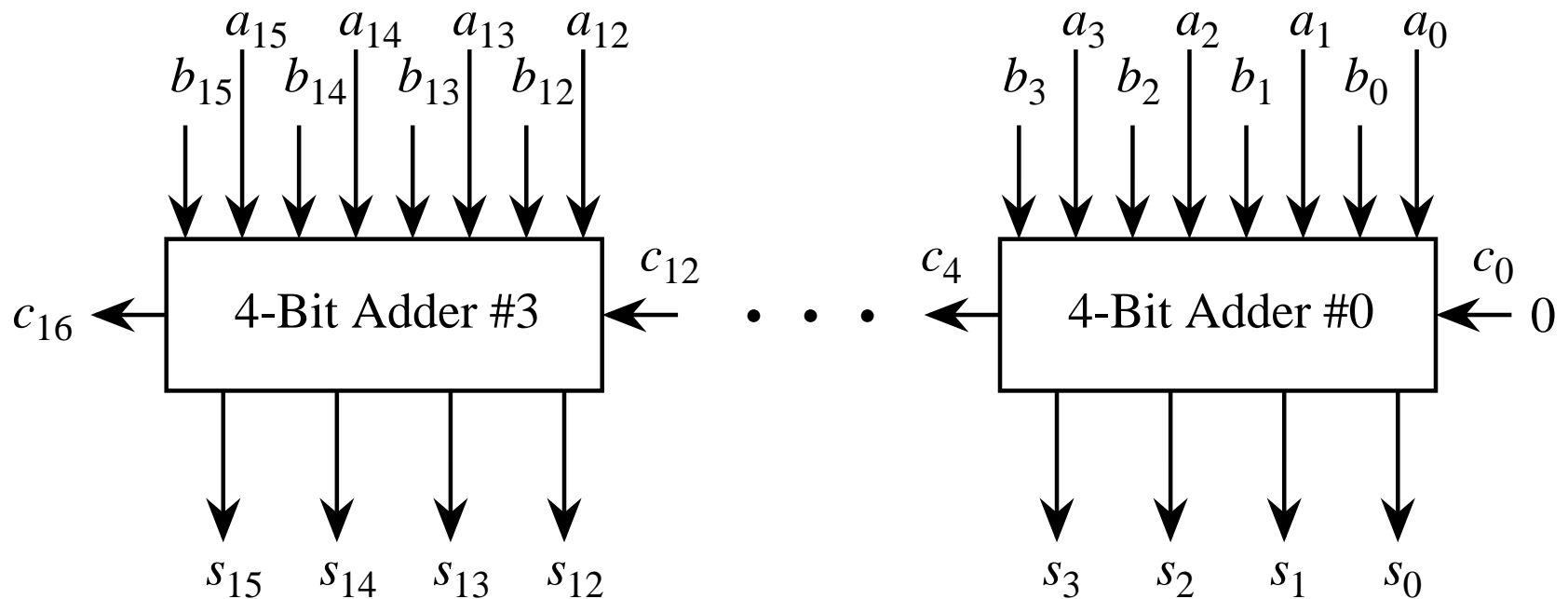
- A 16-bit adder can be made up of a cascade of four 4-bit ripple-carry adders.



Full Subtractor


- Truth table and schematic symbol for a ripple-borrow subtractor:

a_i	b_i	bor_i	$diff_i$	bor_{i+1}
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

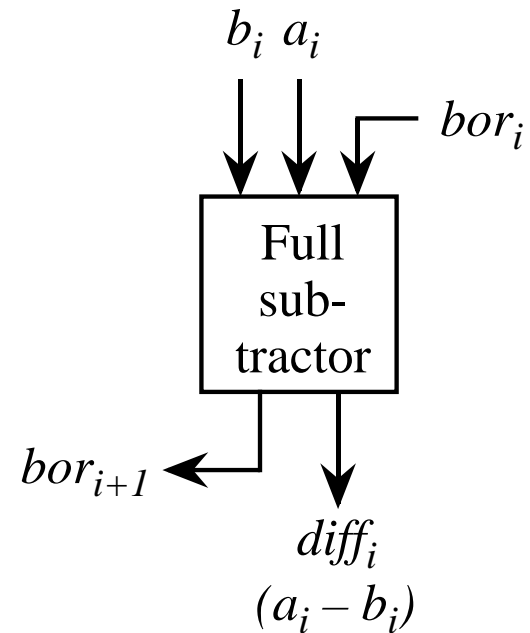


Ripple-Borrow Subtractor

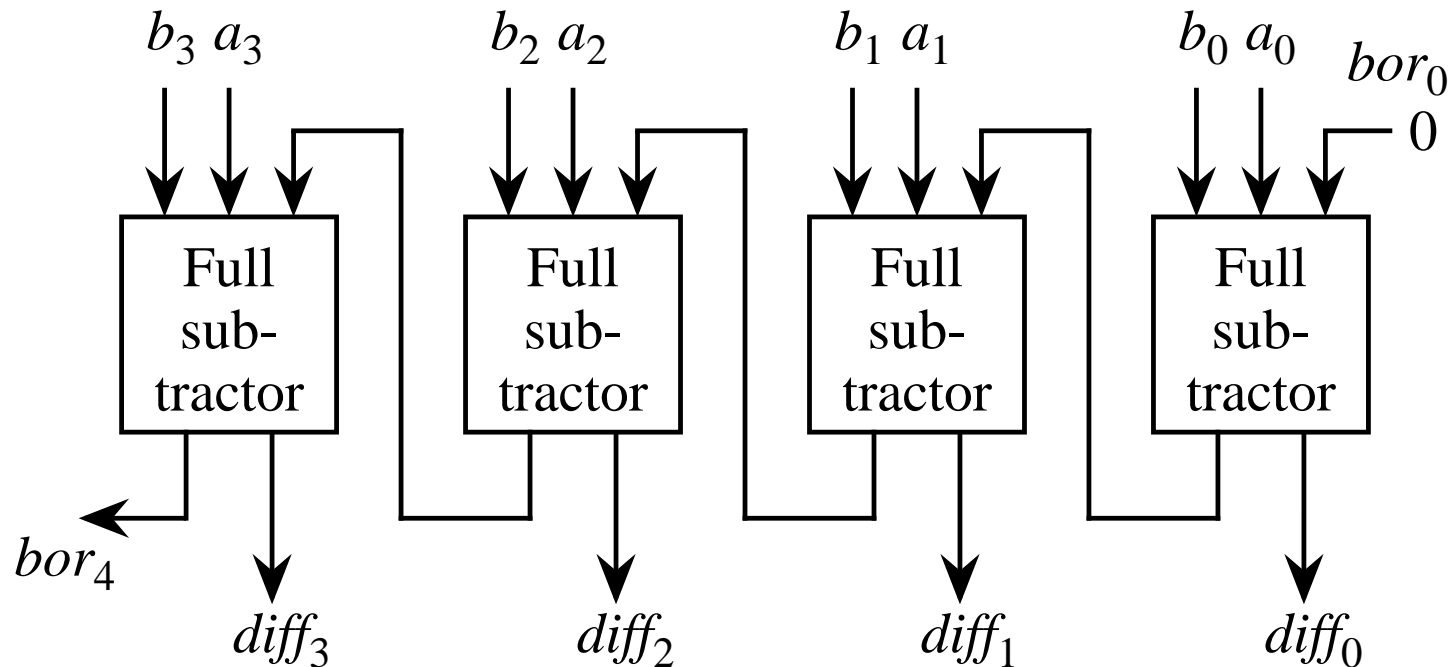- A ripple-borrow subtractor can be composed of a cascade of full subtractors.
- Two binary numbers A and B are subtracted from right to left, creating a difference and a borrow at the outputs of each full subtractor for each bit position.



Combined Adder/Subtractor

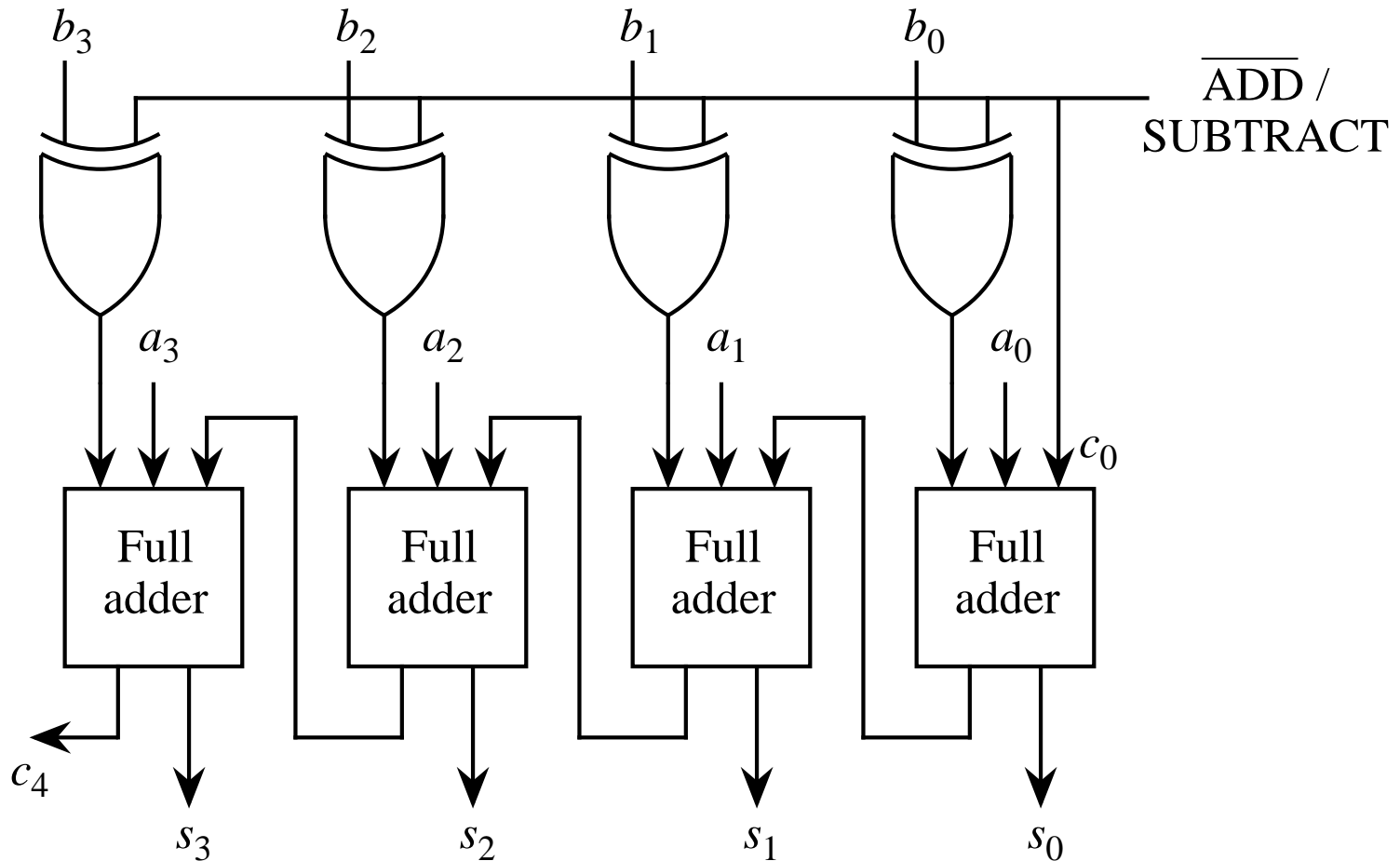- A single ripple-carry adder can perform both addition and subtraction, by forming the two's complement negative for B when subtracting. (Note that $+1$ is added at c_0 for two's complement.)



Carry-Lookahead Addition

$$s_i = \bar{a}_i \bar{b}_i c_i + \bar{a}_i b_i \bar{c}_i + a_i \bar{b}_i \bar{c}_i + a_i b_i c_i$$

$$c_{i+1} = b_i c_i + a_i c_i + a_i b_i$$

$$c_{i+1} = a_i b_i + (a_i + b_i) c_i$$

$$c_{i+1} = G_i + P_i c_i$$

- Carries are represented in terms of G_i (generate) and P_i (propagate) expressions.

$$G_i = a_i b_i \quad \text{and} \quad P_i = a_i + b_i$$

$$c_0 = 0$$


$$c_1 = G_0$$

$$c_2 = G_1 + P_1 G_0$$

$$c_3 = G_2 + P_2 G_1 + P_2 P_1 G_0$$

$$c_4 = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0$$

Carry Lookahead Adder

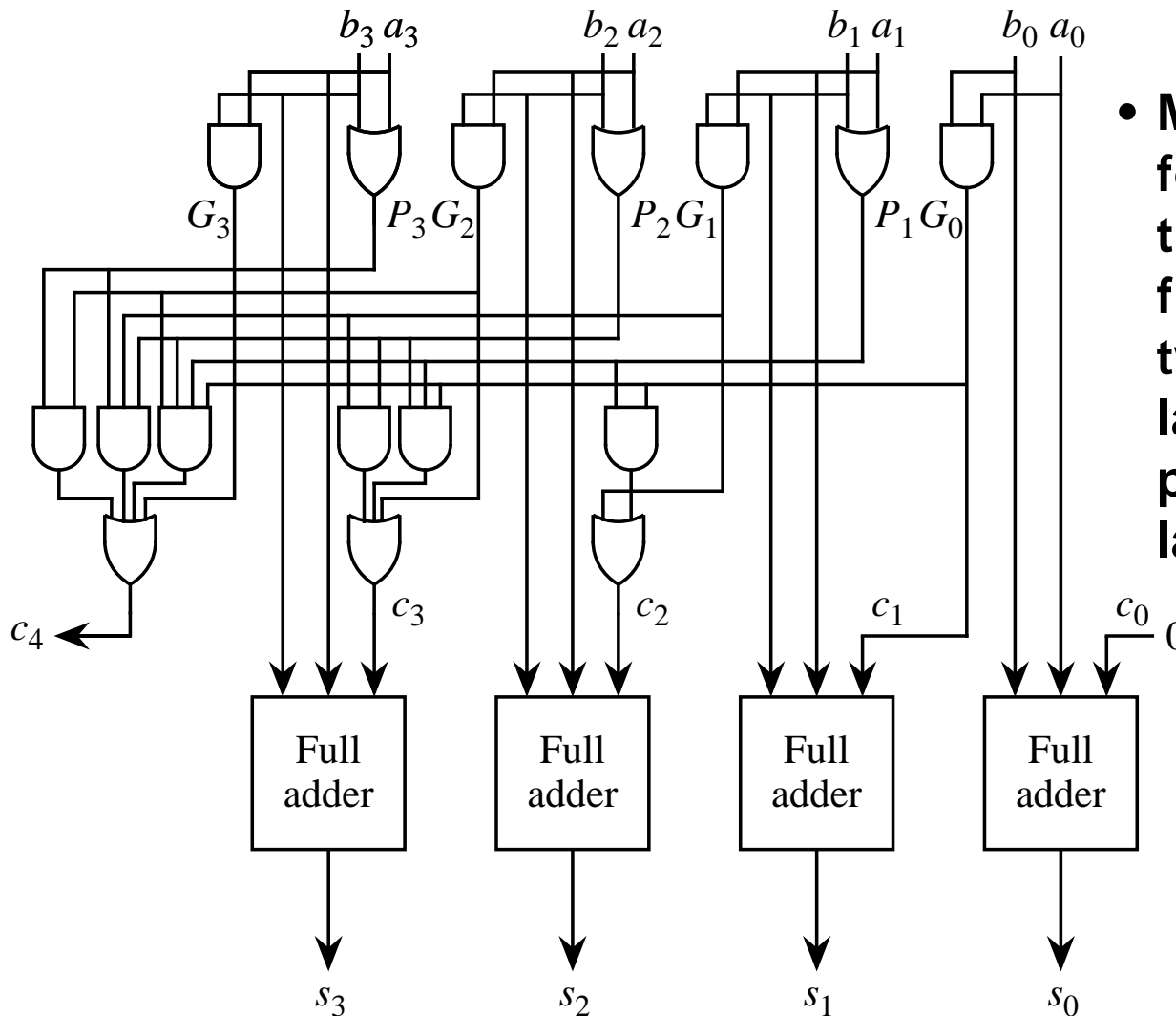

- Maximum gate delay for the carry generation is only 3. The full adders introduce two more gate delays. Worst case path is 5 gate delays.

Next Time

- **In-class Labs**
- **Homework 3 due**
- **Homework 4 assigned**