

CMSC 313 Lecture 20

- Homework 4 Questions
- Karnaugh Map examples

Last Time

- **Combinational logic components**
- **Introduction to Karnaugh Maps**

Karnaugh Maps

- ◇ **Implicant:** rectangle with 1, 2, 4, 8, 16 ... 1's
- ◇ **Prime Implicant:** an implicant that cannot be extended into a larger implicant
- ◇ **Essential Prime Implicant:** the only prime implicant that covers some 1
- ◇ **K-map Algorithm (not from M&H):**
 1. Find ALL the prime implicants. Be sure to check every 1 and to use don't cares.
 2. Include all essential prime implicants.
 3. Try all possibilities to find the minimum cover for the remaining 1's.

Notes on K-maps


- Also works for POS
- Takes 2^n time for formulas with n variables
- Only optimizes two-level logic
 - ◇ Reduces number of terms, then number of literals in each term
- Assumes inverters are free
- Does not consider minimizations across functions
- Circuit minimization is generally a hard problem
- Quine-McCluskey can be used with more variables
- CAD tools are available if you are serious

Circuit Minimization is Hard

- **Unix systems store passwords in encrypted form.**
 - ◇ User types in x , system computes $f(x)$ and looks for $f(x)$ in a file.
- **Suppose we use 64-bit passwords and I want to find the password x , such that $f(x) = y$. Let**
$$g_i(x) = 0 \text{ if } f(x) = y \text{ and the } i\text{th bit of } x \text{ is } 0$$
$$1 \text{ otherwise.}$$
- **If the i th bit of x is 1, then $g_i(x)$ outputs 1 for every x and has a very, very simple circuit.**
- **If you can simplify every circuit quickly, then you can crack passwords quickly.**

3-Level Majority Circuit

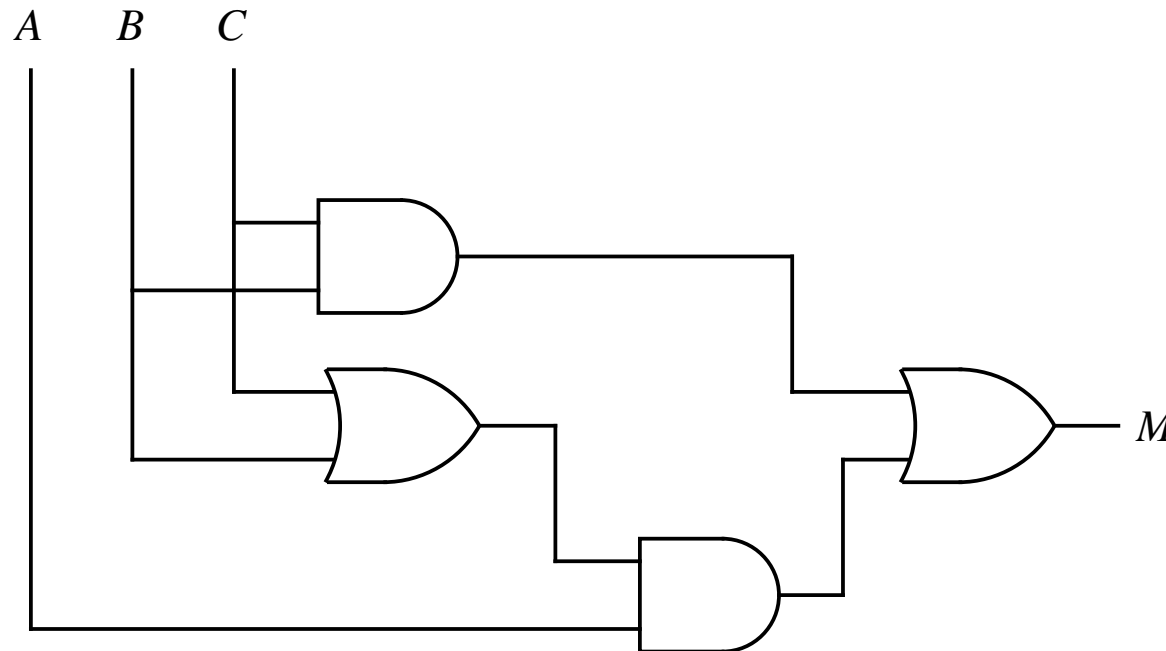- K-Map Reduction results in a reduced two-level circuit (that is, AND followed by OR. Inverters are not included in the two-level count). Algebraic reduction can result in multi-level circuits with even fewer logic gates and fewer inputs to the logic gates.



Due: Thursday, November 13, 2003







1. (10 points) Question A.12, page 494, Murdocca & Heuring
2. (10 points) Question A.16, page 495, Murdocca & Heuring
3. (10 points) Question A.17, page 495, Murdocca & Heuring
4. (50 points) In the following, the notation $\sum m(x_1, \dots, x_j)$ indicates a Boolean function that is the sum of the minterms x_1, \dots, x_j , where x_i is the i th minterm in canonical ordering — i.e., the i th row of the truth table where the input values are ordered as binary numbers. Similarly,

$$\sum m(x_1, \dots, x_j) + d(y_1, \dots, y_k)$$

indicates a Boolean function that is the sum of the minterms x_1, \dots, x_j and whose values for rows y_1, \dots, y_k of the truth table are *don't cares*.

Minimize the following functions using Karnaugh maps. Then, write down a Boolean formula in sum-of-products or product-of-sums form for each function. Show your work (including the Karnaugh maps).

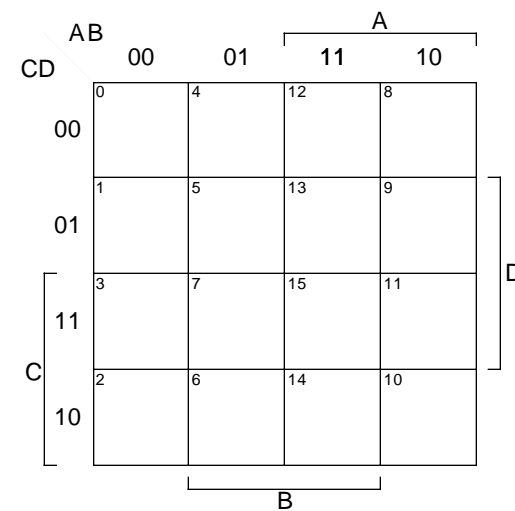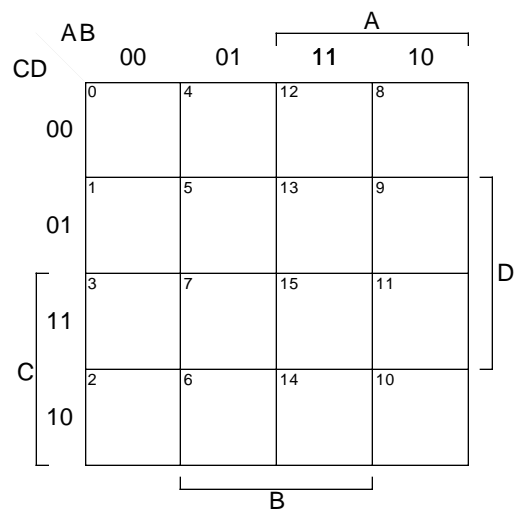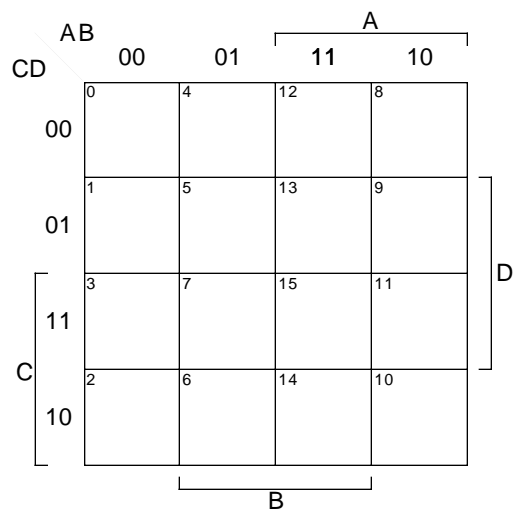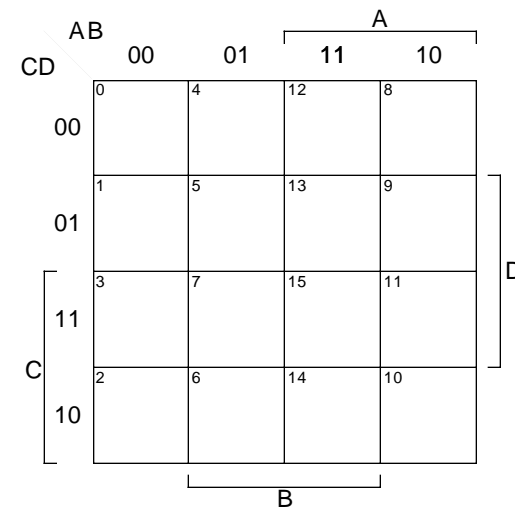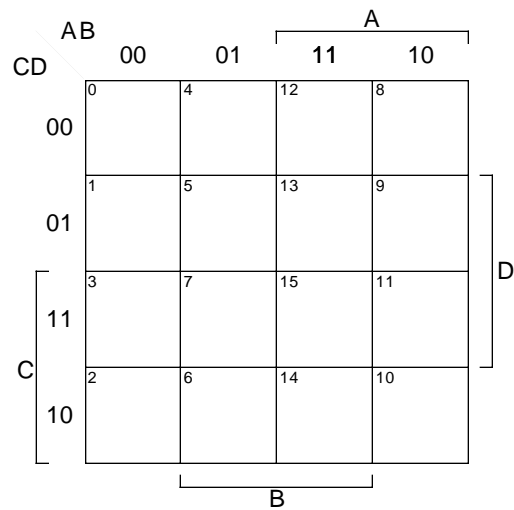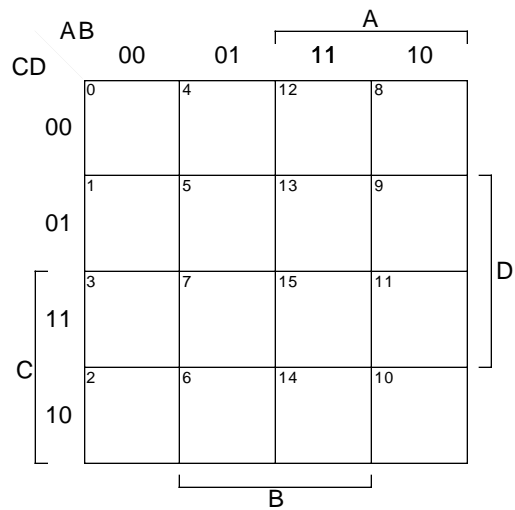- (a) $f(A, B, C) = \sum m(2, 3, 4, 5)$
- (b) $f(A, B, C, D) = \sum m(0, 1, 4, 6, 9, 13, 14, 15)$
- (c) $f(A, B, C, D) = \sum m(0, 1, 2, 8, 9, 10, 11, 12, 13, 14, 15)$
- (d) $f(A, B, C, D) = \sum m(2, 9, 10, 12, 13) + d(1, 5, 14)$
- (e) $f(A, B, C, D) = \sum m(1, 3, 6, 7) + d(4, 9, 11)$



Next Time

- **Quine-McCluskey**
- **Flip Flops**