

**Due: November 11, 2004**

1. (30 points) Draw schematics for the following functions using AND, OR and NOT gates. (Do not simplify the formulas.)

(a)  $\overline{X}Y + XY\overline{Z} + XYZ$

(b)  $(X\overline{Y} + \overline{W}Z)(W\overline{X} + Y\overline{Z})$

(c)  $\overline{(X + Y)}(\overline{X} + \overline{Y})$

2. (30 points) Using the postulates and theorems of Boolean algebra in Table A-1 (p. 451), simplify the following formulas. *Show all of your work.*

(a)  $WXYZ(WXY\overline{Z} + W\overline{X}YZ + \overline{W}XYZ + WX\overline{Y}Z)$

(b)  $AB + AB\overline{C}D + ABDE\overline{E} + AB\overline{C}E + \overline{C}DE$

(c)  $MNO + \overline{Q}P\overline{N} + PRM + \overline{Q}OM\overline{P} + MR$


3. (40 points) For each CMOS circuit below,

(a) Provide a truth table for the circuit's function.


(b) For diagram (a), write down the Sum-of-Products (SOP) Boolean formula for the truth table. For diagram (b), write down the Product-of-Sums (POS) Boolean formula.

(c) Simplify the SOP or POS formula using the postulates and theorems of Boolean Algebra (p. 451). *Show all work.*

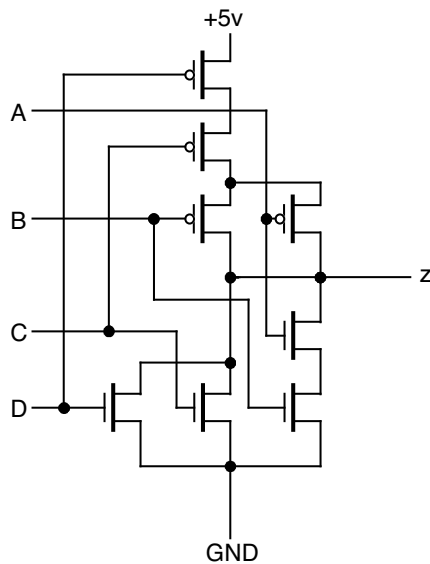(d) Draw the logic diagram of the simplified formula using AND, OR, NAND, NOR and NOT gates.



(a)

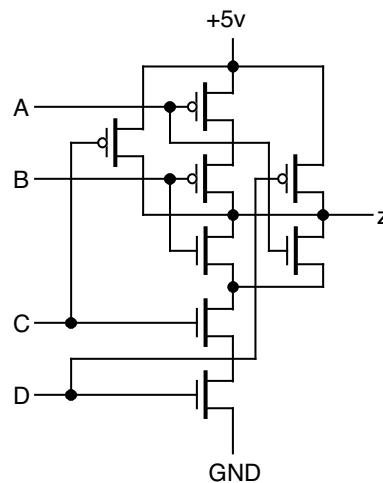

(b)