

CMSC 313 Lecture 18

- **Midterm Exam returned**
- **Assign Homework 3**
- **Circuits for Addition**
- **Digital Logic Components**
- **Programmable Logic Arrays**

Due: November 11, 2004

1. (30 points) Draw schematics for the following functions using AND, OR and NOT gates. (Do not simplify the formulas.)

(a) $\overline{X}Y + XY\overline{Z} + XYZ$

(b) $(X\overline{Y} + \overline{W}Z)(W\overline{X} + Y\overline{Z})$

(c) $\overline{(X + Y)}(\overline{X} + \overline{Y})$

2. (30 points) Using the postulates and theorems of Boolean algebra in Table A-1 (p. 451), simplify the following formulas. *Show all of your work.*

(a) $WXYZ(WXY\overline{Z} + W\overline{X}YZ + \overline{W}XYZ + WX\overline{Y}Z)$

(b) $AB + AB\overline{C}D + ABDE\overline{E} + AB\overline{C}E + \overline{C}DE$

(c) $MNO + \overline{Q}PN + PRM + \overline{Q}OMP + MR$


3. (40 points) For each CMOS circuit below,

(a) Provide a truth table for the circuit's function.


(b) For diagram (a), write down the Sum-of-Products (SOP) Boolean formula for the truth table. For diagram (b), write down the Product-of-Sums (POS) Boolean formula.

(c) Simplify the SOP or POS formula using the postulates and theorems of Boolean Algebra (p. 451). *Show all work.*

 (d) Draw the logic diagram of the simplified formula using AND, OR, NAND, NOR and NOT gates.



(a)

 

(b)

Last Time

- **Postulates & Theorems of Boolean Algebra**
- **Periodic Table & Semiconductors**
- **P-N junction**
- **Field-Effect Transistors**
- **CMOS Logic Gates**

Half Adder

- **Inputs:** A and B
- **Outputs:** S = lower bit of $A + B$, c_{out} = carry bit

A	B	S	c_{out}
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

- Using Sum-of-Products: $S = \overline{A}B + A\overline{B}$, $c_{\text{out}} = AB$.
- Alternatively, we could use XOR: $S = A \oplus B$.

Full Adder


- **Inputs:** A , B and c_{in}
- **Outputs:** S = lower bit of $A + B$, c_{out} = carry bit

A	B	c_{in}	S	c_{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

- $S = \overline{A}\overline{B}C + \overline{A}B\overline{C} + A\overline{B}\overline{C} + ABC = A \oplus B \oplus C.$
- $c_{out} = \text{MAJ3} = AB + BC + AC.$


Ripple Carry Adder

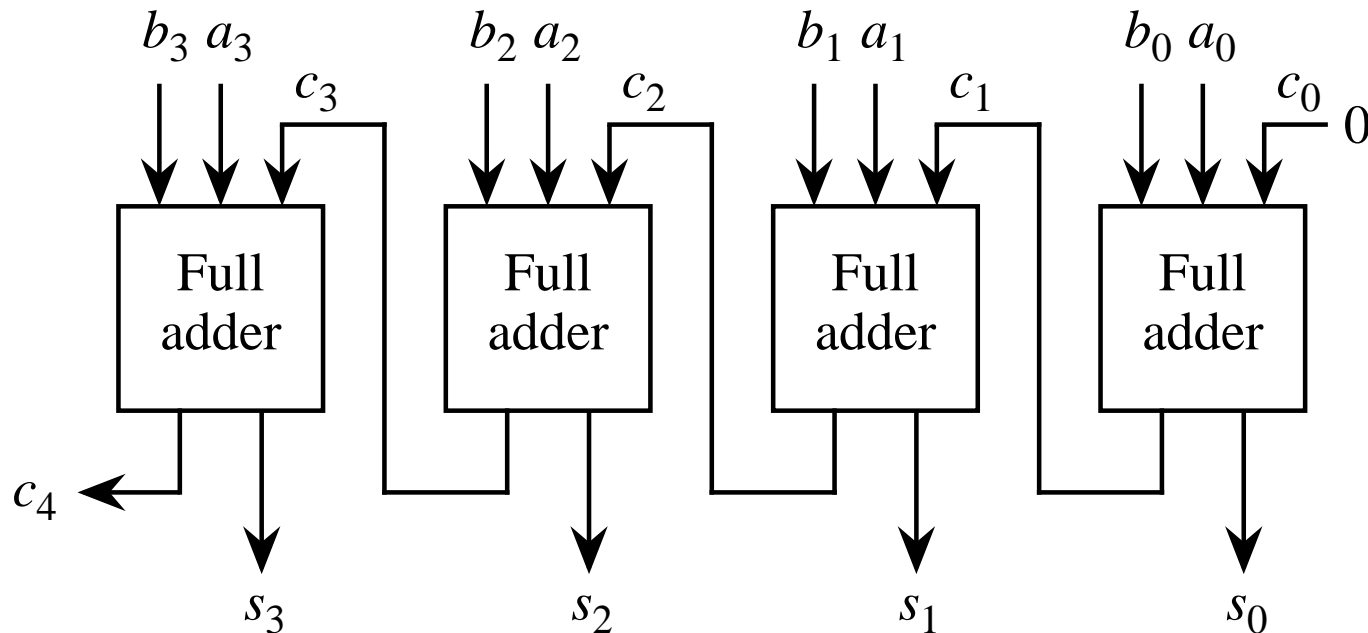- Two binary numbers A and B are added from right to left, creating a sum and a carry at the outputs of each full adder for each bit position.



Constructing Larger Adders

 
- A 16-bit adder can be made up of a cascade of four 4-bit ripple-carry adders.



Full Subtractor


- Truth table and schematic symbol for a ripple-borrow subtractor:

a_i	b_i	bor_i	$diff_i$	bor_{i+1}
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

 


Ripple-Borrow Subtractor

 - A ripple-borrow subtractor can be composed of a cascade of full subtractors.
- Two binary numbers A and B are subtracted from right to left, creating a difference and a borrow at the outputs of each full subtractor for each bit position.



Combined Adder/Subtractor

 - A single ripple-carry adder can perform both addition and subtraction, by forming the two's complement negative for B when subtracting. (Note that $+1$ is added at c_0 for two's complement.)



Carry-Lookahead Addition

$$s_i = \bar{a}_i \bar{b}_i c_i + \bar{a}_i b_i \bar{c}_i + a_i \bar{b}_i \bar{c}_i + a_i b_i c_i$$

$$c_{i+1} = b_i c_i + a_i c_i + a_i b_i$$

$$c_{i+1} = a_i b_i + (a_i + b_i) c_i$$

$$c_{i+1} = G_i + P_i c_i$$

- Carries are represented in terms of G_i (generate) and P_i (propagate) expressions.

$$G_i = a_i b_i \quad \text{and} \quad P_i = a_i + b_i$$

$$c_0 = 0$$


$$c_1 = G_0$$

$$c_2 = G_1 + P_1 G_0$$

$$c_3 = G_2 + P_2 G_1 + P_2 P_1 G_0$$

$$c_4 = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0$$

Carry Lookahead Adder

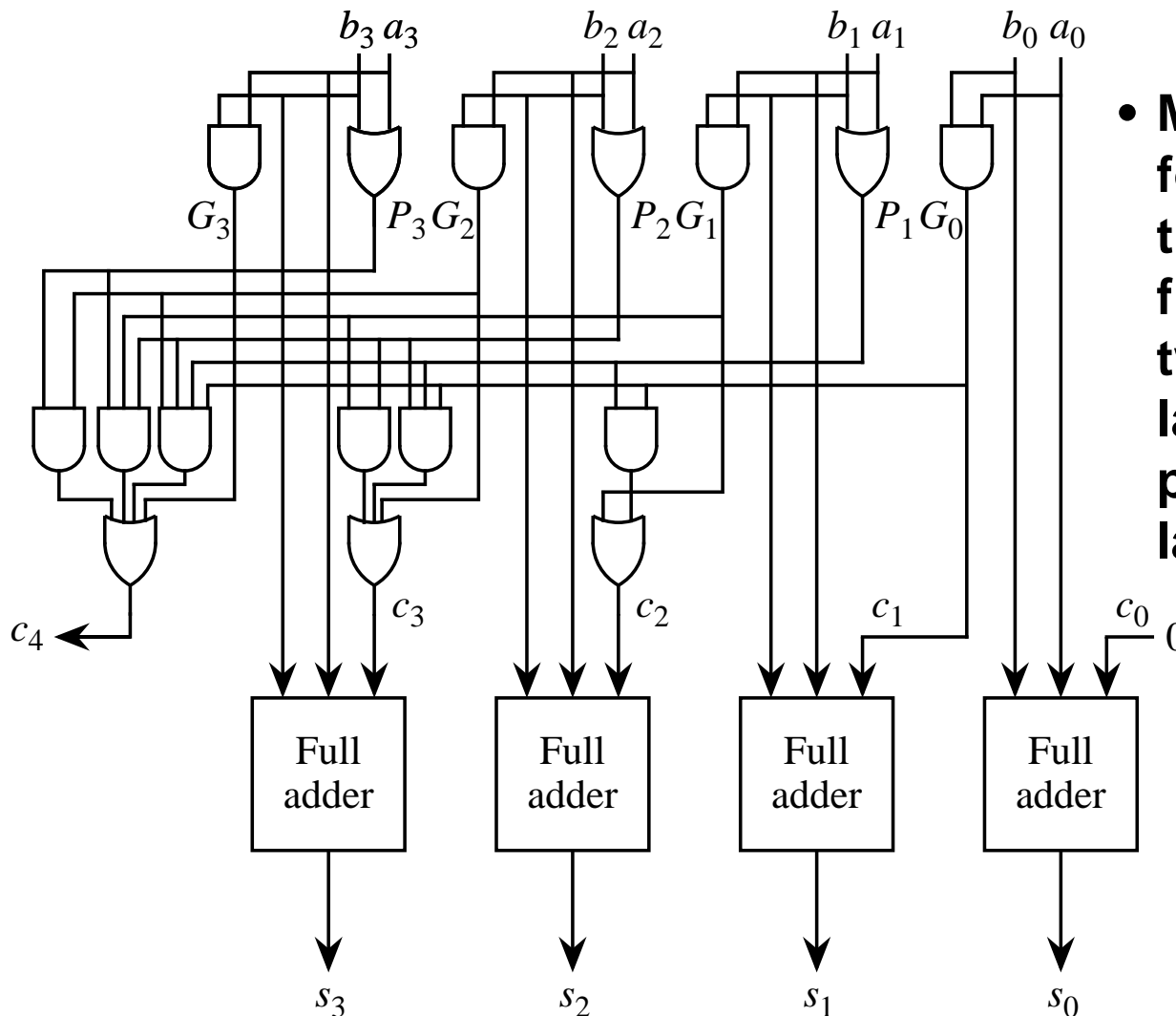


- Maximum gate delay for the carry generation is only 3. The full adders introduce two more gate delays. Worst case path is 5 gate delays.

Digital Components

- High level digital circuit designs are normally created using collections of logic gates referred to as *components*, rather than using individual logic gates.
- Levels of integration (numbers of gates) in an integrated circuit (IC) can roughly be considered as:
 - Small scale integration (SSI): 10-100 gates.
 - Medium scale integration (MSI): 100 to 1000 gates.
 - Large scale integration (LSI): 1000-10,000 logic gates.
 - Very large scale integration (VLSI): 10,000-upward logic gates.
 - These levels are approximate, but the distinctions are useful in comparing the relative complexity of circuits.


Multiplexer

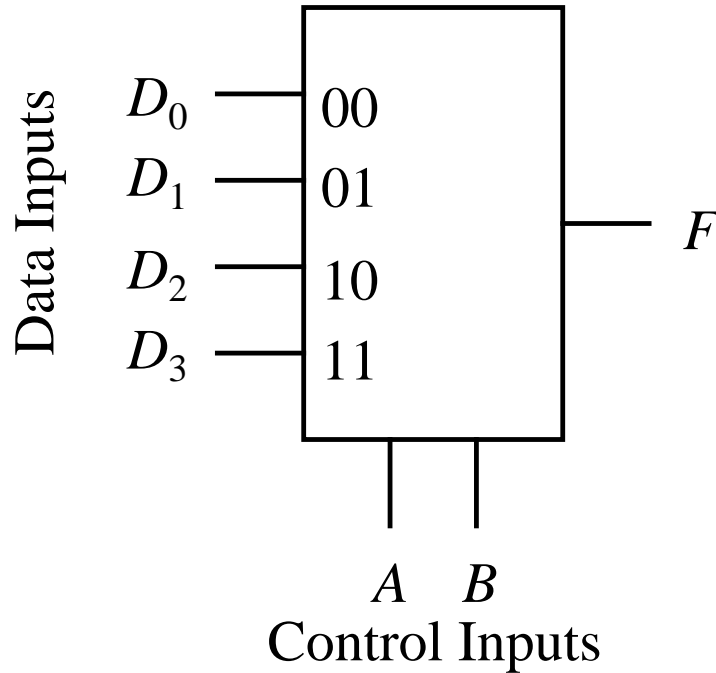

A	B	F
0	0	D_0
0	1	D_1
1	0	D_2
1	1	D_3

$$F = \bar{A} \bar{B} D_0 + \bar{A} B D_1 + A \bar{B} D_2 + A B D_3$$


AND-OR Implementation of MUX

 

MUX Implementation of Majority

- Principle: Use the 3 MUX control inputs to select (one at a time) the 8 data inputs.

<i>A</i>	<i>B</i>	<i>C</i>	<i>M</i>
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

 

4-to-1 MUX Implements 3-Var Function

- **Principle:** Use the A and B inputs to select a pair of minterms. The value applied to the MUX data input is selected from $\{0, 1, C, \bar{C}\}$ to achieve the desired behavior of the minterm pair.

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

