


CMSC 313 Lecture 19

- **Combinational Logic Components**
- **Programmable Logic Arrays**
- **Karnaugh Maps**

Last Time & Before

- Returned midterm exam
- Half adders & full adders
- Ripple carry adders vs carry lookahead adders
- Propagation delay
- Multiplexers


Multiplexer

 

A	B	F
0	0	D_0
0	1	D_1
1	0	D_2
1	1	D_3

$$F = \bar{A} \bar{B} D_0 + \bar{A} B D_1 + A \bar{B} D_2 + A B D_3$$

Demultiplexer

 


$$F_0 = D \bar{A} \bar{B} \quad F_2 = D A \bar{B}$$


$$F_1 = D \bar{A} B \quad F_3 = D A B$$

D	A	B	F_0	F_1	F_2	F_3
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	0	0	0	0
0	1	1	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1

Gate-Level Implementation of DEMUX

 

Decoder

 

		Enable = 1			
A	B	D_0	D_1	D_2	D_3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

		Enable = 0			
A	B	D_0	D_1	D_2	D_3
0	0	0	0	0	0
0	1	0	0	0	0
1	0	0	0	0	0
1	1	0	0	0	0


$$D_0 = \overline{A} \overline{B}$$

$$D_1 = \overline{A} B$$

$$D_2 = A \overline{B}$$


$$D_3 = A B$$

Gate-Level Implementation of Decoder

 


Decoder Implementation of Majority Function

 - **Note that the enable input is not always present. We use it when discussing decoders for memory.**



Priority Encoder

 - An encoder translates a set of inputs into a binary encoding.
- Can be thought of as the converse of a decoder.
- A priority encoder imposes an order on the inputs.
- A_i has a higher priority than A_{i+1}




$$F_0 = \overline{A_0} \overline{A_1} A_3 + \overline{A_0} A_1 A_2$$

$$F_1 = \overline{A_0} A_2 A_3 + \overline{A_0} A_1$$



A_0	A_1	A_2	A_3	F_0	F_1
0	0	0	0	0	0
0	0	0	1	1	1
0	0	1	0	1	0
0	0	1	1	1	0
0	1	0	0	0	1
0	1	0	1	0	1
0	1	1	0	0	1
0	1	1	1	0	1
1	0	0	0	0	0
1	0	0	1	0	0
1	0	1	0	0	0
1	0	1	1	0	0
1	1	0	0	0	0
1	1	0	1	0	0
1	1	1	0	0	0
1	1	1	1	0	0

 AND-OR Implementation of Priority Encoder




Programmable Logic Array

  - A PLA is a customizable AND matrix followed by a customizable OR matrix.
- Black box view of PLA:




 Simplified Representation of PLA Implementation of Majority Function




Full Adder

A_i	B_i	C_i	S_i	C_{i+1}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

 

PLA Realization of Full Adder


 


Reduction (Simplification) of Boolean Expressions

- It is usually possible to simplify the canonical SOP (or POS) forms.
- A smaller Boolean equation generally translates to a lower gate count in the target circuit.
- We cover three methods: algebraic reduction, Karnaugh map reduction, and tabular (Quine-McCluskey) reduction.

Karnaugh Maps: Venn Diagram Representation of Majority Function

  - Each distinct region in the “Universe” represents a minterm.
- This diagram can be transformed into a *Karnaugh Map*.



K-Map for Majority Function

- Place a “1” in each cell that corresponds to that minterm.
- Cells on the outer edge of the map “wrap around”

Minterm Index	A	B	C	F
0	0	0	0	0
1	0	0	1	0
2	0	1	0	0
3	0	1	1	1
4	1	0	0	0
5	1	0	1	1
6	1	1	0	1
7	1	1	1	1


		AB			
		00	01	11	10
C	0			1	
	1		1	1	1

Adjacency Groupings for Majority Function

$C \backslash AB$	00	01	11	10
0			1	
1		1	1	1


- $F = BC + AC + AB$


Minimized AND-OR Majority Circuit

 


- $F = BC + AC + AB$
- The K-map approach yields the same minimal two-level form as the algebraic approach.

K-Map Groupings

 - Minimal grouping is on the left, non-minimal (but logically equivalent) grouping is on the right.
- To obtain minimal grouping, create *smallest* groups first. 



 
$$F = \bar{A}B\bar{C} + \bar{A}CD + ABC + A\bar{C}D$$




$$F = BD + \bar{A}B\bar{C} + \bar{A}CD + ABC + A\bar{C}D$$

Example Requiring More Rules

 


K-Map Corners are Logically Adjacent

 


$$F = B C D + \bar{B} \bar{D} + \bar{A} B$$

K-Maps and Don't Cares

 - There can be more than one minimal grouping, as a result of don't cares.


 
$$F = \overline{B} \overline{C} \overline{D} + B D$$




$$F = \overline{A} \overline{B} \overline{D} + B D$$

Gray Code

- Two bits: 00, 01, 11, 10
- Three bits: 000, 001, 011, 010, 110, 111, 101, 100
- Successive bit patterns only differ at 1 position
- For Karnaugh maps, adjacent 1's represent minterms that can be simplified using the rule:


 
$$ABC' + A'BC' = (A + A')BC' = 1 BC' = BC'$$



Karnaugh Maps

- ◇ **Implicant:** rectangle with 1, 2, 4, 8, 16 ... 1's
- ◇ **Prime Implicant:** an implicant that cannot be extended into a larger implicant
- ◇ **Essential Prime Implicant:** the only prime implicant that covers some 1
- ◇ **K-map Algorithm (not from M&H):**
 1. Find ALL the prime implicants. Be sure to check every 1 and to use don't cares.
 2. Include all essential prime implicants.
 3. Try all possibilities to find the minimum cover for the remaining 1's.

K-map Example

  

$$A'B + AC'D + AB'D'$$

Notes on K-maps

- Also works for POS
- Takes 2^n time for formulas with n variables
- Only optimizes two-level logic
 - ◇ Reduces number of terms, then number of literals in each term
- Assumes inverters are free
- Does not consider minimizations across functions
- Circuit minimization is generally a hard problem
- Quine-McCluskey can be used with more variables
- CAD tools are available if you are serious

Circuit Minimization is Hard

- **Unix systems store passwords in encrypted form.**
 - ◇ User types in x , system computes $f(x)$ and looks for $f(x)$ in a file.
- **Suppose we use 64-bit passwords and I want to find the password x , such that $f(x) = y$. Let**
$$g_i(x) = 0 \text{ if } f(x) = y \text{ and the } i\text{th bit of } x \text{ is } 0$$
$$1 \text{ otherwise.}$$
- **If the i th bit of x is 1, then $g_i(x)$ outputs 1 for every x and has a very, very simple circuit.**
- **If you can simplify every circuit quickly, then you can crack passwords quickly.**

3-Level Majority Circuit

- K-Map Reduction results in a reduced two-level circuit (that is, AND followed by OR. Inverters are not included in the two-level count). Algebraic reduction can result in multi-level circuits with even fewer logic gates and fewer inputs to the logic gates.

