

# CMSC 313 Lecture 20

- **More Karnaugh Map examples**
- **Quine-McCluskey (Tabular Reduction)**

# Last Time

- **Combinational logic components**
- **Introduction to Karnaugh Maps**

# Notes on K-maps


- Also works for POS
- Takes  $2^n$  time for formulas with  $n$  variables
- Only optimizes two-level logic
  - ◇ Reduces number of terms, then number of literals in each term
- Assumes inverters are free
- Does not consider minimizations across functions
- Circuit minimization is generally a hard problem
- Quine-McCluskey can be used with more variables
- CAD tools are available if you are serious

# Circuit Minimization is Hard

- **Unix systems store passwords in encrypted form.**
  - ◇ User types in  $x$ , system computes  $f(x)$  and looks for  $f(x)$  in a file.
- **Suppose we use 64-bit passwords and I want to find the password  $x$ , such that  $f(x) = y$ . Let**  
$$g_i(x) = \begin{cases} 0 & \text{if } f(x) = y \text{ and the } i\text{th bit of } x \text{ is } 0 \\ 1 & \text{otherwise.} \end{cases}$$
- **If the  $i$ th bit of  $x$  is 1, then  $g_i(x)$  outputs 1 for every  $x$  and has a very, very simple circuit.**
- **If you can simplify every circuit quickly, then you can crack passwords quickly.**






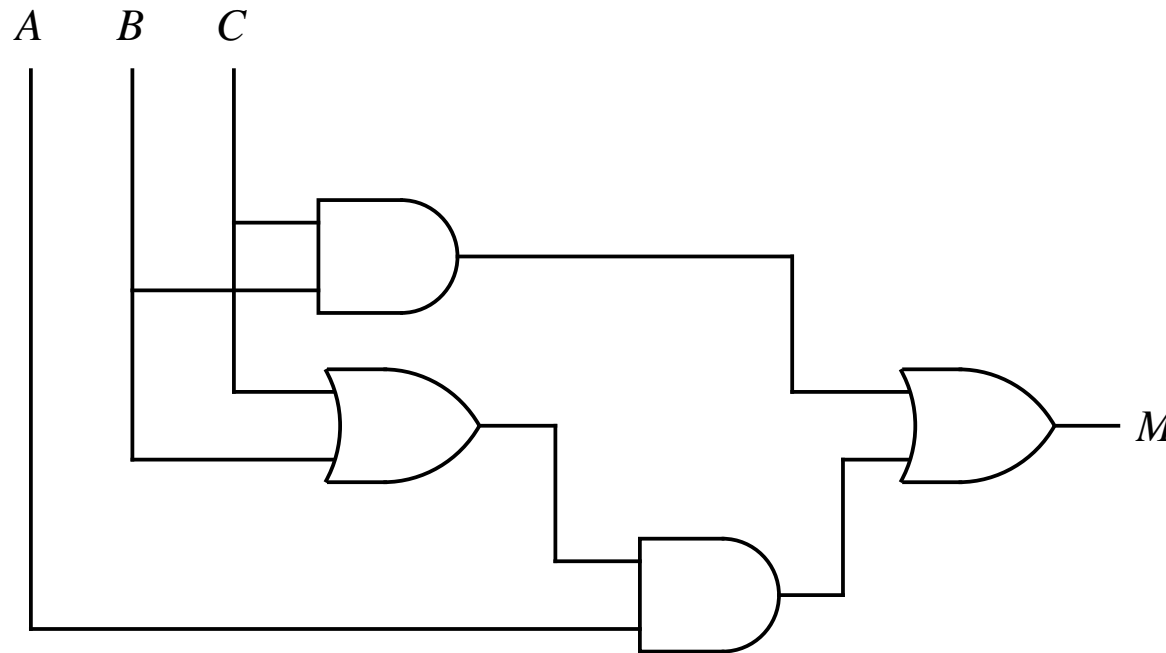
# 3-Level Majority Circuit

- K-Map Reduction results in a reduced two-level circuit (that is, AND followed by OR. Inverters are not included in the two-level count). Algebraic reduction can result in multi-level circuits with even fewer logic gates and fewer inputs to the logic gates.


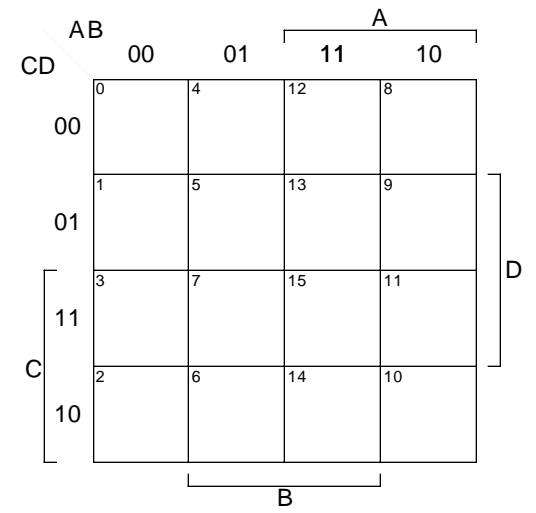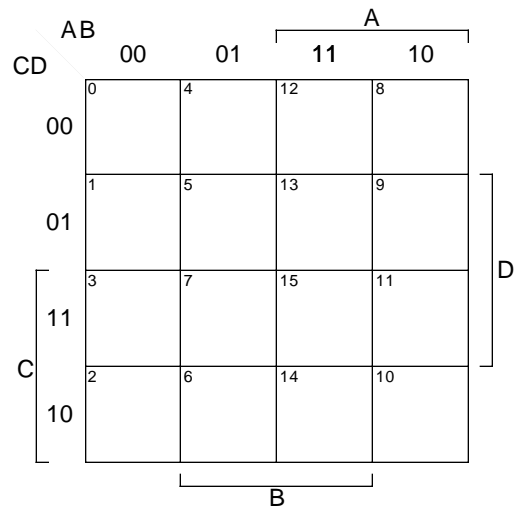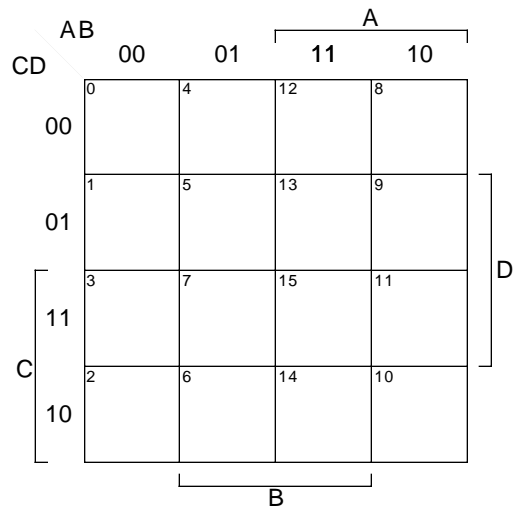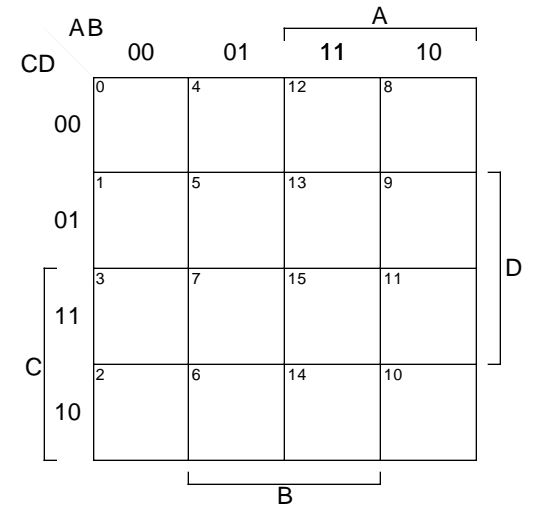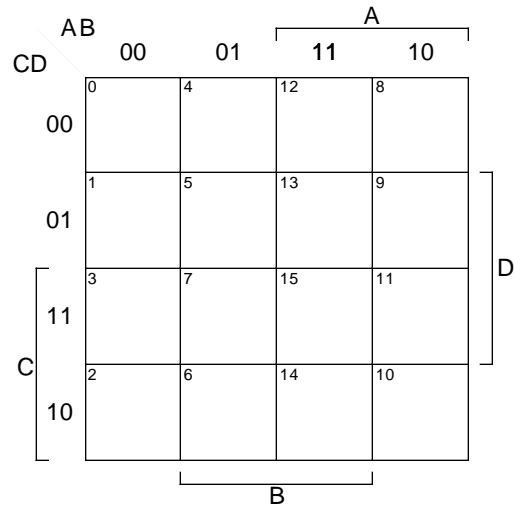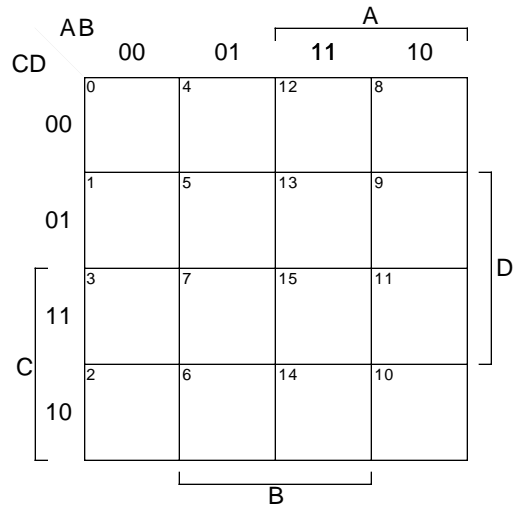
# Karnaugh Maps

- ◇ **Implicant:** rectangle with 1, 2, 4, 8, 16 ... 1's
- ◇ **Prime Implicant:** an implicant that cannot be extended into a larger implicant
- ◇ **Essential Prime Implicant:** the only prime implicant that covers some 1
- ◇ **K-map Algorithm (not from M&H):**
  1. Find ALL the prime implicants. Be sure to check every 1 and to use don't cares.
  2. Include all essential prime implicants.
  3. Try all possibilities to find the minimum cover for the remaining 1's.



**Due: Thursday, November 18, 2003**

1. (10 points) Question 3.9, page 96, Murdocca & Heuring
2. (10 points) Question 3.14, page 97, Murdocca & Heuring
3. (10 points) Question A.12, page 494, Murdocca & Heuring
4. (50 points) In the following, the notation  $\sum m(x_1, \dots, x_j)$  indicates a Boolean function that is the sum of the minterms  $x_1, \dots, x_j$ , where  $x_i$  is the  $i$ th minterm in canonical ordering — i.e., the  $i$ th row of the truth table where the input values are ordered as binary numbers. Similarly,

$$\sum m(x_1, \dots, x_j) + d(y_1, \dots, y_k)$$

indicates a Boolean function that is the sum of the minterms  $x_1, \dots, x_j$  and whose values for rows  $y_1, \dots, y_k$  of the truth table are *don't cares*.


Minimize the following functions using Karnaugh maps. Then, write down a Boolean formula in sum-of-products or product-of-sums form for each function. Show your work (including the Karnaugh maps).

- (a)  $f(A, B, C, D) = \sum m(0, 1, 2, 8, 9, 14, 15)$
- (b)  $f(A, B, C, D) = \sum m(0, 2, 3, 4, 7, 8, 9, 10, 11, 12, 13, 15)$
- (c)  $f(A, B, C, D) = \sum m(2, 3, 4, 5, 6, 7, 8, 9, 10, 13)$
- (d)  $f(A, B, C, D) = \sum m(4, 12, 13, 14, 15) + d(0, 3, 5, 8)$
- (e)  $f(A, B, C, D) = \sum m(0, 2, 4, 8, 10, 12, 13) + d(5, 14, 15)$


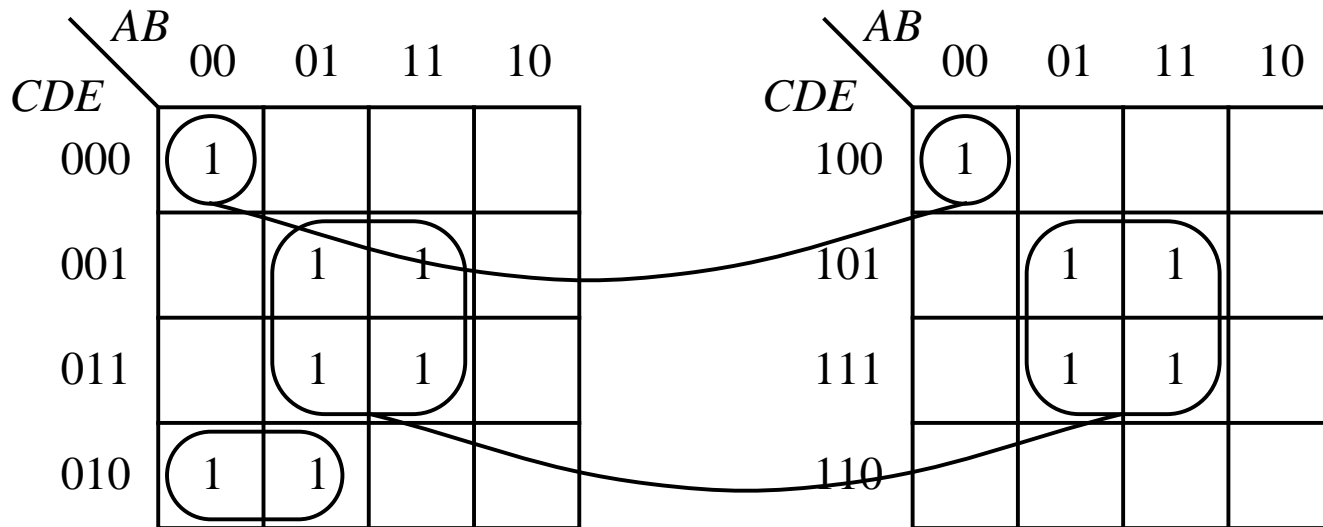
# Five-Variable K-Map


- Visualize two 4-variable K-maps stacked one on top of the other; groupings are made in three dimensional cubes.



$$F = \overline{A} \overline{C} D \overline{E} + \overline{A} B \overline{D} \overline{E} + B E$$
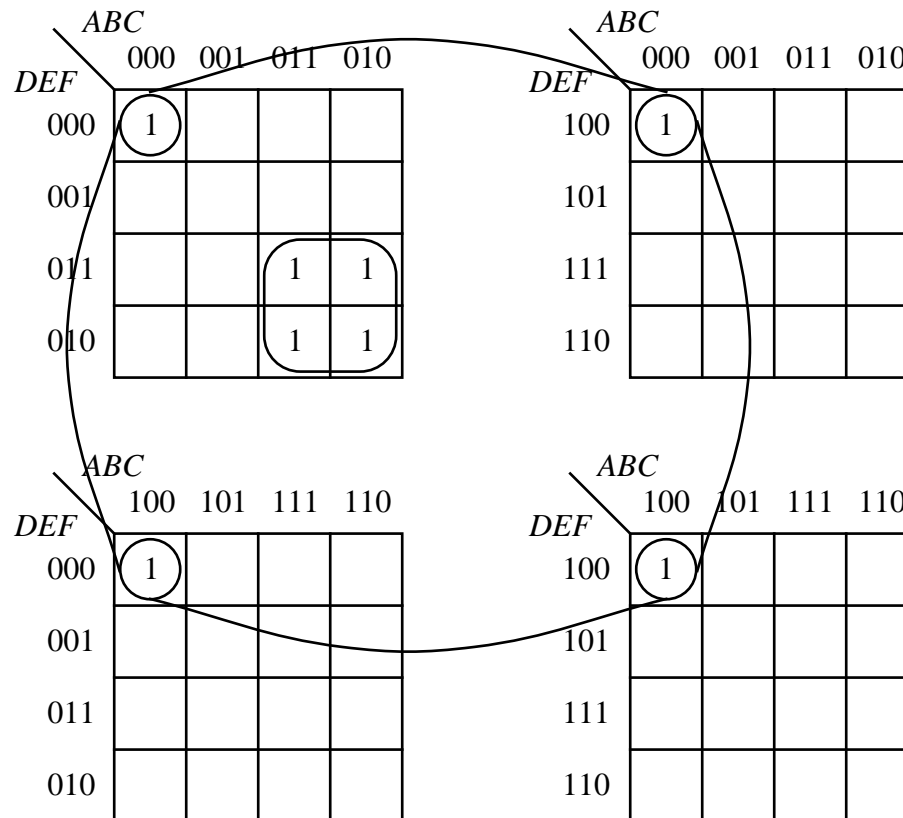
# Six-Variable K-Map

- Visualize four 4-variable K-maps stacked one on top of the other; groupings are made in three dimensional cubes.



$$G = \overline{B} \overline{C} \overline{E} \overline{F} + \overline{A} B \overline{D} E$$

# Truth Table with Don't Cares

- A truth table representation of a single function with don't cares.

<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>F</i>
0	0	0	0	<i>d</i>
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	<i>d</i>
1	1	0	0	0
1	1	0	1	1
1	1	1	0	0
1	1	1	1	<i>d</i>

# Tabular (Quine-McCluskey) Reduction

- Tabular reduction begins by grouping minterms for which  $F$  is nonzero according to the number of 1's in each minterm. Don't cares are considered to be nonzero.
- The next step forms a consensus (the logical form of a cross product) between each pair of adjacent groups for all terms that differ in only one variable.

Initial setup

A	B	C	D	
0	0	0	0	√
0	0	0	1	√
0	0	1	1	√
0	1	0	1	√
0	1	1	0	√
1	0	1	0	√
0	1	1	1	√
1	0	1	1	√
1	1	0	1	√
1	1	1	1	√

(a)

After first reduction

A	B	C	D	
0	0	0	-	*
0	0	-	1	√
0	-	0	1	√
0	-	1	1	√
-	0	1	1	√
0	1	-	1	√
-	1	0	1	√
0	1	1	-	*
1	0	1	-	*
-	1	1	1	√
1	-	1	1	√
1	1	-	1	√

(b)

After second reduction

A	B	C	D	
0	-	-	1	*
-	-	1	1	*
-	1	-	1	*

(c)

# Table of Choice

- The prime implicants form a set that completely covers the function, although not necessarily minimally.
- A *table of choice* is used to obtain a minimal cover set.

Prime Implicants	Minterms						
	0001	0011	0101	0110	0111	1010	1101
0 0 0 _	√						
* 0 1 1 _				√	√		
* 1 0 1 _						√	
0 _ _ 1	√	√	√		√		
_ _ 1 1		√			√		
* _ 1 _ 1			√		√		√

# Reduced Table of Choice

- In a reduced table of choice, the essential prime implicants and the minterms they cover are removed, producing the *eligible set*.
- $F = \bar{A}BC + A\bar{B}C + BD + \bar{A}D$

Eligible Set	Minterms	
	0001	0011
X 000_	√	
Y 0__1	√	√
Z __11		√

Set 1      Set 2  
 000\_      0\_\_1  
 \_\_11

# Multiple Output Truth Table

- The power of tabular reduction comes into play for multiple functions, in which minterms can be shared among the functions.

Minterm	A	B	C	$F_0$	$F_1$	$F_2$
$m_0$	0	0	0	1	0	0
$m_1$	0	0	1	0	1	0
$m_2$	0	1	0	0	0	1
$m_3$	0	1	1	1	1	1
$m_4$	1	0	0	0	1	0
$m_5$	1	0	1	0	0	0
$m_6$	1	1	0	0	1	1
$m_7$	1	1	1	1	1	1

# Multiple Output Table of Choice

$$F_0(A,B,C) = \bar{A}\bar{B}\bar{C} + BC$$

$$F_1(A,B,C) = \bar{A}C + A\bar{C} + BC$$

$$F_2(A,B,C) = B$$

Prime Implicants	Min-terms	$F_0(A,B,C)$			$F_1(A,B,C)$					$F_2(A,B,C)$			
		$m_0$	$m_3$	$m_7$	$m_1$	$m_3$	$m_4$	$m_6$	$m_7$	$m_2$	$m_3$	$m_6$	$m_7$
$F_0$	* 0 0 0	√											
$F_1$	* 0 _ 1				√	√							
$F_1$	* 1 _ 0						√	√					
$F_2$	* _ 1 _									√	√	√	√
$F_{1,2}$	1 1 _							√	√			√	√
$F_{0,1,2}$	* _ 1 1		√	√		√			√		√		√