

Due: TUESDAY, November 27, 2012

1. (30 points) Draw schematics for the following functions using AND, OR and NOT gates. (Do not simplify the formulas.)

(a) $\bar{X}Y + XY\bar{Z} + XYZ$

(b) $(X\bar{Y} + \bar{W}Z)(W\bar{X} + Y\bar{Z})$

(c) $\overline{(X + Y)(\bar{X} + \bar{Y})}$

2. (30 points) Using the Basic Identities of Boolean Algebra in Table 3.5 (p. 125), simplify the following formulas. *Show all of your work.*

(a) $WXYZ(WXY\bar{Z} + W\bar{X}YZ + \bar{W}XYZ + WX\bar{Y}Z)$

(b) $AB + AB\bar{C}D + ABDE + AB\bar{C}E + \bar{C}DE$

(c) $MNO + \bar{Q}P\bar{N} + PRM + \bar{Q}OMP + MR$


3. (40 points) For each CMOS circuit below,

(a) Provide a truth table for the circuit's function.


(b) For diagram (a), write down the Sum-of-Products (SOP) Boolean formula for the truth table. For diagram (b), write down the Product-of-Sums (POS) Boolean formula.

(c) Simplify the SOP or POS formula using the Basic Identities of Boolean Algebra (p. 125). *Show all work.*

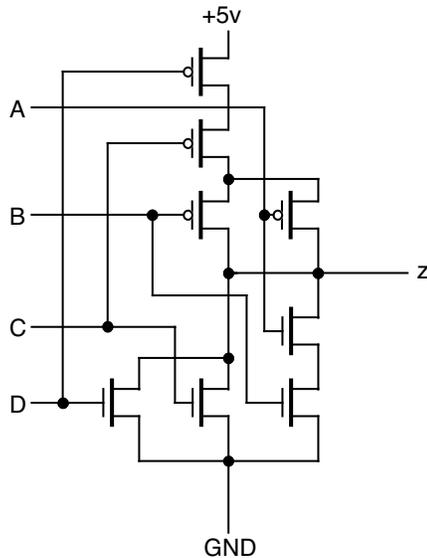(d) Draw the logic diagram of the simplified formula using AND, OR, NAND, NOR and NOT gates.



(a)

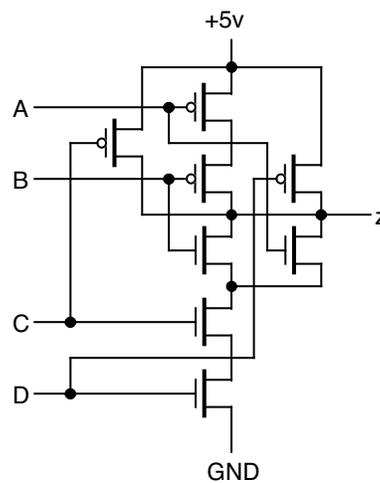

(b)