

CMSC 313
COMPUTER ORGANIZATION
&
ASSEMBLY LANGUAGE
PROGRAMMING

LECTURE 22, FALL 2012



TOPICS TODAY

- **Circuits for Addition**
- **Standard Logic Components**
- **Logisim Demo**



CIRCUITS FOR ADDITION



3.5 Combinational Circuits

- Combinational logic circuits give us many useful devices.
- One of the simplest is the *half adder*, which finds the sum of two bits.
- We can gain some insight as to the construction of a half adder by looking at its truth table, shown at the right.

Inputs		Outputs	
X	Y	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Half Adder


- **Inputs:** A and B
- **Outputs:** S = lower bit of $A + B$, c_{out} = carry bit

A	B	S	c_{out}
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

- Using Sum-of-Products: $S = \overline{A}B + A\overline{B}$, $c_{\text{out}} = AB$.
- Alternatively, we could use XOR: $S = A \oplus B$.

 3.5 Combinational Circuits

- As we see, the sum can be found using the XOR operation and the carry using the AND operation.



Inputs		Outputs	
X	Y	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

3.5 Combinational Circuits

- We can change our half adder into to a full adder by including gates for processing the carry bit.
- The truth table for a full adder is shown at the right.

Inputs			Outputs	
X	Y	Carry In	Sum	Carry Out
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Full Adder


- **Inputs:** A , B and c_{in}
- **Outputs:** S = lower bit of $A + B$, c_{out} = carry bit

A	B	c_{in}	S	c_{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

- $S = \overline{A}\overline{B}C + \overline{A}B\overline{C} + A\overline{B}\overline{C} + ABC = A \oplus B \oplus C.$
- $c_{out} = \text{MAJ3} = AB + BC + AC.$

3.5 Combinational Circuits


- Here's our completed full adder.

 

Inputs			Outputs	
X	Y	Carry In	Sum	Carry Out
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

 3.5 Combinational Circuits


- Just as we combined half adders to make a full adder, full adders can be connected in series.
- The carry bit “ripples” from one adder to the next; hence, this configuration is called a *ripple-carry adder*.



Today's systems employ more efficient adders.

Constructing Larger Adders

 
- A 16-bit adder can be made up of a cascade of four 4-bit ripple-carry adders.



Full Subtractor


- Truth table and schematic symbol for a ripple-borrow subtractor:

a_i	b_i	bor_i	$diff_i$	bor_{i+1}
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

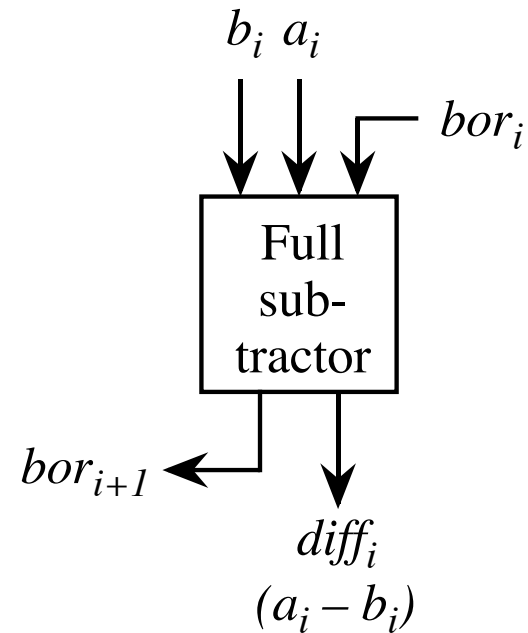

Combined Adder/Subtractor

 - A single ripple-carry adder can perform both addition and subtraction, by forming the two's complement negative for B when subtracting. (Note that $+1$ is added at c_0 for two's complement.)



Carry-Lookahead Addition

$$s_i = \bar{a}_i \bar{b}_i c_i + \bar{a}_i b_i \bar{c}_i + a_i \bar{b}_i \bar{c}_i + a_i b_i c_i$$

$$c_{i+1} = b_i c_i + a_i c_i + a_i b_i$$

$$c_{i+1} = a_i b_i + (a_i + b_i) c_i$$

$$c_{i+1} = G_i + P_i c_i$$

- Carries are represented in terms of G_i (generate) and P_i (propagate) expressions.

$$G_i = a_i b_i \quad \text{and} \quad P_i = a_i + b_i$$

$$c_0 = 0$$


$$c_1 = G_0$$

$$c_2 = G_1 + P_1 G_0$$

$$c_3 = G_2 + P_2 G_1 + P_2 P_1 G_0$$

$$c_4 = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0$$

Carry Lookahead Adder

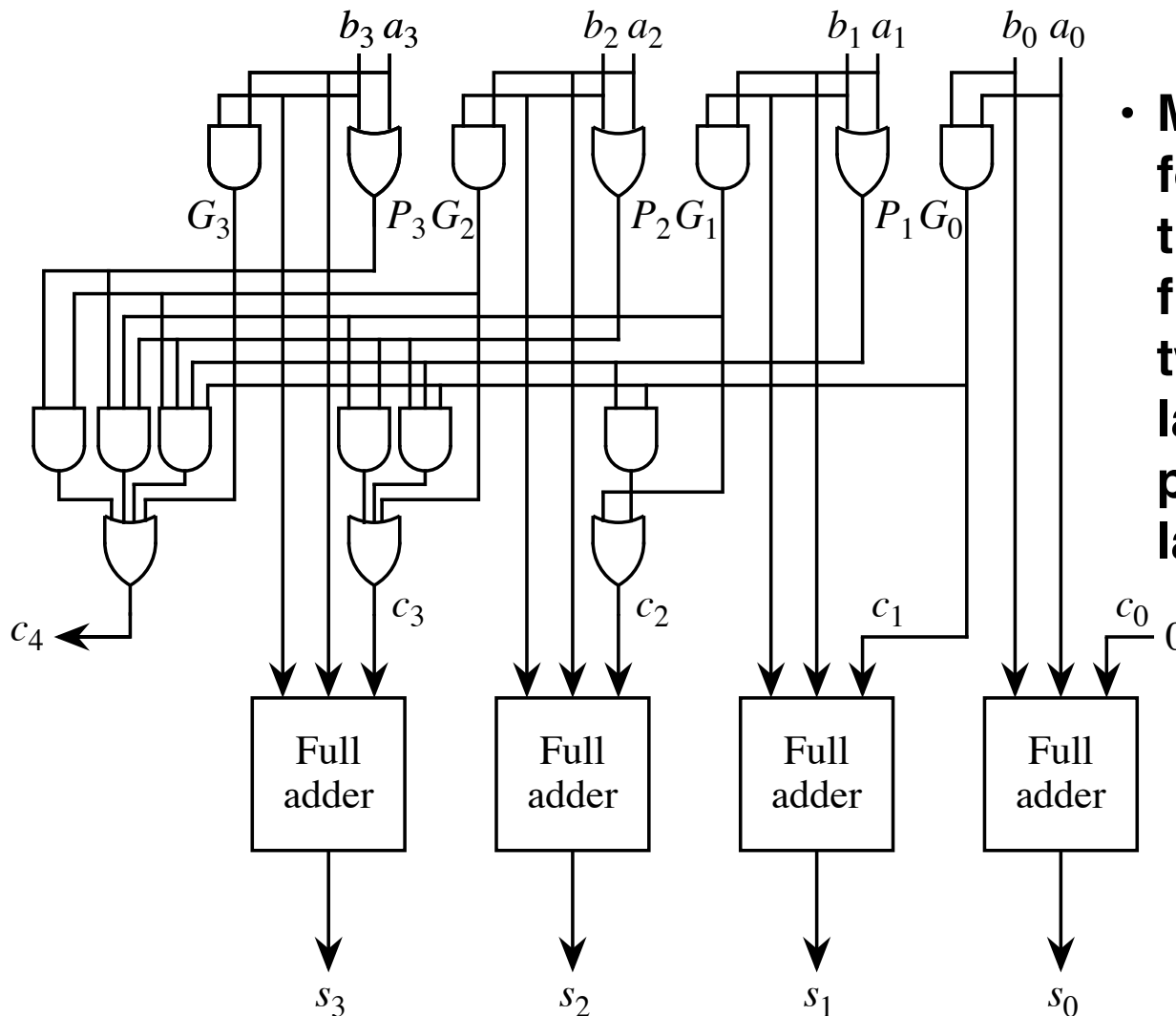

- Maximum gate delay for the carry generation is only 3. The full adders introduce two more gate delays. Worst case path is 5 gate delays.


STANDARD LOGIC COMPONENTS



3.5 Combinational Circuits


- Decoders are another important type of combinational circuit.
- Among other things, they are useful in selecting a memory location according a binary value placed on the address lines of a memory bus.
- Address decoders with n inputs can select any of 2^n locations.

This is a block diagram for a decoder.

 

 3.5 Combinational Circuits


- This is what a 2-to-4 decoder looks like on the inside.



**If $x = 0$ and $y = 1$,
which output line
is enabled?**

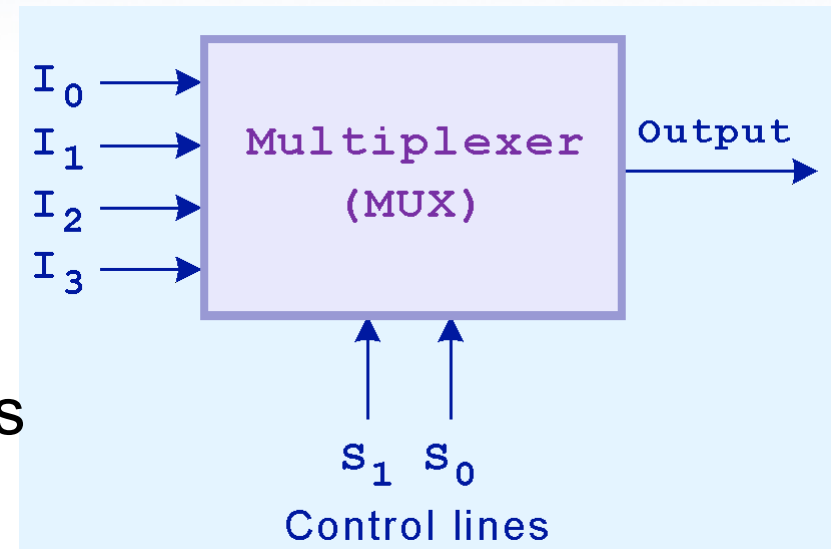3.5 Combinational Circuits


- A multiplexer does just the opposite of a decoder.
- It selects a single output from several inputs.
- The particular input chosen for output is determined by the value of the multiplexer's control lines.
- To be able to select among n inputs, $\log_2 n$ control lines are needed.



This is a block diagram for a multiplexer.

 
3.5 Combinational Circuits

- This is what a 4-to-1 multiplexer looks like on the inside.



**If $S_0 = 1$ and $S_1 = 0$,
which input is
transferred to the
output?**

Demultiplexer

 


D	A	B	F_0	F_1	F_2	F_3
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	0	0	0	0
0	1	1	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1

$$F_0 = D \overline{A} \overline{B} \quad F_2 = D A \overline{B}$$


$$F_1 = D \overline{A} B \quad F_3 = D A B$$

Gate-Level Implementation of DEMUX

 

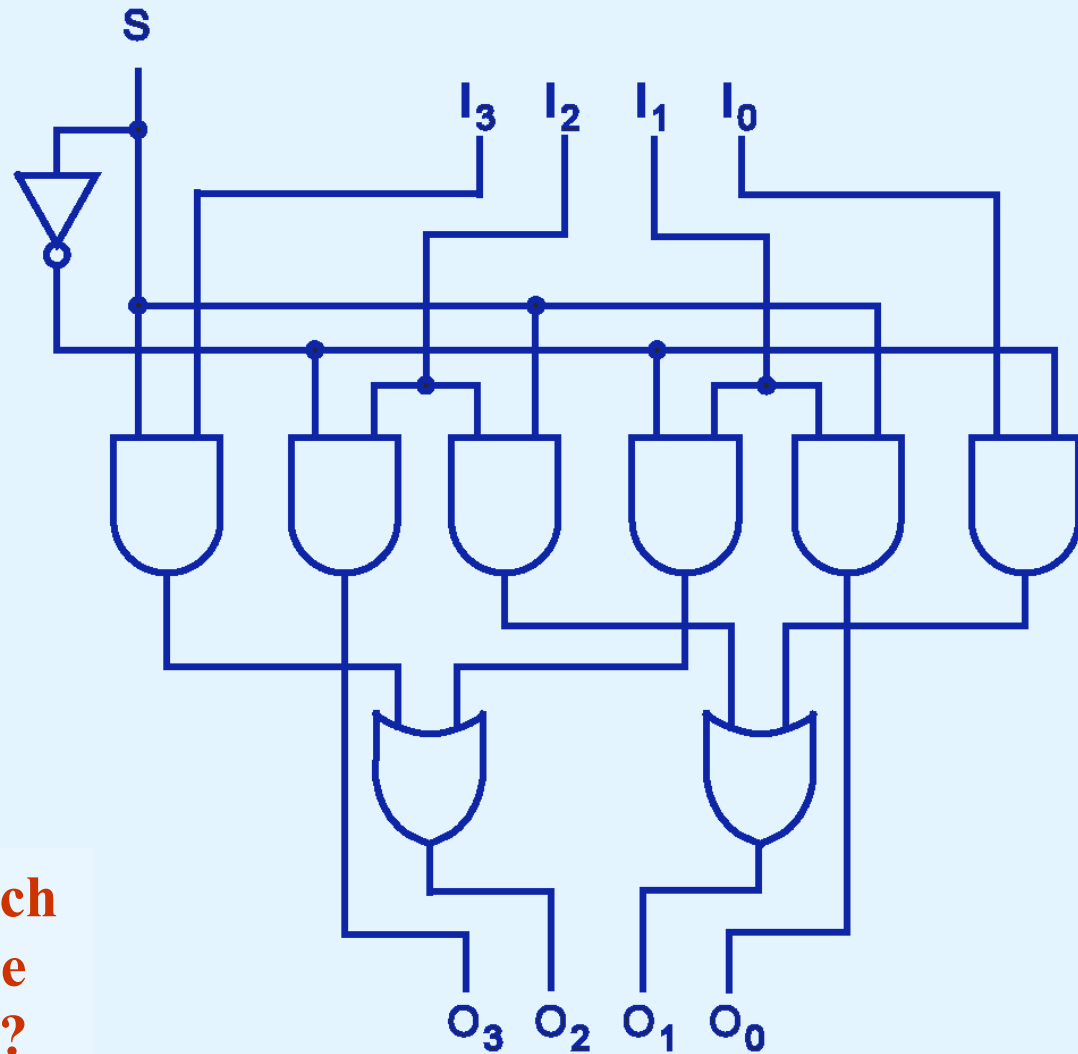3.5 Combinational Circuits

- This shifter moves the bits of a nibble one position to the left or right.



If $S = 0$, in which direction do the input bits shift?

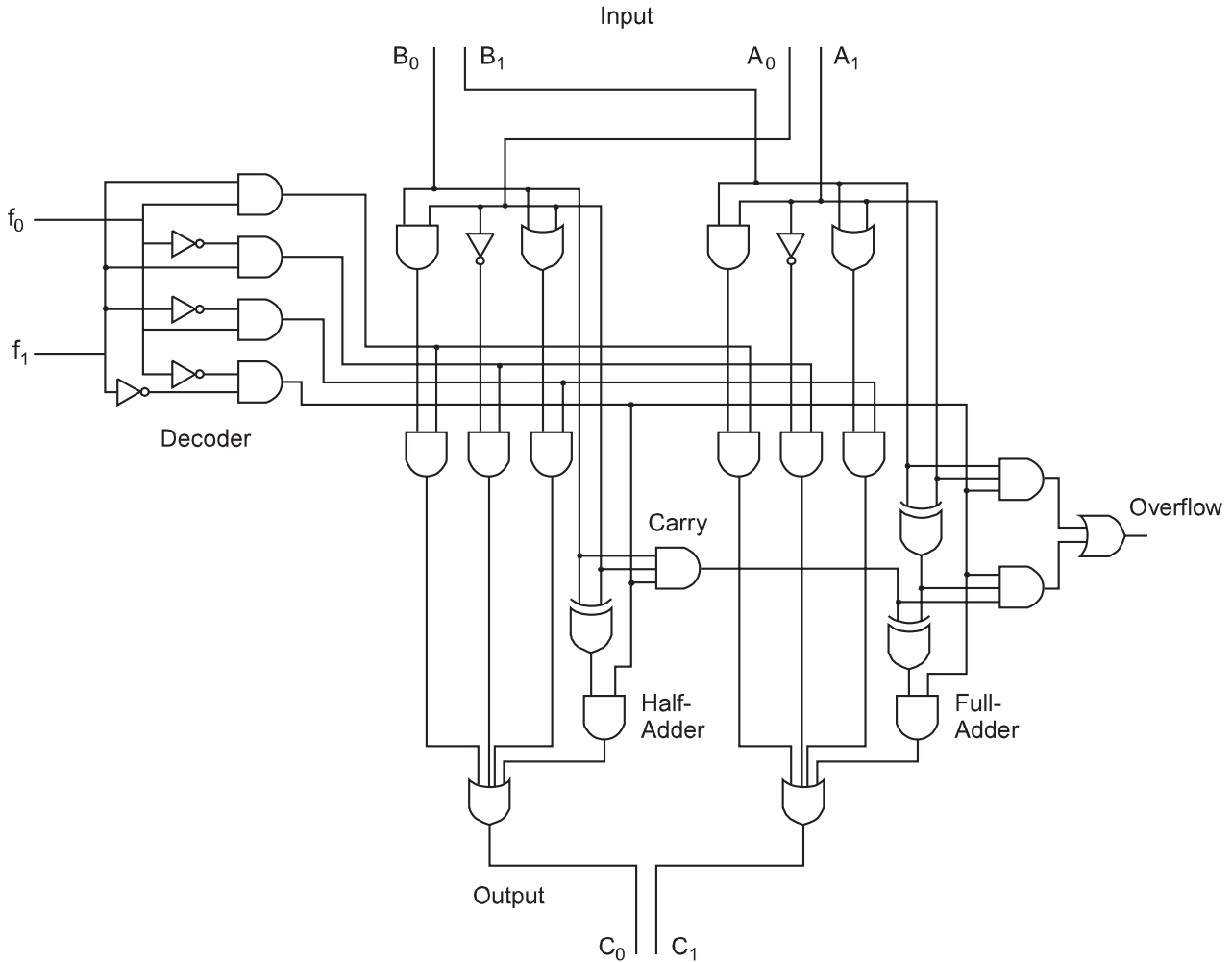


FIGURE 3.17 A Simple Two-Bit ALU

NEXT TIME

- 2-bit ALU
- Flip-flops

