

CMSC 313
COMPUTER ORGANIZATION
&
ASSEMBLY LANGUAGE
PROGRAMMING

LECTURE 25, FALL 2012

TOPICS TODAY

- **Finite State Machine Simplification**
- **A 2-bit "CPU"**



FINITE STATE MACHINE SIMPLIFICATION STEPS

- **Minimize combinational logic circuit (hard)**
- **Reduce number of states**
- **Apply state assignment heuristics**
- **Consider choice of flip flops (e.g., J-K vs D)**

**EXAMPLE:
SEQUENCE DETECTOR**




Example: A Sequence Detector

 - **Example:** Design a machine that outputs a 1 when exactly two of the last three inputs are 1.
- *e.g.* input sequence of 011011100 produces an output sequence of 001111010.
- Assume input is a 1-bit serial line.
- Use D flip-flops and 8-to-1 Multiplexers.
- Start by constructing a state transition diagram (next slide).


Sequence Detector State Transition Diagram

- Design a machine that outputs a 1 when exactly two of the last three inputs are 1.



Sequence Dectector

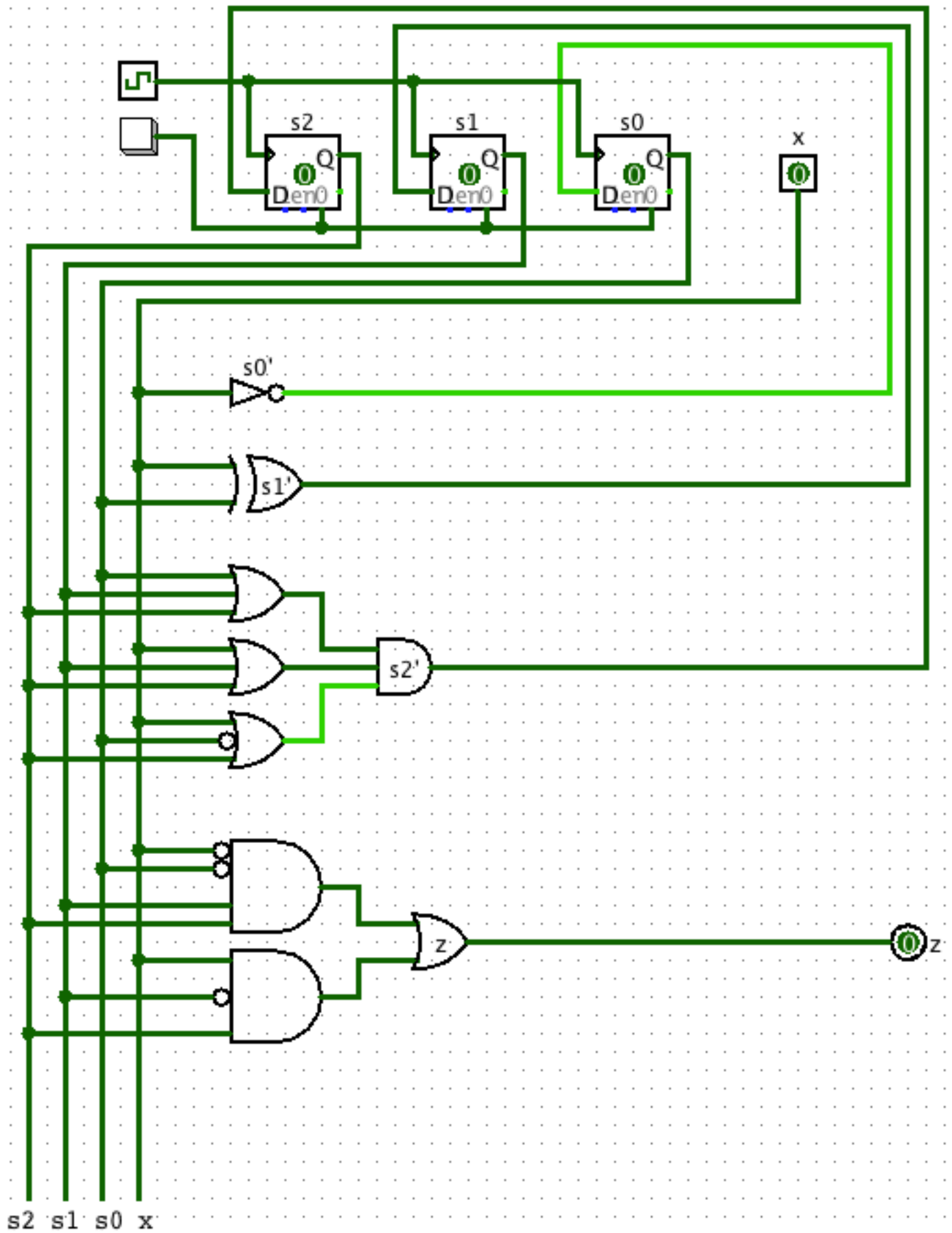Output 1 when EXACTLY two of last three bits are 1




COMBINATIONAL LOGIC CIRCUIT MINIMIZATION



Sequence Detector


	s2	s1	s0	x	s2'	s1'	s0'	z
0	0	0	0	0	0	0	1	0
1	0	0	0	1	0	1	0	0
2	0	0	1	0	0	1	1	0
3	0	0	1	1	1	0	0	0
4	0	1	0	0	1	0	1	0
5	0	1	0	1	1	1	0	0
6	0	1	1	0	0	1	1	0
7	0	1	1	1	1	0	0	0
8	1	0	0	0	1	0	1	0
9	1	0	0	1	1	1	0	1
10	1	0	1	0	0	1	1	0
11	1	0	1	1	1	0	0	1
12	1	1	0	0	1	0	1	1
13	1	1	0	1	1	1	0	0
14	1	1	1	0	d	d	d	d
15	1	1	1	1	d	d	d	d

 

$$s2' = (\overline{s0} + x) (s2 + s1 + s0)$$

Sequence Detector


	s2	s1	s0	x	s2'	s1'	s0'	z
0	0	0	0	0	0	0	1	0
1	0	0	0	1	0	1	0	0
2	0	0	1	0	0	1	1	0
3	0	0	1	1	1	0	0	0
4	0	1	0	0	1	0	1	0
5	0	1	0	1	1	1	0	0
6	0	1	1	0	0	1	1	0
7	0	1	1	1	1	0	0	0
8	1	0	0	0	1	0	1	0
9	1	0	0	1	1	1	0	1
10	1	0	1	0	0	1	1	0
11	1	0	1	1	1	0	0	1
12	1	1	0	0	1	0	1	1
13	1	1	0	1	1	1	0	0
14	1	1	1	0	d	d	d	d
15	1	1	1	1	d	d	d	d

 

$$s1' = \overline{s0} x + s0 \overline{x} = s0 \text{ xor } x$$

Sequence Detector


	s2	s1	s0	x	s2'	s1'	s0'	z
0	0	0	0	0	0	0	1	0
1	0	0	0	1	0	1	0	0
2	0	0	1	0	0	1	1	0
3	0	0	1	1	1	0	0	0
4	0	1	0	0	1	0	1	0
5	0	1	0	1	1	1	0	0
6	0	1	1	0	0	1	1	0
7	0	1	1	1	1	0	0	0
8	1	0	0	0	1	0	1	0
9	1	0	0	1	1	1	0	1
10	1	0	1	0	0	1	1	0
11	1	0	1	1	1	0	0	1
12	1	1	0	0	1	0	1	1
13	1	1	0	1	1	1	0	0
14	1	1	1	0	d	d	d	d
15	1	1	1	1	d	d	d	d

 

$$s0' = \overline{x}$$

Sequence Detector


	s2	s1	s0	x	s2'	s1'	s0'	z
0	0	0	0	0	0	0	1	0
1	0	0	0	1	0	1	0	0
2	0	0	1	0	0	1	1	0
3	0	0	1	1	1	0	0	0
4	0	1	0	0	1	0	1	0
5	0	1	0	1	1	1	0	0
6	0	1	1	0	0	1	1	0
7	0	1	1	1	1	0	0	0
8	1	0	0	0	1	0	1	0
9	1	0	0	1	1	1	0	1
10	1	0	1	0	0	1	1	0
11	1	0	1	1	1	0	0	1
12	1	1	0	0	1	0	1	1
13	1	1	0	1	1	1	0	0
14	1	1	1	0	d	d	d	d
15	1	1	1	1	d	d	d	d

 

$$z = s2 \overline{s1} x + s2 s1 \overline{x}$$

Sequence Dectector (optimized)

 Output 1 when EXACTLY two of last three bits are 1



Circuit Minimization is Hard


- **Unix systems store passwords in encrypted form.**
 - ◇ User types in x , system computes $f(x)$ and looks for $f(x)$ in a file.
- **Suppose we use 64-bit passwords and I want to find the password x , such that $f(x) = y$. Let**
$$g_i(x) = 0 \text{ if } f(x) = y \text{ and the } i\text{th bit of } x \text{ is } 0$$
$$1 \text{ otherwise.}$$
- **If the i th bit of x is 1, then $g_i(x)$ outputs 1 for every x and has a very, very simple circuit.**
- **If you can simplify every circuit quickly, then you can crack passwords quickly.**

STATE REDUCTION




Sequence Detector State Transition Diagram

 - Design a machine that outputs a 1 when exactly two of the last three inputs are 1.



6-State Sequence Detector

 

State Reduction Algorithm

1. Use a 2-dimensional table — an entry for each pair of states.
2. Two states are "distinguished" if:
 - a. States X and Y of a finite state machine M are distinguished if there exists an input r such that the output of M in state X reading input r is different from the output of M in state Y reading input r .
 - b. States X and Y of a finite state machine are distinguished if there exists an input r such that M in state X reading input r goes to state X' , M in state Y reading input r goes to state Y' and we already know that X' and Y' are distinguished states.
3. For each pair (X, Y) , check if X and Y are distinguished using the definition above.
4. At the end of the algorithm, states that are not found to be distinguished are in fact equivalent.

Sequence Detector State Reduction Table

	A	B	C	D	E	F	G
A	X	x	x	x	x	x	x
B	X	X	x		x	x	x
C	X	X	X	x	x	x	x
D	X	X	X	X	x	x	x
E	X	X	X	X	X	x	x
F	X	X	X	X	X	X	x
G	X	X	X	X	X	X	X

State Reduction Algorithm Performance

- As stated, the algorithm takes $O(n^4)$ time for a FSM with n states, because each pass takes $O(n^2)$ time and we make at most $O(n^2)$ passes.
- A more clever implementation takes $O(n^2)$ time.
- The algorithm produces a FSM with the fewest number states possible.
- Performance and correctness can be proven.


STATE ASSIGNMENT



State Assignment Heuristics

- **No known efficient alg. for best state assignment**
- **Some heuristics (rules of thumb):**
 - ◇ **The initial state should be simple to reset — all zeroes or all ones.**
 - ◇ **Minimize the number of state variables that change on each transition.**
 - ◇ **Maximize the number of state variables that don't change on each transition.**
 - ◇ **Exploit symmetries in the state diagram.**
 - ◇ **If there are unused states (when the number of states s is not a power of 2), choose the unused state variable combinations carefully. (Don't just use the first s combination of state variables.)**
 - ◇ **Decompose the set of state variables into bits or fields that have well-defined meaning with respect to the input or output behavior.**
 - ◇ **Consider using more than the minimum number of states to achieve the objectives above.**

6-State Sequence Detector

 

Sequence Detector State Assignment

Present state \ Input	X	
	0	1
$S_2S_1S_0$	$S_2S_1S_0Z$	$S_2S_1S_0Z$
$A': 000$	001/0	010/0
$B': 001$	001/0	011/0
$C': 010$	100/0	101/0
$D': 011$	100/0	101/1
$E': 100$	001/0	011/1
$F': 101$	100/1	101/0

Improved Sequence Detector?

- **Formulas from the 7-state FSM:**

$$s2' = (\overline{s0} + x) (s2 + s1 + s0)$$

$$s1' = \overline{s0} x + s0 \overline{x} = s0 \text{ xor } x$$

$$s0' = \overline{x}$$

$$z = s2 \overline{s1} x + s2 s1 \overline{x}$$

- **Formulas from the 6-state FSM:**

$$s2' = s2 s0 + s1$$

$$s1' = \overline{s2} \overline{s1} x + s2 \overline{s0} x$$

$$s0' = \overline{s2} \overline{s1} \overline{x} + s0 x + s2 \overline{s0} + s1 x$$

$$z = s2 \overline{s0} x + s1 s0 x + s2 s0 \overline{x}$$

Sequence Detector State Assignment

7-state

	s2	s1	s0	x	s2'	s1'	s0'	z
0	0	0	0	0	0	0	1	0
1	0	0	0	1	0	1	0	0
2	0	0	1	0	0	1	1	0
3	0	0	1	1	1	0	0	0
4	0	1	0	0	1	0	1	0
5	0	1	0	1	1	1	0	0
6	0	1	1	0	0	1	1	0
7	0	1	1	1	1	0	0	0
8	1	0	0	0	1	0	1	0
9	1	0	0	1	1	1	0	1
10	1	0	1	0	0	1	1	0
11	1	0	1	1	1	0	0	1
12	1	1	0	0	1	0	1	1
13	1	1	0	1	1	1	0	0
14	1	1	1	0	d	d	d	d
15	1	1	1	1	d	d	d	d

new 6-state

	s2	s1	s0	x	s2'	s1'	s0'	z
0	0	0	0	0	0	0	1	0
1	0	0	0	1	0	1	0	0
2	0	0	1	0	0	0	1	0
3	0	0	1	1	1	0	0	0
4	0	1	0	0	1	0	1	0
5	0	1	0	1	1	1	0	0
6	0	1	1	0	d	d	d	d
7	0	1	1	1	d	d	d	d
8	1	0	0	0	1	0	1	0
9	1	0	0	1	1	1	0	1
10	1	0	1	0	0	0	1	0
11	1	0	1	1	1	0	0	1
12	1	1	0	0	1	0	1	1
13	1	1	0	1	1	1	0	0
14	1	1	1	0	d	d	d	d
15	1	1	1	1	d	d	d	d

A = 000

B = 001

C = 010

D = 011

E = 100

F = 101

G = 110

A = 000

B/D = 001

C = 010

~~**D = 011**~~

E = 100

F = 101

G = 110

Improved Sequence Detector

- **Textbook formulas for the 6-state FSM:**

$$s2' = s2 s0 + s1$$

$$s1' = \overline{s2} \overline{s1} x + s2 \overline{s0} x$$

$$s0' = \overline{s2} \overline{s1} \overline{x} + s0 x + s2 \overline{s0} + s1 x$$

$$z = s2 \overline{s0} x + s1 s0 x + s2 s0 \overline{x}$$

- **New formulas for the 6-state FSM:**

$$s2' = (\overline{s0} + x) (s2 + s1 + s0)$$

$$s1' = \overline{s0} x$$

$$s0' = \overline{x}$$

$$z = s2 \overline{s1} x + s2 s1 \overline{x}$$

CHOICE OF FLIP FLOP



Excitation Tables

- Each table shows the settings that must be applied at the inputs at time t in order to change the outputs at time $t+1$.

*S-R
flip-flop*

Q_t	Q_{t+1}	S	R
0	0	0	0
0	1	1	0
1	0	0	1
1	1	0	0

*D
flip-flop*

Q_t	Q_{t+1}	D
0	0	0
0	1	1
1	0	0
1	1	1

*J-K
flip-flop*

Q_t	Q_{t+1}	J	K
0	0	0	d
0	1	1	d
1	0	d	1
1	1	d	0

*T
flip-flop*

Q_t	Q_{t+1}	T
0	0	0
0	1	1
1	0	1
1	1	0

6-State Sequence Detector

Q	Q'	J	K
0	0	0	<i>d</i>
0	1	1	<i>d</i>
1	0	<i>d</i>	1
1	1	<i>d</i>	0

	s2	s1	s0	x	s2'	s1'	s0'	z	j2	k2	j1	k1	j0	k0
0	0	0	0	0	0	0	1	0	0	<i>d</i>	0	<i>d</i>	1	<i>d</i>
1	0	0	0	1	0	1	0	0	0	<i>d</i>	1	<i>d</i>	0	<i>d</i>
2	0	0	1	0	0	0	1	0	0	<i>d</i>	0	<i>d</i>	<i>d</i>	0
3	0	0	1	1	1	0	0	0	1	<i>d</i>	0	<i>d</i>	<i>d</i>	1
4	0	1	0	0	1	0	1	0	1	<i>d</i>	<i>d</i>	1	1	<i>d</i>
5	0	1	0	1	1	1	0	0	1	<i>d</i>	<i>d</i>	0	0	<i>d</i>
6	0	1	1	0	<i>d</i>	<i>d</i>	<i>d</i>	<i>d</i>	<i>d</i>	<i>d</i>	<i>d</i>	<i>d</i>	<i>d</i>	<i>d</i>
7	0	1	1	1	<i>d</i>	<i>d</i>	<i>d</i>	<i>d</i>	<i>d</i>	<i>d</i>	<i>d</i>	<i>d</i>	<i>d</i>	<i>d</i>
8	1	0	0	0	1	0	1	0	<i>d</i>	0	0	<i>d</i>	1	<i>d</i>
9	1	0	0	1	1	1	0	1	<i>d</i>	0	1	<i>d</i>	0	<i>d</i>
10	1	0	1	0	0	0	1	0	<i>d</i>	1	0	<i>d</i>	<i>d</i>	0
11	1	0	1	1	1	0	0	1	<i>d</i>	0	0	<i>d</i>	<i>d</i>	1
12	1	1	0	0	1	0	1	1	<i>d</i>	0	<i>d</i>	1	1	<i>d</i>
13	1	1	0	1	1	1	0	0	<i>d</i>	0	<i>d</i>	0	0	<i>d</i>
14	1	1	1	0	<i>d</i>	<i>d</i>	<i>d</i>	<i>d</i>	<i>d</i>	<i>d</i>	<i>d</i>	<i>d</i>	<i>d</i>	<i>d</i>
15	1	1	1	1	<i>d</i>	<i>d</i>	<i>d</i>	<i>d</i>	<i>d</i>	<i>d</i>	<i>d</i>	<i>d</i>	<i>d</i>	<i>d</i>

Improved Sequence Detector

- **Formulas for the 6-state FSM with D Flip-flops:**

$$s2' = (\overline{s0} + x) (s2 + s1 + s0)$$

$$s1' = \overline{s0} x$$

$$s0' = \overline{x}$$

- **Formulas for the 6-state FSM with J-K Flip-flops:**


$$J2 = s1 + s0 x \quad K2 = s0 \overline{x}$$

$$J1 = \overline{s0} x \quad K1 = \overline{x}$$

$$J0 = \overline{x} \quad K0 = x$$

Sequence Dectector (J-K flip flops)

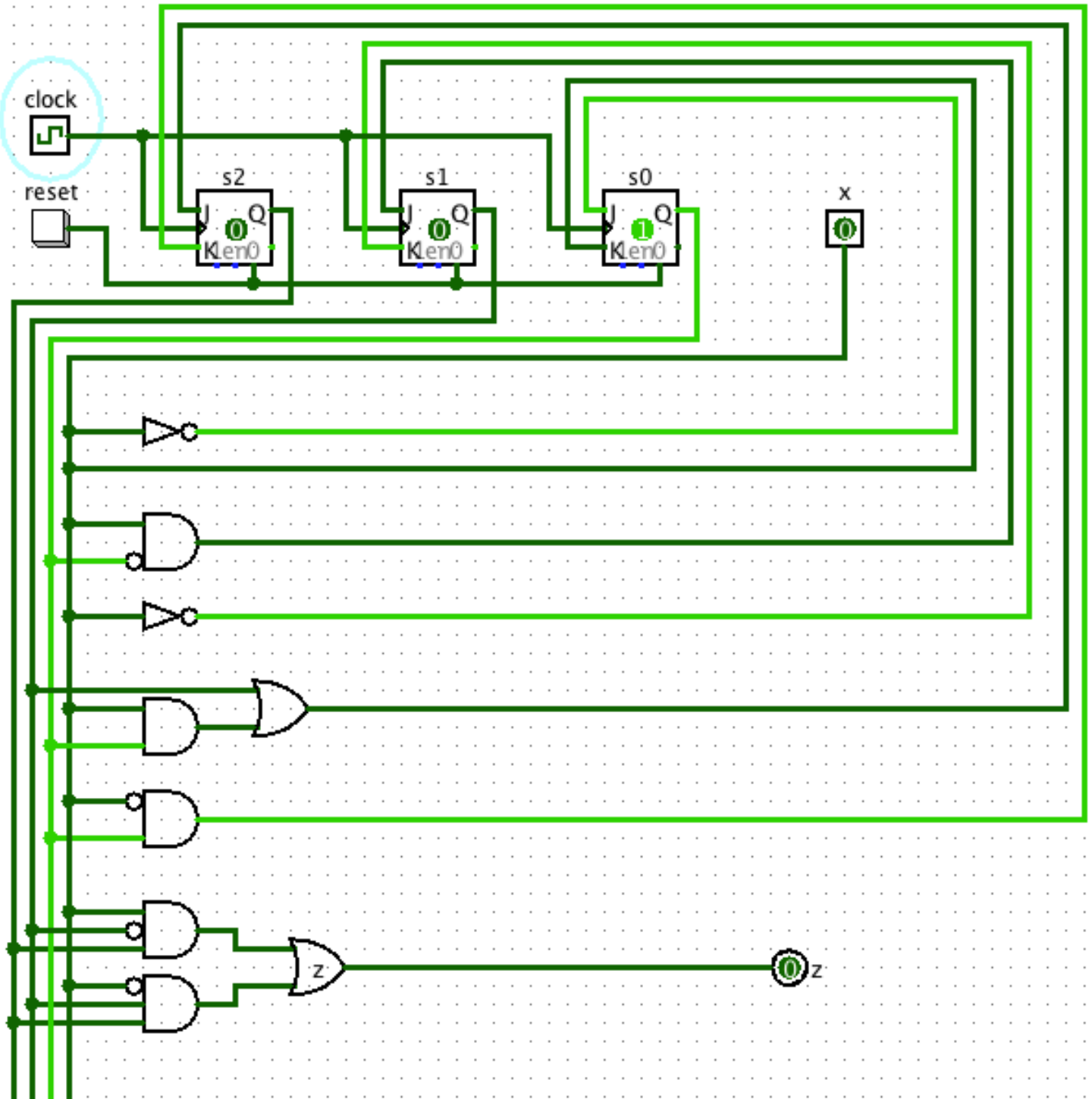Output 1 when EXACTLY two of last three bits are 1




A 2-BIT "CPU"



2-BIT CPU: VERSION 1

 
- **2-bit ALU in sub-circuit**
- **Connect two 2-bit registers to 2-bit ALU**
- **Output of ALU stored in Register 1**



Instructions:
 00 = ADD A
 01 = A AND B
 10 = A OR B
 11 = NOT

**A 2-bit
 Arithmetic Logic Unit
 (ALU)**


2-bit CPU, version 1

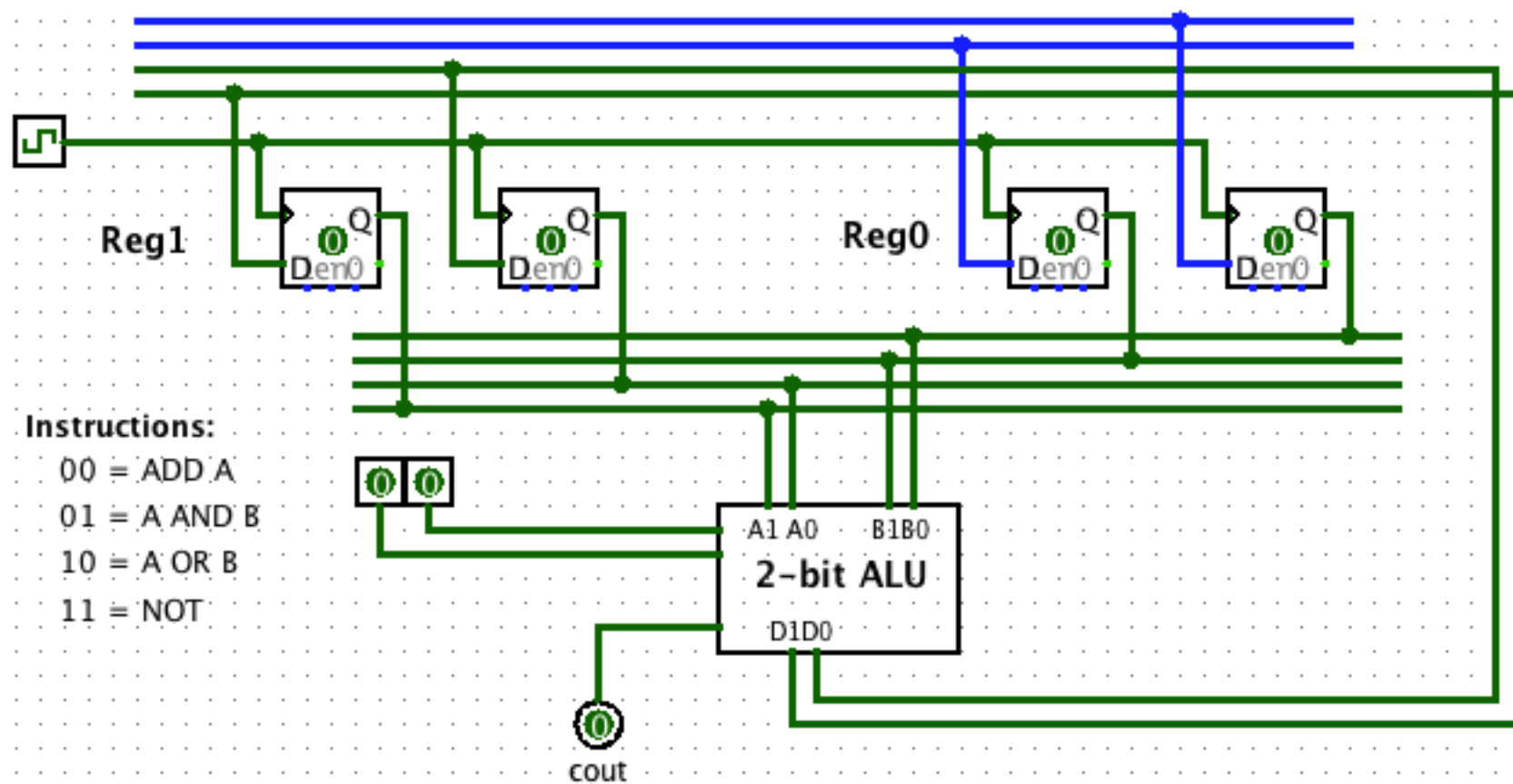

2-BIT CPU: VERSION 2

- **Use DEMUX to select destination register**
- **Use Logisim wire bundles**

2-bit CPU, version 2

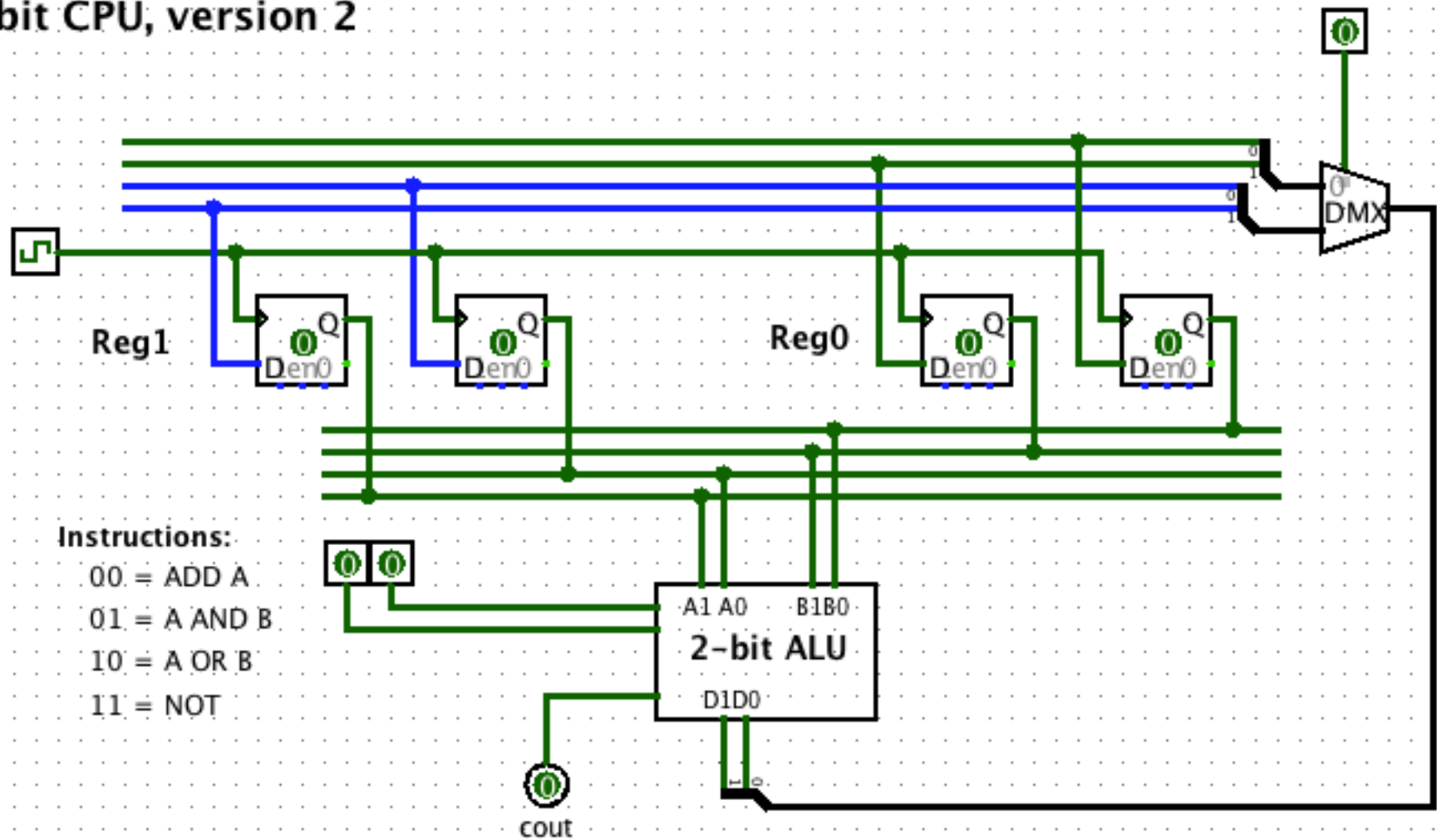


2-BIT CPU: VERSION 3

Use MUX to select input to each ALU "port".




2-bit CPU, version 3

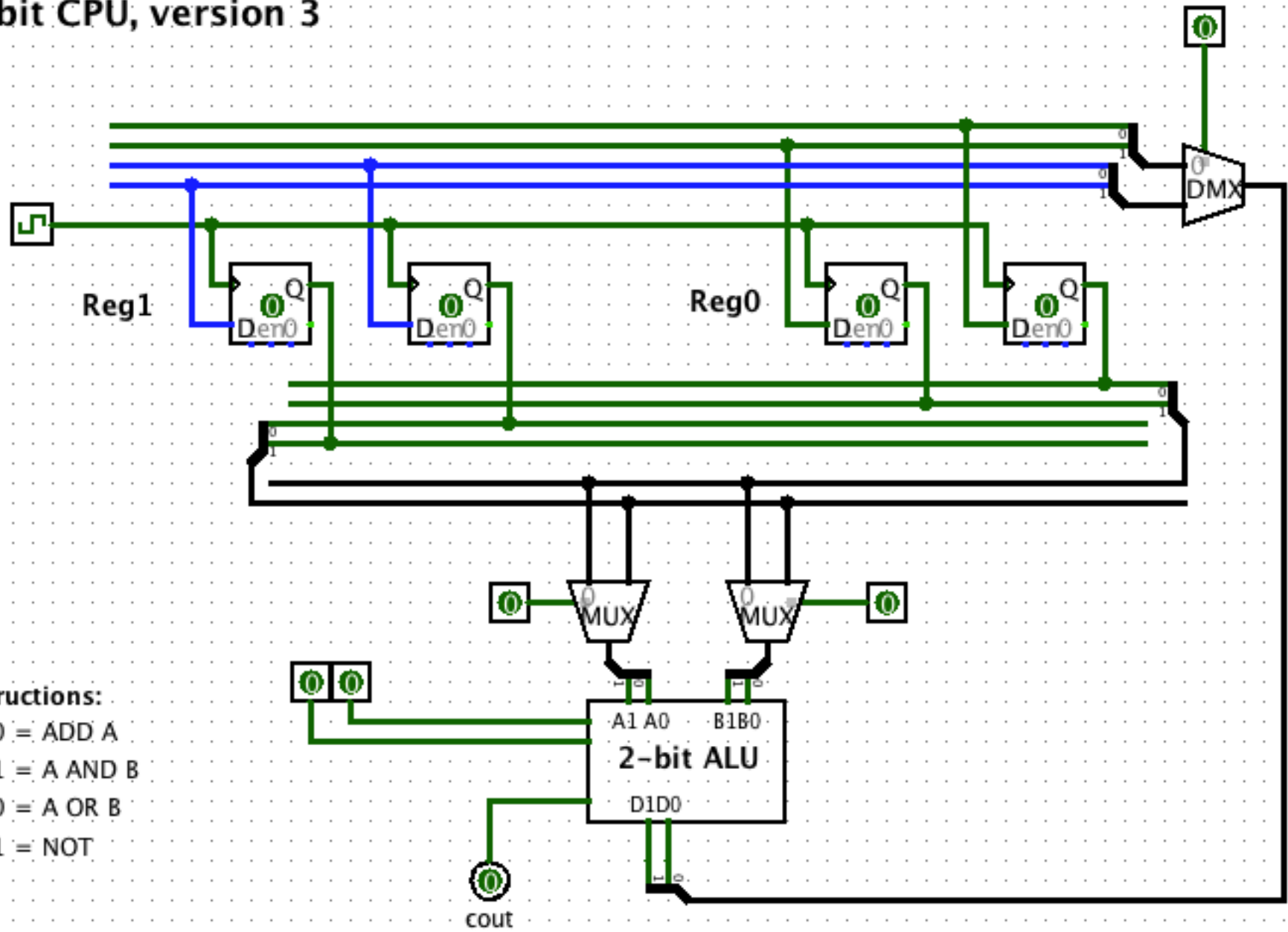

2-BIT CPU: VERSION 4

- Simplify "data bus" using wire bundles
- Add immediate operand to data bus
- Use result MUX to select input to DEMUX for destination register. Input may be:
 - Register 0
 - Register 1
 - Immediate Operand
 - ALU output


2-bit CPU, version 4

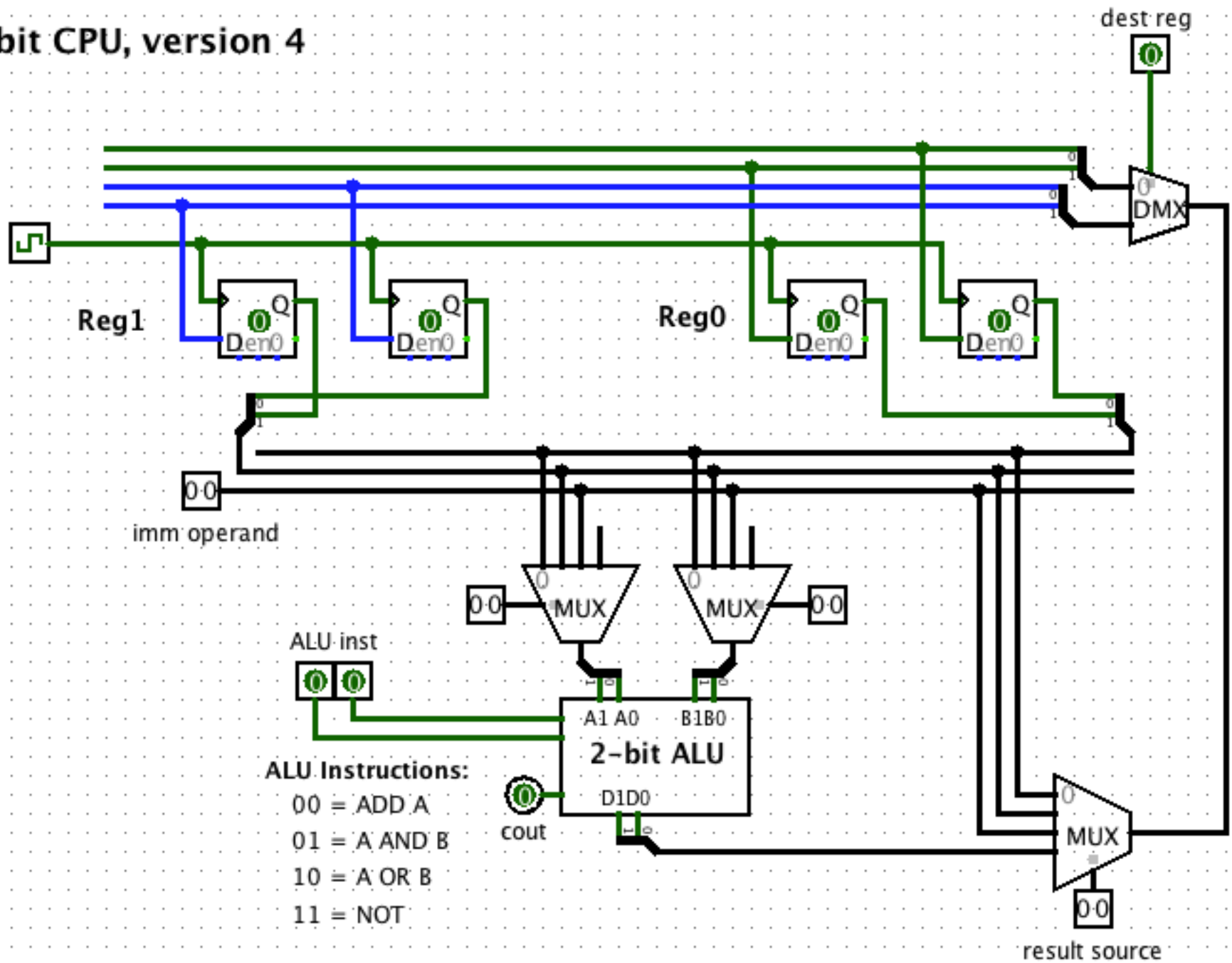

2-BIT CPU: VERSION 5

Consolidate controls to a "control bus"




 

2-bit CPU, version 5


ALU Instructions:

 - 00 = ADD A
- 01 = A AND B
- 10 = A OR B
- 11 = NOT



2-BIT CPU: VERSION 6

Use 8-bit "instruction code"

 

- i7:** 0 if ALU instruction, 1 otherwise
- i6 i5:** ALU instruction
- i4:** operand 1 register (Reg 0 or Reg 1)
- i3 i2 i1:** 0rx = operand 2 is Reg r
1xy = immediate operand xy
- i0:** destination register

2-BIT CPU: VERSION 6

Use 8-bit "instruction code"

i7	i6	i5	i4	i3	i2	i1	i0
1	0	0	0				

- i7:** 0 if ALU instruction, 1 otherwise
- i6 i5 i4:** 000 = move, others not implemented
- i3 i2 i1:** 0rx = source operand is Reg r
1xy = immediate operand xy
- i0:** destination register

INSTRUCTION DECODER

MUX for ALU port B

$$B1 = i3$$

$$B0 = \overline{i3} i2 \overline{i1} + \overline{i3} i2 i1$$
$$= \overline{i3} i2$$

i3	i2	i1	B1	B0	
0	0	0	0	0	} Reg 0
0	0	1	0	0	
0	1	0	0	1	} Reg 1
0	1	1	0	1	
1	0	0	1	0	} Imm
1	0	1	1	0	
1	1	0	1	0	
1	1	1	1	0	


INSTRUCTION DECODER

Result MUX control

$$M1 = \overline{i7} + i3$$

$$M0 = \overline{i7} + \overline{i3} i2$$

i7	i3	i2	i1	M1	M0	
0	0	0	0	1	1	ALU
0	0	0	1	1	1	
0	0	1	0	1	1	
0	0	1	1	1	1	
0	1	0	0	1	1	
0	1	0	1	1	1	
0	1	1	0	1	1	
0	1	1	1	1	1	
1	0	0	0	0	0	Reg0
1	0	0	1	0	0	
1	0	1	0	0	1	Reg1
1	0	1	1	0	1	
1	1	0	0	1	0	Imm
1	1	0	1	1	0	
1	1	1	0	1	0	
1	1	1	1	1	0	

 

00000000

Instr. Decode

2-bit CPU, version 6

ALU Instructions:


- 00 = ADD A
- 01 = A AND B
- 10 = A OR B
- 11 = NOT

00 00 00 00 11 0
 ALU inst ALU.A ALU.B imm Res MUX dest

ALU MUX RES MUX
 00=Reg0 01=Reg1 00=Reg0 01=Reg1
 10=imm 11=xx 10=imm 11=ALU

0-0-0-0-0-0

Instruction Decoder

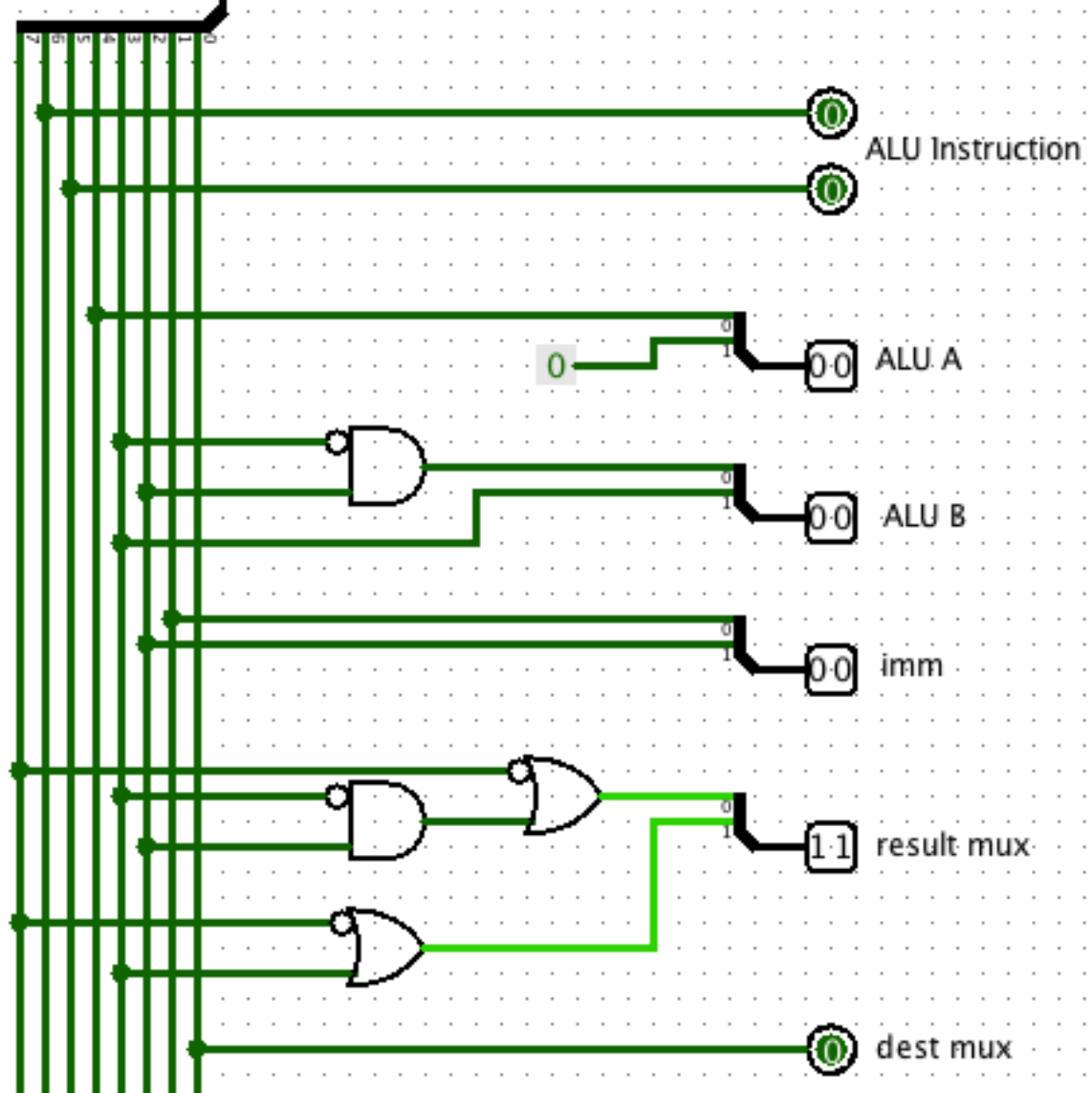

ALU Instruction

ALU A

ALU B

imm


result mux

dest mux

2-BIT CPU: VERSION 7

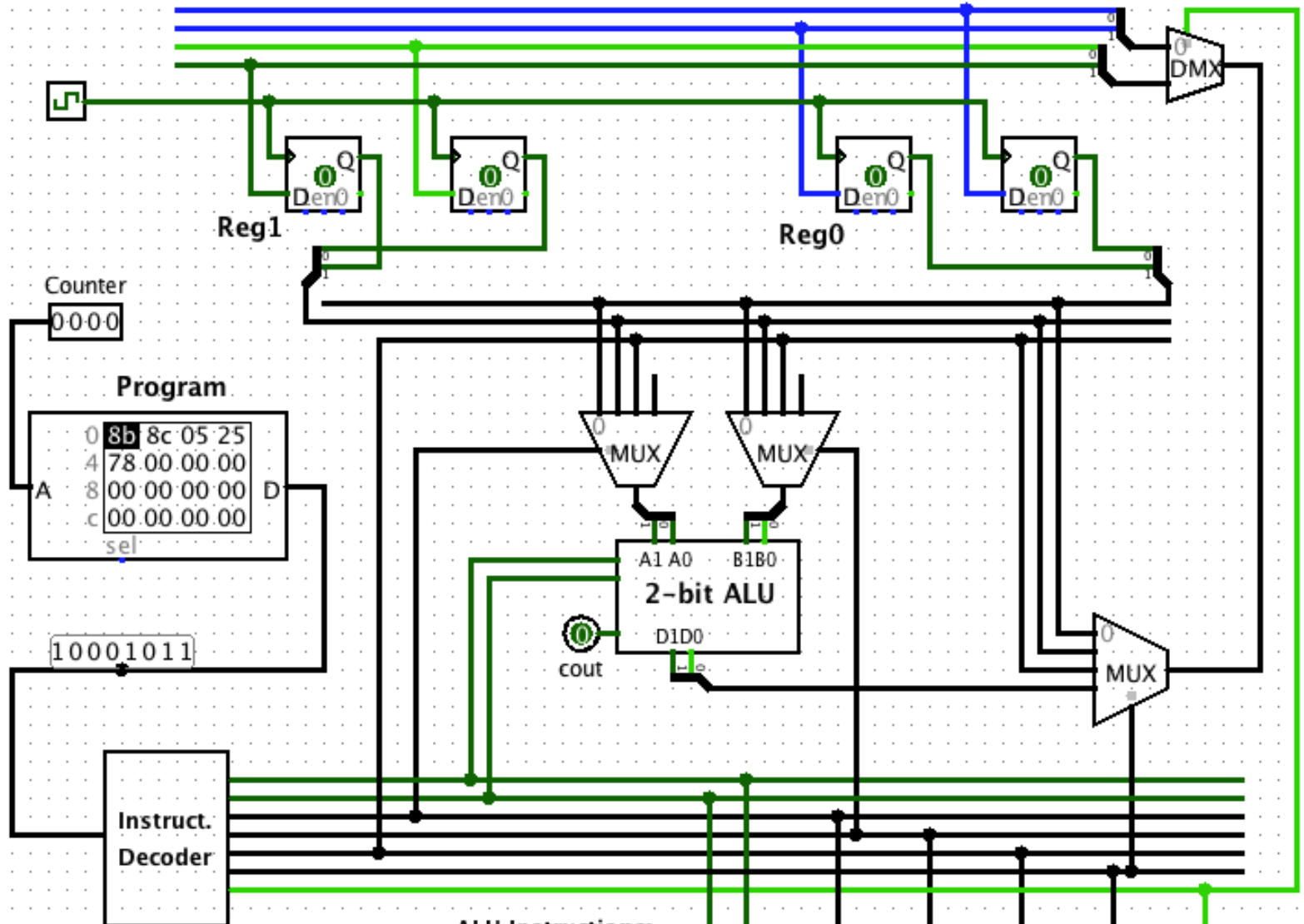Added Program ROM which can store up to 16 instructions.





2-bit CPU, version 7

ALU Instructions:

- 00 = ADD A
- 01 = A AND B
- 10 = A OR B
- 11 = NOT

00 ALU inst 00 ALU A 10 ALU B 01 imm 10 Res MUX 11 dest

ALU MUX

00=Reg0 01=Reg1
 10=imm 11=xx


RES MUX

00=Reg0 01=Reg1
 10=imm 11=ALU

2-BIT CPU: VERSION 8

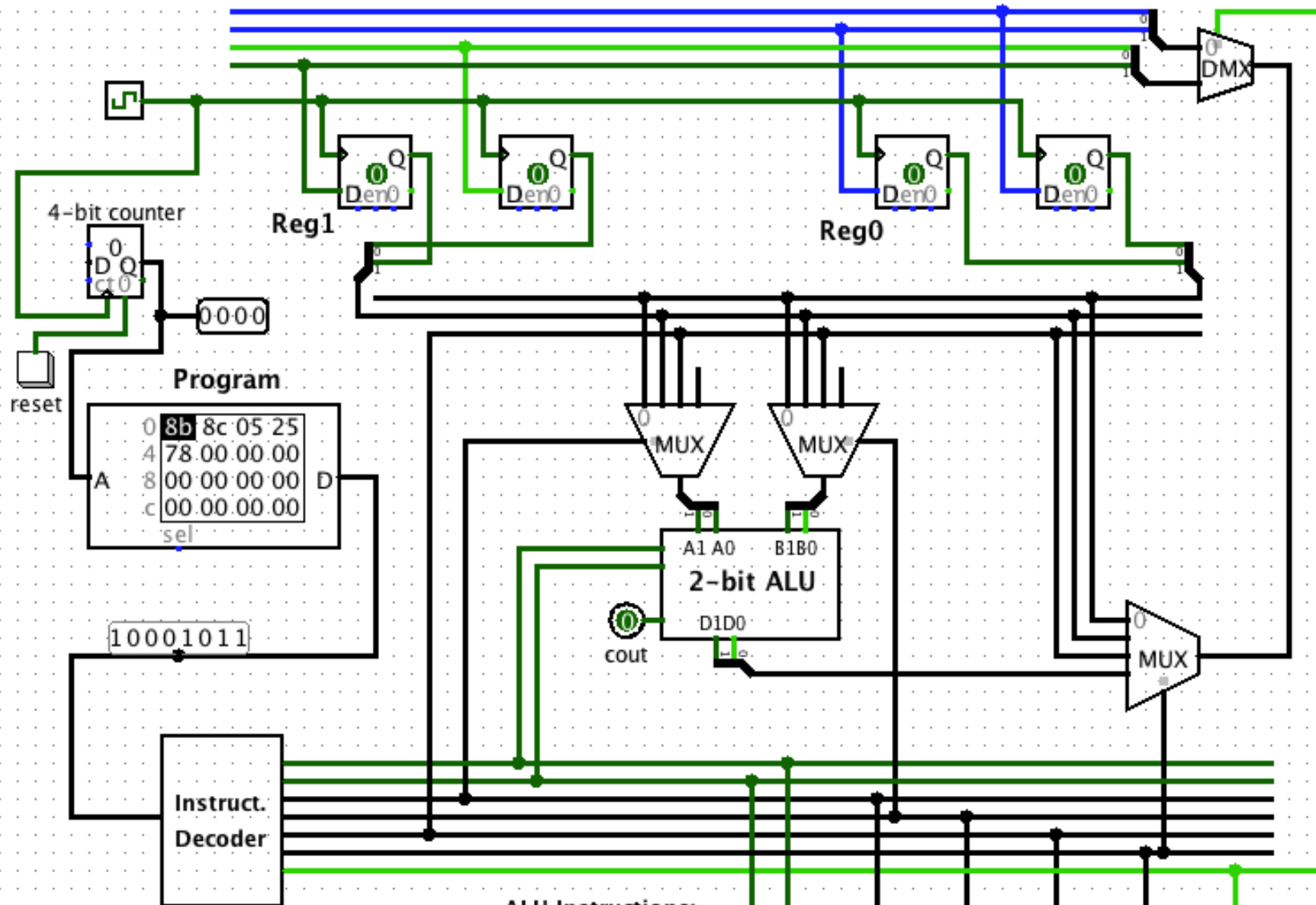Added 4-bit counter which automatically advances Program ROM to next instruction.







2-bit CPU, version 8

ALU Instructions:

  - 00 = ADD A
- 01 = A AND B
- 10 = A OR B
- 11 = NOT




2-BIT CPU: VERSION 9

Implement 4-bit counter from scratch.



4-bit Counter

 


2-BIT CPU: VERSION 10


Implement Program ROM from scratch.



16-bit ROM

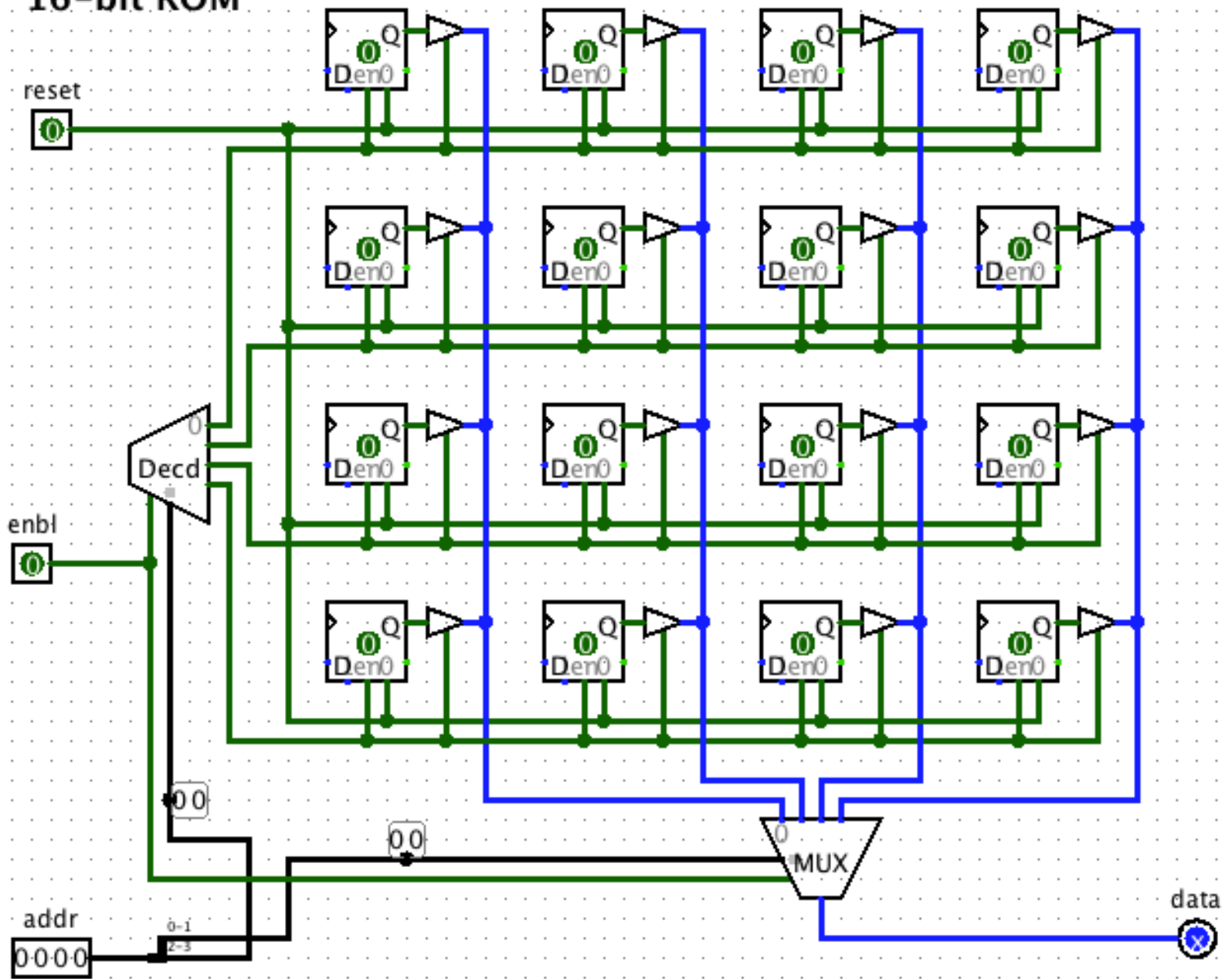

8 x 16-bit ROM

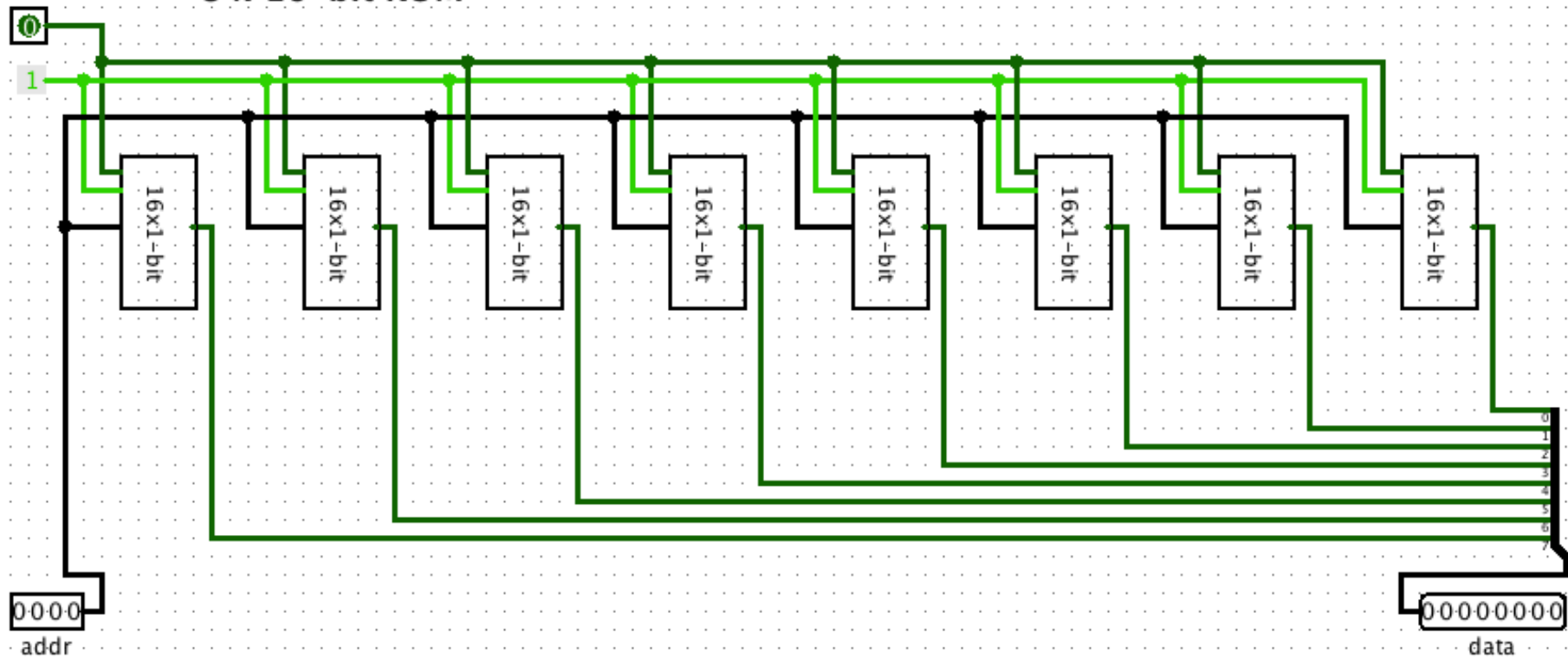

NEXT TIME

- **Memory Hierarchy**
- **Virtual Memory**

