

Lecture 7: Arithmetic Logic Unit

Spring 2024
Jason Tang

Topics


- Logical operations
- 1-bit adder (mostly review)
- Lookahead adder

Rolling and Shifting

- A **roll** (or **rotate**) pushes bits off of one end and reinserts them at the other end



 
- A **left shift** pushes bits towards MSB, inserting zeroes in vacated bit positions



- Two different types of right shift, both pushing towards LSB:
 - **Logical right shift**: vacated bits are set to zero
 - **Arithmetic right shift**: vacated bits are signed extended

Shifting Dangers

 - Left shifting can be used as a cheap way to multiply by a power of 2 (but beware of overflow)
 - Left shifting a two's complement number could result in flipping the sign bit
- Right-shifting **sometimes** results in dividing by a power of two, but only when original value was non-negative, or correct shift operation was used




C and Java Shift Operators

- In both C and Java, << is logical left shift
- In Java. >> is arithmetic right shift, >>> is logical right shift
- In C, usually, >> is arithmetic for signed values and logical for unsigned

```
#include <stdio.h>

 int main(void) {
    signed char a = -42;
    printf("a is %02x, shifted: %02x\n",
        a, (a >> 4));
    unsigned char b = (unsigned char) a;
    printf("b is %02x, shifted: %02x\n",
        b, (b >> 4));
    return 0;
}
```



```
a is ffffffff d6, shifted: ffffffff d
b is d6, shifted: 0d
```

Bitwise Operations

- Even though memory is (somewhat) cheap, one optimization is to **pack** different values into a single word
 - Example: store 8 separate boolean variables in a 8-bit **bitfield**
- Use logical AND, OR, and NOT (or NEGATE) instructions to isolate individual bits
 - AND often used to create a **bitmask**
- Other operators are NAND, NOR, XOR, and NXOR

C Bitwise Operations

- Combination of AND and shift are used to extract individual bits from an integer
- Combination of OR and shift are used to set individual bits in an integer

```
#include <stdio.h>

int main(void) {
    unsigned char a = 0b11000101;
    printf("orig a: %02x\n", a);
    printf("middle 4: %02x\n", ((a >> 2) & 0xf));
    a = (0x03 << 4) | (a & 0x0f);
    printf("new a: %02x\n", a);
    unsigned char b = ~a;
    printf("b: %02x\n", b);
    return 0;
}
```



```
orig a: c5
middle 4: 01
new a: 35
b: ca
```

C Bitfields

- Combination of unions and bitfield structs can be used to manipulate individual bits
 - Almost always involves unsigned **fixed-width** integers
- Is **compiler dependent** as to **packing** and **endianness** order of bitfield
 - Bitfields are convenient if the code will only be compiled with a particular compiler and run on a particular architecture
 - Otherwise use bitwise operations to remain portable

C Bitfield Example

```
#include <stdio.h>
#include <stdint.h>

union u {
    uint8_t val;
    struct {
        unsigned upper: 4;
        unsigned next: 2;
        unsigned flag1: 1;
        unsigned flag2: 1;
    } bits;
};

int main(void) {
    union u a;
    a.val = 0b11000101;
    printf("orig a: %02x\n", a.val);
    printf("upper 4: %02x\n", a.bits.upper);
    a.bits.flag1 = 0;
    printf("new a: %02x\n", a.val);
    return 0;
}
```


On macOS, with
clang 900.0.39.2



```
orig a: c5
upper 4: 05
new a: 85
```

Arithmetic Logic Unit

 - Hardware device that performs simple **integer** operations
- Handles up to two operands
- Has a selector to choose which operation to perform:





- Add or subtract; usually logical operations like rotate, shift, and bitwise
- Sometimes more complex operations like square root
- Typically, set **condition code** (also known as **status**) based upon operation

1-Bit Half Addition

- In simplest case, a **half-adder** (also known as a (2, 2) **adder**) adds two bits together, and calculates a sum and a carry-out

$$\begin{aligned} \text{Sum} &= A \oplus B \\ &= A \cdot \overline{B} + \overline{A} \cdot B \end{aligned} \quad \text{CarryOut} = A \cdot B$$

| Input | | Outputs | |
|-------|---|---------|-----------|
| A | B | Sum | Carry Out |
| 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |

  



1-Bit Full Adder

- A **full-adder** (also known as **(3, 2) adder**) includes a carry-in bit as well

$$Sum = (A \cdot \overline{B} \cdot \overline{C_{in}}) + (\overline{A} \cdot B \cdot \overline{C_{in}}) + (\overline{A} \cdot \overline{B} \cdot C_{in}) + (A \cdot B \cdot C_{in})$$

$$\begin{aligned} C_{out} &= (B \cdot C_{in}) + (A \cdot C_{in}) + (A \cdot B) + (A \cdot B \cdot C_{in}) \\ &= (B \cdot C_{in}) + (A \cdot C_{in}) + (A \cdot B) \end{aligned}$$


| Inputs | | | Outputs | |
|--------|---|----------|---------|-----------|
| A | B | Carry In | Sum | Carry Out |
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 |

 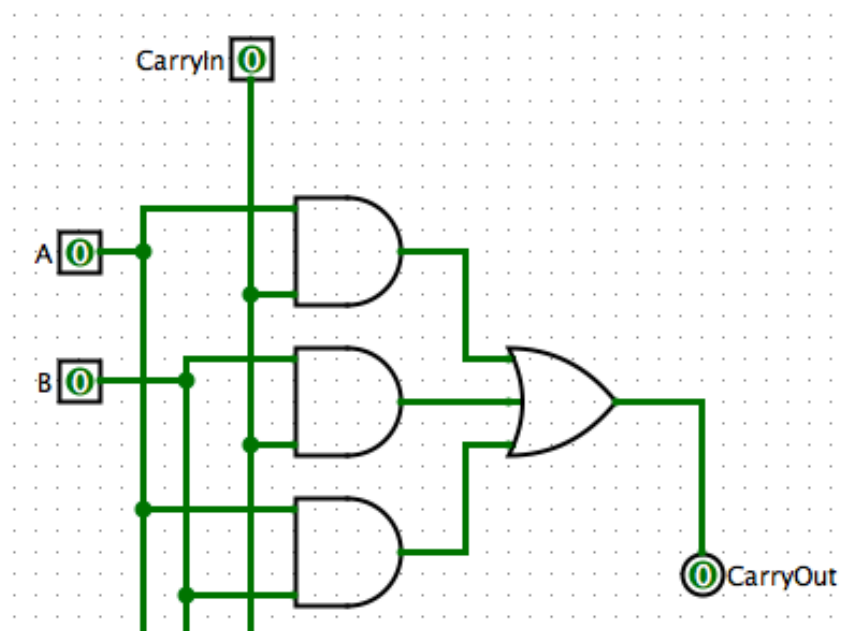

Sum calculation is left as an exercise to the reader

ALU Selector

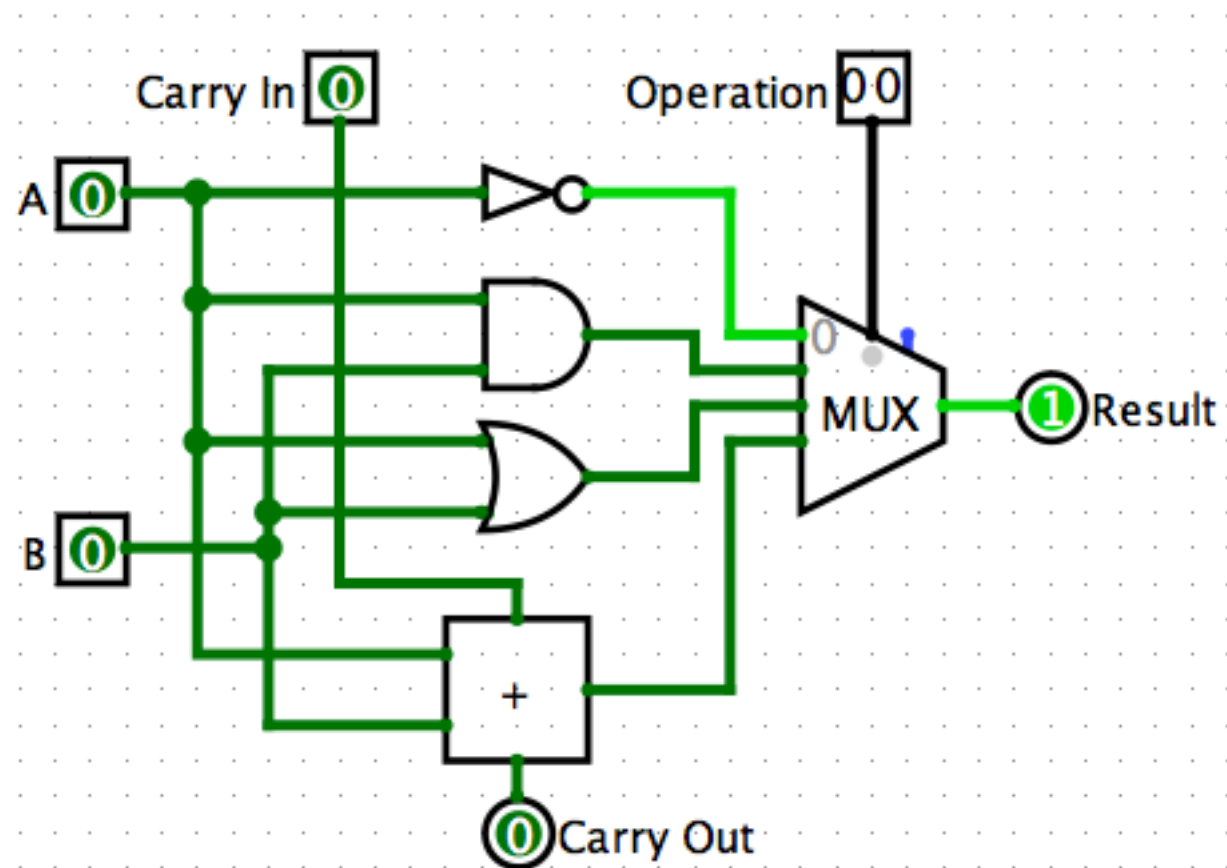
- ALU has a selector to choose which operation to perform
- Example ALU that supports 4 operations:



| Operation | | Usage |
|-----------|---|--------------|
| 0 | 0 | $\neg A$ |
| 0 | 1 | $A \wedge B$ |
| 1 | 0 | $A \vee B$ |
| 1 | 1 | $A + B$ |


Supporting Subtraction

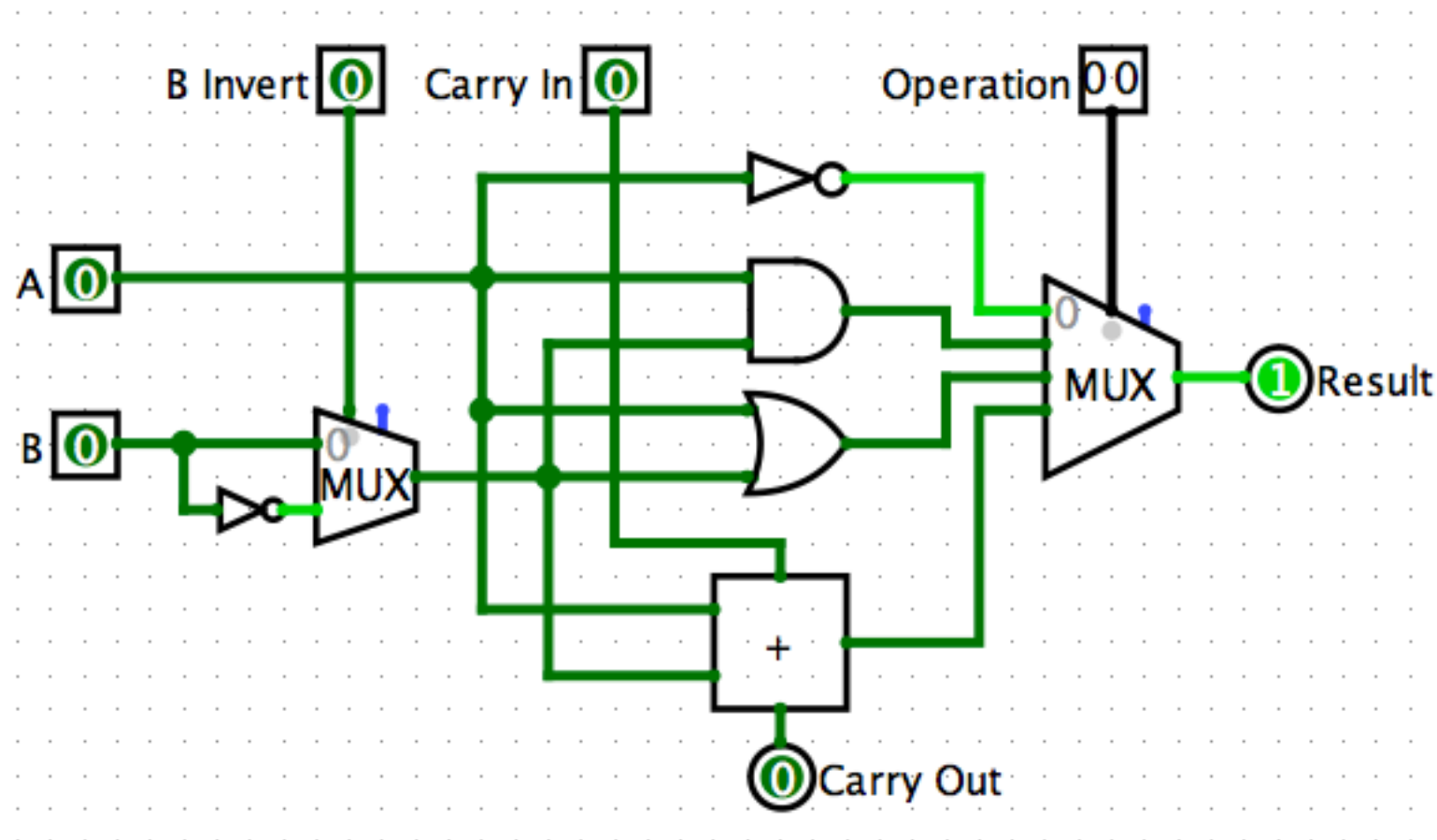- Subtraction means adding the negative, and the negative in two's complement is a bit inversion, plus one: $A - B = A + \overline{B} + 1$
- By adding a selector to **B** operand, the same adder is used for addition and subtraction




Multibit ALU Design

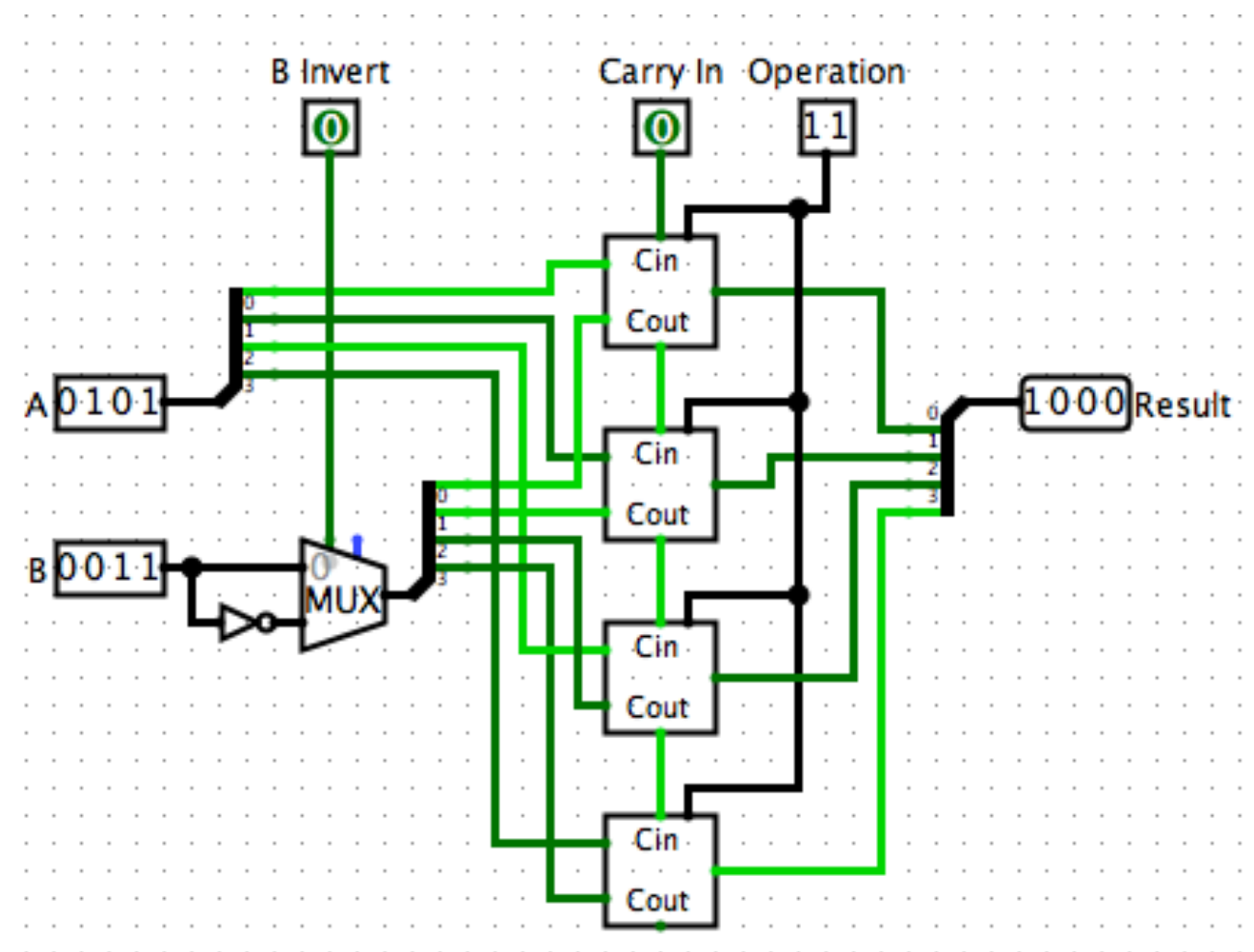- A full ALU (16-bit, 32-bit, etc) can be created by connecting adjacent 1-bit ALUs, using Carry In and Carry Out lines
 - Chain Carry Out from one adder to Carry In of next adder (a **ripple carry adder**)
 - Slow due to gate propagation delay
- Perform subtraction by inverting B and set first Carry In to 1



Alternative Multibit ALU Design

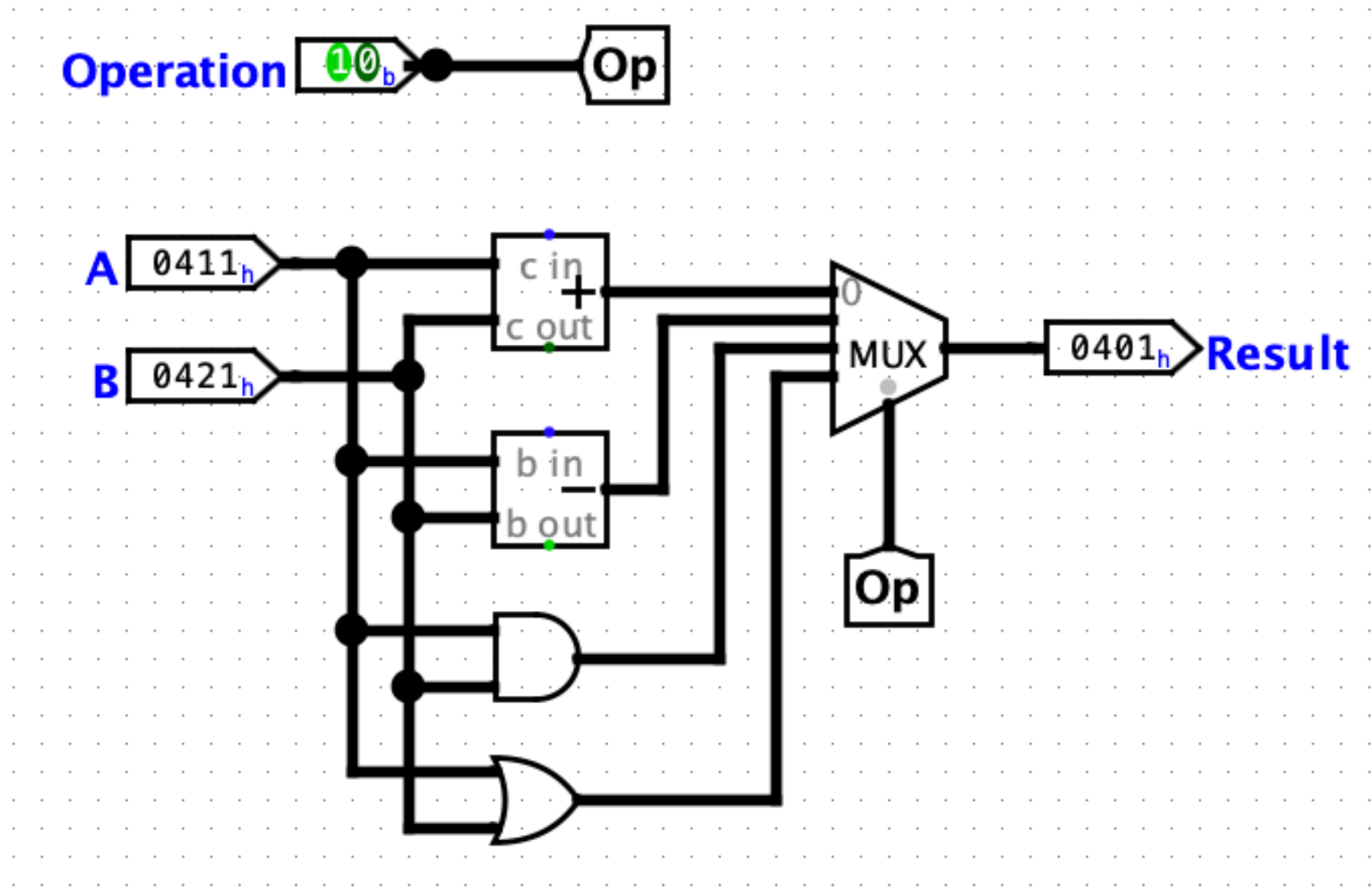


Setting Condition Codes

- Recall that **condition code register** bits are set automatically as a result of some operations

| condition | set by |
|--------------|------------------|
| zero (Z) | result is zero |
| carry (C) | carry out of MSB |
| negative (N) | MSB was 1 |
| overflow (V) | an overflow |

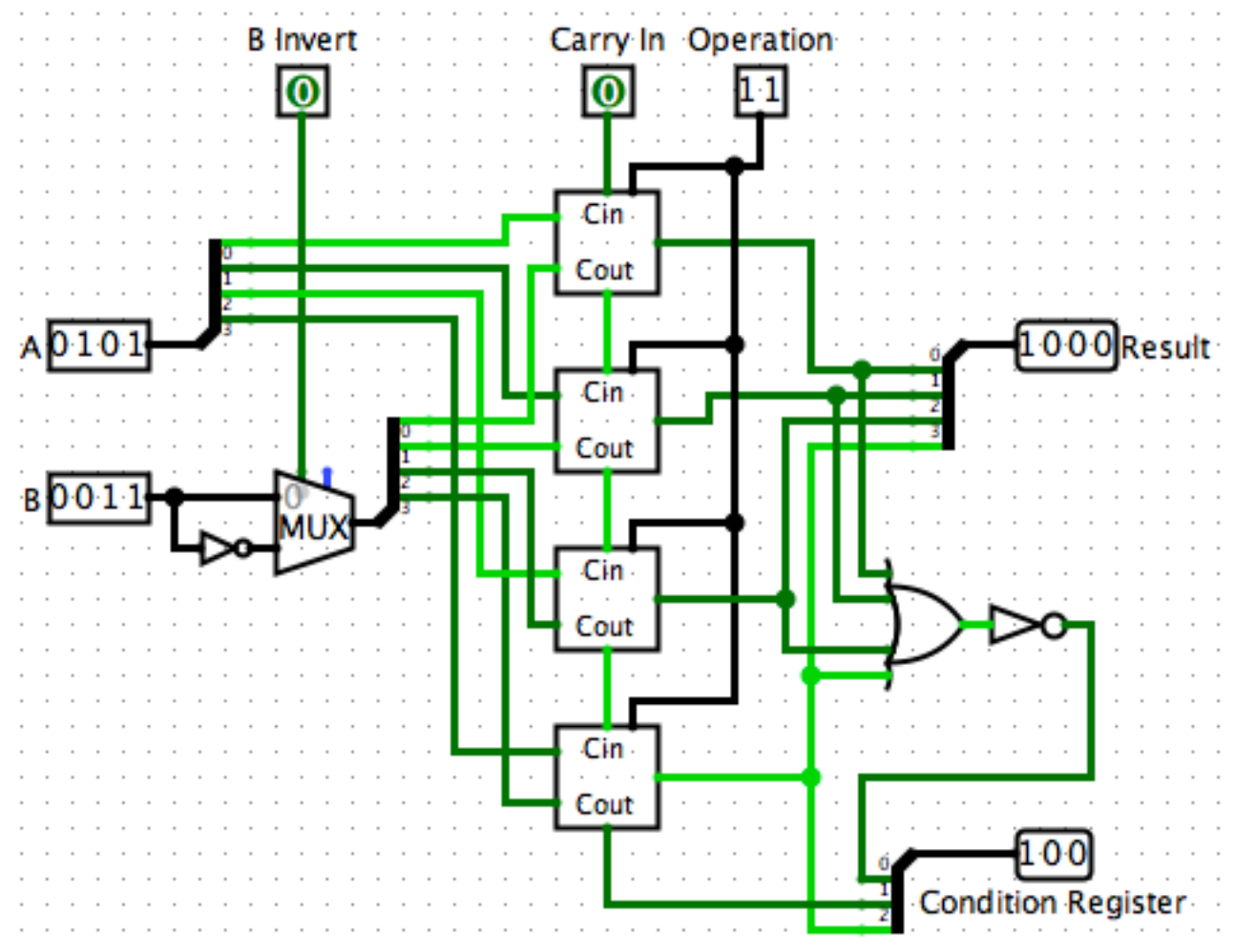- By examining the Carry Out bit of MSB adder and resulting value, ALU sets condition bits



Overflow calculation is left
as an exercise to the reader

Propagation Delays in Ripple ALUs


- Carry In of a 1-bit adder depends upon result of previous 1-bit adder
- Result of adding most significant bits is only available after all bits (i.e., after **n**-1 single bit additions)
 - Too slow in time-critical hardware
- Carry Lookahead ALU anticipates value of Carry Out
 - Takes many more gates to anticipate carry
 - Worst case scenario is $\log_2(\mathbf{n})$, where **n** is number bits in the adder

Carry Lookahead Theory

- Let the **generate function** $G(A, B)$ be 1 if A plus B will generate a Carry Out
 - In binary arithmetic, $G(A, B) = A \cdot B$, regardless of Carry In (C_{in})
- Let the **propagate function** $P(A, B)$ be 1 if A plus B will generate a Carry Out, but only when C_{in} is 1
 - $P(A, B) = A + B$; or $P(A, B) = A \oplus B$ because of $G(A, B)$ will be 1
- Then the Carry Out for bit i is $C_i = G_i + (P_i \cdot C_{i-1})$
- For a **carry lookahead group** with size 2, $C_i = G_i + (P_i \cdot (G_{i-1} + (P_{i-1} \cdot C_{i-2})))$
 - By the Distributive Law, $C_i = G_i + (P_i \cdot G_{i-1}) + (P_i \cdot P_{i-1} \cdot C_{i-2})$


Using Carry Lookahead Groups

 - For a carry lookahead group size 4, $C_4 = G_3 + (P_3 \cdot G_2) + (P_3 \cdot P_2 \cdot G_1) + (P_3 \cdot P_2 \cdot P_1 \cdot G_0) + (P_3 \cdot P_2 \cdot P_1 \cdot P_0 \cdot C_{in})$
- Therefore, all Carry Outs for the group can be calculated in parallel:



Cascading Carry Lookahead

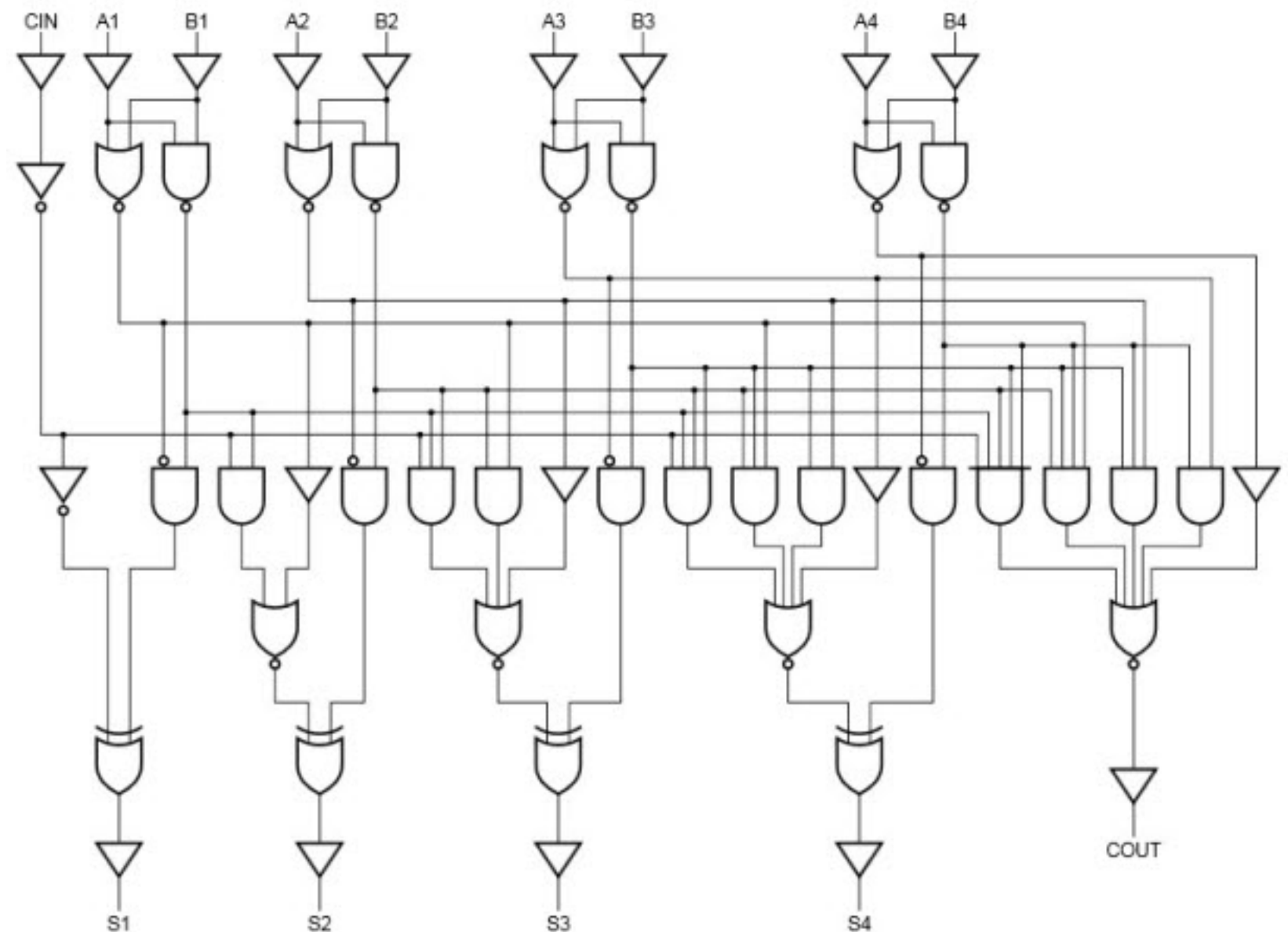- For this circuit, S2 and S4 have equal gate delays
- Carry Out of one group is propagated to next carry lookahead group
- 16-bit adder can be implemented as 4 groups of 4-bit adders
- Can create **supergroups** of carry lookahead groups



Speed of Carry Generation

- For *this* 1-bit adder, the gate delays are 2 for the Carry Out and 3 for the Sum
- If this 1-bit adder were chained together into a 16-bit ripple adder, the gate delays are $(16 \times 2) = 32$ for the last Carry Out, $(15 \times 2 + 3) = 33$ for last Sum bit
- If instead the adder had 4 sets of 4-bit groups, the delays are $(4 \times 2) = 8$ for last Carry Out, $(3 \times 2 + 3) = 9$ for last sum bit
 - Larger groups would be faster, but use more gates

