


Lecture 16: Pipeline Controls

Spring 2024
Jason Tang

Topics


- Designing pipelined datapath
- Controlling pipeline operations

Instruction Pipelining

 


- Goal is to start executing next instruction on every clock cycle
- Pipelining only works when there are no resource contentions
 - If so, then either intentionally stall pipeline or duplicate those resources


Multicycle Datapath

 


Pipelined Datapath

 


Pipeline Registers

 

Pipeline Controls

 


Controls and Datapath

 

Pipeline Control Generation


- In single and multicycle datapaths, a single instruction decoder takes instruction register contents to generate control signals
- In pipelined datapaths, either:
 - Single instruction decoder decodes upfront, then writes controls into **data stationary registers** to be used on subsequent cycles, or
 - Instruction register value itself is copied into data stationary registers, and then a local decoder generates signals for that portion of the datapath

Pipelining Instructions

 


- Pipeline conflict (specifically, a structural hazard) when two instructions try to write to register file on same clock cycle
 - Register file can only store one new value at a time
 - Caused by uneven pipeline stages

Solution 1: Insert Bubble into Pipeline

 


- Insert bubble into pipeline to prevent simultaneous writes
 - Control logic can be complex
 - No instruction started on Cycle 7

Solution 2: Delay Write by One Cycle

 


- Delay R-Type's write by one cycle
 - R-Type MEM Ctrl is a no-op; it generates no controls
- Now pipeline has same length for all instruction types

Pipelined Operations

 

- IM = Instruction Memory, Reg = Register File, DM = Data Memory
- Shaded on right side = read, Shaded on left = write

Pipeline Controls

 


- PC is updated every cycle, so no need for a control signal to control writing to PC
- Pipeline registers (green boxes) are also updated every cycle

Setting Pipeline Controls

Instruction	EX Ctrls			MEM Ctrls		WB Ctrls	
	ALUSrcA	ALUSrcB	ALUOp	MemRead	MemWrite	MemToReg	RegWrite
add	A	B	add	0	0	Out	1
sub	A	B	sub	0	0	Out	1
ldur	A	Ext (imm9)	add	1	0	M	1
stur	A	Ext (imm9)	add	0	1	X	0


- Instruction decoder calculates control signal values given instruction register
 - Writes those values to pipeline registers, to be used by later cycles

Example of Pipeline: Cycle 0

 


- Initial state (Cycle 0): PC = 00

Example of Pipeline: After Cycle 1

 


- Fetch from 00h, then increment PC

Example of Pipeline: After Cycle 2

 


- Fetch from 04h; decode **ldur x10, [x10, #40]** and generate controls

Example of Pipeline: After Cycle 3

 


- Fetch from 08h; decode **sub x11, x2, x3**; execute **ldur**

Example of Pipeline: After Cycle 4

 


- Fetch 0Ah; decode **add x12, x3, x4**; execute **sub**; mem access **ldur**

Example of Pipeline: After Cycle 5

 


- Fetch 10h; decode **stur** X13, [X1, #48]; execute **add**; mem access **sub** (noop); write **ldur**

Example of Pipeline: After Cycle 6

 


- Decode **add** X14, X5, X6; execute **stur**; mem access **add** (noop); write **sub**

Example of Pipeline: After Cycle 7

 


- Execute **add**; mem access **stur**; write **add**

Example of Pipeline: After Cycle 8

 

- Mem access **add** (noop); write **stur** (noop)

Example of Pipeline: After Cycle 9

 

- Write **add**