 


VERILOG I

Verilog

- Hardware Description Language
- Design process
 - Think
 - Draw diagram of hardware, figure out where logic and registers go, choose signal names carefully
 - Think
 - Then...
 - Write verilog
 - Test it



Verilog

- You'll write far better verilog if you think of it differently than a standard programming language
 - A way to code an *algorithm*
 - Often more elegant to use the finer features of the language
- Hardware description language
 - A way to code *hardware!*
 - It is far better to use only the most basic structures of the language
 - Synthesis tools will have fewer opportunities to interpret (alter) what you really want
 - Less-used CAD tools (such as place & route, design rule checking (DRC), layout versus schematic (LVS), formal verification, automatic test pattern generation (ATPG), etc.) often do not work properly with uncommon language constructs

B. Baas, © 2011

EEC 281

3

Writing Efficient Code

- Think about what kind of hardware will result from some particular code even if the code looks simple

```
if (x<y) begin
    a = 4'b0001;
end
```
- An inequality requires a slow carry-propagate subtractor. It is simplified since the *sum* bits do not need to be computed, but the slow *carry-out* of the entire adder is needed

B. Baas, © 2011

EEC 281

4

Verilog Simulator Tools

- Cadence
 - NC Verilog –what we will use
 - Simvision – waveform viewer
 - Verilog XL – slower, but faster start up time as it doesn't compile before running
 - Often gives different (helpful!) and slightly more descriptive (helpful!) error messages than NC Verilog
- Synopsys
 - VCS – similar to NC Verilog
 - Virsim – waveform viewer and environment
- Many others...


Verilog vs. VHDL

- Verilog
 - Invented in 1983 at Automated Integrated Design Systems (later Gateway Design Automation) which was purchased by Cadence in 1990. It was transferred into the public domain in 1990 and it became IEEE Std. 1364-1995, or *Verilog-95*.
 - Later versions include *Verilog-2001* and *Verilog-2005*.
 - Strong similarities to C
 - Seems to be more commonly used in high-tech companies
- VHDL (VHSIC Hardware Description Language)
 - Published in 1987 with Dept. of Defense support as IEEE Std. 1076-1987. Updated in 1993 as IEEE Std. 1076-1993, which is still the most widely-used version.
 - Later versions in 2000, 2002, and 2008.
 - Strong similarities to Ada
 - The only(?) HDL language used in government and defense organizations, and seems to be more often used in east-coast companies. Widely taught in universities ↔ used in textbooks—who started it?!

Verilog

- Modules are basic building blocks
 
```
module abc (in1, in2, out);
    input in1;
    input in2;
    output out;
    <body of module>
endmodule
```




- “Hardware” blocks vs. “Testing” blocks
 - Hardware verilog: only simplest, cleanest code
 - Testing verilog: anything is fine
- Main ways to do logic
 - 1) wires, assign statements
 - 2) registers, always blocks

wire, assign

- Picture “always active” hardwired logic
- For now, declare all wires


```
wire a, b;
wire out;
```

 

wire, assign

- Example:


```
wire out;  
assign out = a & b;
```

 

wire, assign

 - Example, multibit operands:

```
wire [3:0] c, d;  
wire [4:0] sum; // sum one bit wider  
assign sum = {c[3],c} + {d[3],d};
```



reg, always

- Picture a much more general way of assigning “wires” or “nodes”
- Use “if/else” and “case” statements
- Can, but don’t use “for” in logic blocks (testing blocks ok)
- Sequential execution – statements execute in order

B. Baas, © 2011


EEC 281

11

reg, always

 - Example:

```
reg out;  
always @ (a or b) begin  
    out = a & b;  
end
```



B. Baas, © 2011


EEC 281

12

reg, always

 - Example, 2-input multiplexer:

```
reg out;  
always @(a or b or s) begin  
    out = s ? b : a;  
end
```



B. Baas, © 2011

EEC 281

13

reg, case

- Example using case:

```
reg out;  
wire [1:0] in;          // "in" could be wire or reg  
  
always @(in or a) begin  
    case (in)  
        2'b00: begin  
            out = s;  
        end  
        2'b11: begin  
            out = a;  
        end  
        default: begin  
            out = 1'b0; // zero  
        end  
    endcase  
end      // end of always block
```

B. Baas, © 2011


EEC 281

14

Instantiating Flip-Flops/Registers

- How to build a FF/register (not the best one)

 
```
reg a;  
always @ (posedge clk) begin  
    a = a_c;  
end
```



- The “=” is a “blocking assignment” which causes the simulator to “block” on an assignment until the operation is completed

- It causes a possible race condition
 
```
reg b, c;  
always @ (posedge clk) begin  
    b = a;  
    c = b;  
end
```



- In this case, *a* races to *c* in one cycle!

B. Baas, © 2011


EEC 281

15

Instantiating Flip-Flops/Registers

- The solution is to use a “non-blocking assignment” written with a “<=” which causes the simulator to schedule all assignments at a particular point in time and perform them all simultaneously
- In this case, the registers perform as normal FFs behave without a race
 
```
reg b, c;  
always @ (posedge clk) begin  
    b <= a;  
    c <= b;  
end
```



B. Baas, © 2011

EEC 281

16

Verilog Register Assignments

- Rule #1 (always follow in 281):
For combinational logic blocks, use blocking assignments (“=”)

```
// OR gate
always @ (a or b) begin
    c = a | b;
end
```

B. Baas, © 2011

EEC 281

17


Verilog Register Assignments

- Rule #2 (always follow in 281):
For flip-flops (registers), use non-blocking assignments (“<=”)

```
always @ (posedge clk) begin
    sum     <= #1 c_sum;
    r_product <= #1 product;
end
```

- Add “#1” to give one unit of clock-to-Q delay to increase waveform readability

 - This does, however, produce a warning during synthesis, but it can be ignored (the only warning that can be automatically ignored!)




B. Baas, © 2011

EEC 281

18

Register Naming Conventions

 - It is helpful to have conventions for signal names
 - Easier for others to understand your code
 - Easier for YOU to understand your code
- *_c – input to a register (e.g., sum_c)
- *_r – output of a register (e.g., sum_r)
- Make it a suffix of signal names




B. Baas, © 2011

EEC 281

19

Register Naming Conventions

 - Another possibility I have seen used in industry is to make it a prefix
- c_* – input to a register (e.g., c_sum)
- r_* – output of a register (e.g., r_sum)



B. Baas, © 2011

EEC 281

20

Avoid Inferring State For Combinational Circuits

1. Assign (specify) all regs in **all** paths through every **always** block
2. Include **all input** variables in sensitivity list!
3. Use default values immediately after entering **always** block
 - Greatly reduce chance of bugs if you do this
 - Setting output to `x` in the default of a case statement can help debugging, but may also cause warnings with some CAD tools

B. Baas, © 2011


EEC 281

21

Avoid Inferring State For Combinational Circuits

- Common mistake:

 - `always @(a) begin`
 `out = a & b;`
`end`
 - `out` updates only when `a` changes!
 - Synthesis tools and lint checkers will give a warning



B. Baas, © 2011

EEC 281

22


Good Style With *regs* and *case* statements

- Example combinational circuit with output `c_freq`
 - Always declare default values at beginning of always block
 - If helpful, declare default values in case statements

```
always @(freq or xyz or abc) begin
    //defaults
    c_freq = freq;    // hold previous value in this case

    if (xyz==4'b0010) begin
        c_freq = abc;
    end

     case (freq) begin
        3'b000: c_freq = abc;
        3'b001: c_freq = abc+3'b001;
        default: c_freq = 3'bxxxx;    // error case
    endcase
end
```



B. Baas, © 2011

EEC 281

23