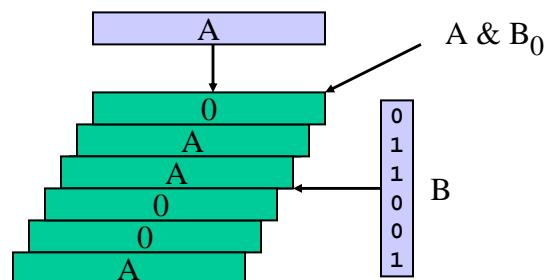


FIXED-INPUT MULTS


Fixed-input Multiplier

- Sometimes, one input is fixed
 - So remove partial products that are always zero



Fixed-input Multiplier

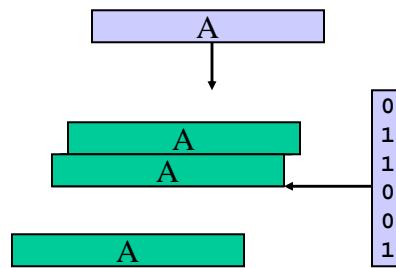- Remove partial products that are always zero




B. Baas, © 2009

EEC 281, Winter 2009

109

Fixed-input Multiplier

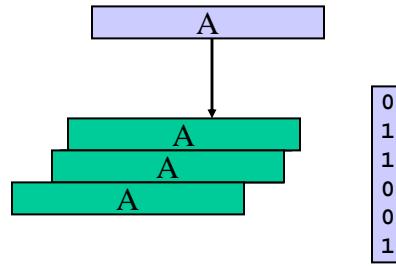- Reduce size by half on average, often more if you can pick the “multiplier” carefully



B. Baas, © 2009

EEC 281, Winter 2009

110

Fixed-input Multiplier

- The goal is to find the minimum number of power-of-2 numbers to add together to equal the fixed multiplier input
- Ex: multiply by 3
 $x3 = (x2) + (x1)$

B. Baas, © 2009

EEC 281, Winter 2009

111

Multiply by 3

- Ex: multiply by 3
 - $x3 = (x2) + (x1)$
 - Verilog:

| | | |
|---|----|---|
| S | in | |
| S | in | 0 |

```
input [7:0] in;
wire [9:0] product;
// multiply by 3
assign product = {in[7], in, 1'b0}
           + {in[7], in[7], in};
```

B. Baas, © 2009


EEC 281, Winter 2009

112

Multiply by 56

- Ex: multiply by 56

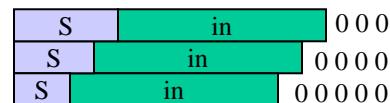- $x56 = (x32) + (x16) + (x8)$
- Verilog:



```
input [7:0] in;
wire [13:0] product;
// multiply by 56
assign product =
    {in[7], in, 5'b00000}
    + {in[7], in[7], in, 4'b0000}
    + {in[7], in[7], in[7], in, 3'b000};
```

B. Baas, © 2009


EEC 281, Winter 2009

113

Multiply by 56 (better)

- Ex: multiply by 56 (better)

- $x56 = (x64) - (x8)$
- Verilog:

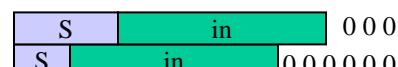

```
input [7:0] in;
wire [13:0] product;
// multiply by 56
assign product =
    {in, 6'b000000}
    - {in[7], in[7], in[7], in, 3'b000};

assign product_same =
    {in, 6'b000001}
    + {-in[7], ~in[7], ~in[7], ~in, 3'b111}; // one way of many
```


B. Baas, © 2009

EEC 281, Winter 2009


114

Dot Diagram Example

- $\text{out} = X*3 + Y*56$
 - Inputs: 6-bit 2's complement
- Procedure
 - Input range: $[-32, +31]$
 - Decompose $\times 3 = \times 2 + \times 1$
 - Decompose $\times 56 = \times 64 - \times 8$
 - Output range: $[-32, +31] \times [59] = [-1888, +1829]$
 - Output width: 12 bits
 - Fill out dot diagram
 - S = sign extension bit
 - invert bits when necessary
 - show zeros if dot alignment is not obvious
- Two approaches of thinking of negative partial products (with identical product of course)
 - 1) Shift PP then invert entire word
 - 2) Invert PP then shift

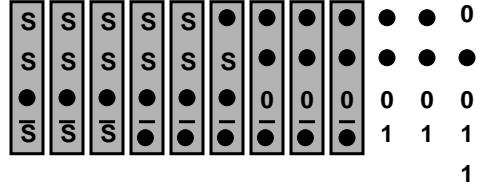

- OR -

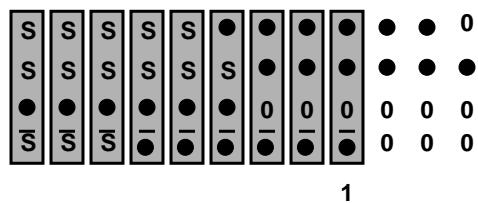

1