

SATURATION

Saturation (or Clipping)

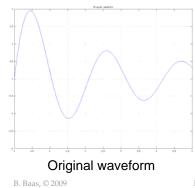- Eliminates MSB bits
- Common to saturate a signal after an operation which will or *may* cause the magnitude of a signal to increase



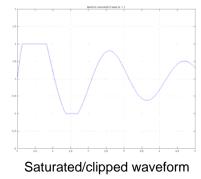

EEC 281, Winter 2009


141

Saturation (or Clipping)

 Matlab code that produced previous example waveforms

Saturation (or Clipping)

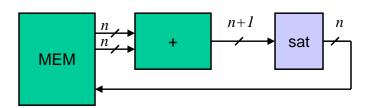- Normally accompanied by a reduction in the word width
- Preserves precision of a fixed-width number representation




B. Baas, © 2009

EEC 281, Winter 2009

143

Saturation (Clipping)

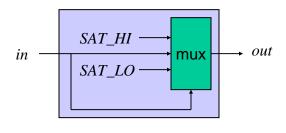- Basically check for 3 possibilities
 - $-in > SAT_HI$
 - in < SAT_LO
 - else
- Think of saturator as a three-input mux



B. Baas, © 2009 EEC 281, Winter 2009

0111 SAT_HI 0110 SAT_HI 0101 SAT_HI 0100 SAT_HI 0**011** either 0010 in 0001 in 0000 in 1111 in 1110 in 1101 in 1**100** either 1011 SAT_LO 1010 SAT_LO 1001 SAT_LO 1000 SAT_LO

Saturation (Clipping)

- Look for when MSB and MSB-1 bits are different. When they are different, the MSB can not be dropped and the output must be saturated.
 - if (in[MSB:MSB-1] == 2'b01)
 - if (in[MSB:MSB-1] == 2'b10)
 - out = in[MSB-1:0];
- Similar approach to saturate more than one bit
 - To saturate S-1 bits, look for when the S MSB bits are not all the same value

0111 SAT_HI 0110 SAT_HI 0101 SAT_HI 0100 SAT_HI 0**011** either 0010 in 0001 in 0000 in 1111 in 1110 in 1101 in 1**100** either 1011 SAT_LO 1010 SAT_LO 1001 SAT_LO 1000 SAT_LO

B. Baas, © 2009

EEC 281, Winter 2009

143

Saturation Bias Effects

- Usually clip to: (+) 01111...111 (-) 10000...000
- But this gives a non-zero mean
- This may cause problems
 - Very sensitive circuits; e.g., a signal path containing an accumulator
 - Worse for small-width words
- Sensitive circuits may require clipping to:
 - (+) 01111...111
 - (-) 10000...00**1**
 - The SAT_LO comparison is now more complex: the saturation detection circuit in the critical path must now look at all bits in the input word

B. Baas, © 2009 EEC 281, Winter 2009 146