
CONTROL CIRCUITS

Control in Digital Systems


- Three primary components of digital systems
 - Datapath (does the work)
 - **Control (manager)**
 - Memory (storage)

Control in Digital Systems

- Control blocks in chips
 - Typically small amount of HW
 - Typically substantial verilog code
 - Can be complex
 - Many opportunities for bugs
 - May be impossible to test all states and transitions
 - Often the focus of testing by Verification Engineers


Control with Finite State Machines

 - Moore type FSM
 - outputs depend only on the state
- Mealy type FSM
 - outputs depend on state and inputs



Sequential Logic

 - Combinational circuits' outputs are a function of the circuit's inputs and a time delay
- Sequential circuits' outputs are a function of the circuit's inputs, previous circuit state, and a time delay



B. Baas, © 2011

_ 281

98

Writing Verilog for State Machines

- Design process
 - Think
 - Draw state diagrams if helpful
 - Draw block diagrams if helpful
 - Pick signal names
 - Think
 - Then...
 - Write verilog
 - Test it

B. Baas, © 2011

EEC 281

99

Verilog Signal Names

- Good to have conventions for signal names
- *c_** – input to a register (e.g., *c_sum*)
- *r_** – output of a register (e.g., *r_sum*)
- Ex:
 - *c_state* -> *state*
 - *indata* -> *r_indata*

State in FSMs

- Clear code = bugs less likely
- Reduce the amount of state if possible (clarity)
 - Ex: Maybe better to have one global state machine instead of two separate ones
- Increase the amount of state if helpful (clarity)
 - Ex: Instantiate a separate counter to count events

Control Block Example

- Four states
 - IDLE
 - PREP
 - Do something for 10 cycles
 - JOB1
 - Do something for 5 cycles
 - JOB2
 - Do something for 20 cycles
- *Reset* at any time returns control to IDLE

Control Block Example

- State registers
 - Choose two bits
- Counter(s)
 - Choose one five bit counter since states are independent and counter can be shared
 - Count *down* may be best (simpler comparator)
- Safest to keep registers (flip-flops) separate from state machine logic
- Sometimes cleaner to define states with

```
parameter IDLE = 2'h0;
```

`define vs. parameter

- Two methods
 - **parameter**
 - Convenient method to use text to represent a number
 - Local to a module
 - Usage

```
parameter  HALT = 4'b0101;
...
if (inst == HALT) begin    // no "back tick"
```
 - **`define macro**
 - Global text macro substitution using a compiler directive
 - Best when helpful to put all definitions in a global file
 - Usage

```
`define  HALT 4'b0101
...
if (inst == `HALT) begin    // requires "back tick"
```


B. Baas, © 2011

EEC 281

104

Example State Machine

- State diagram

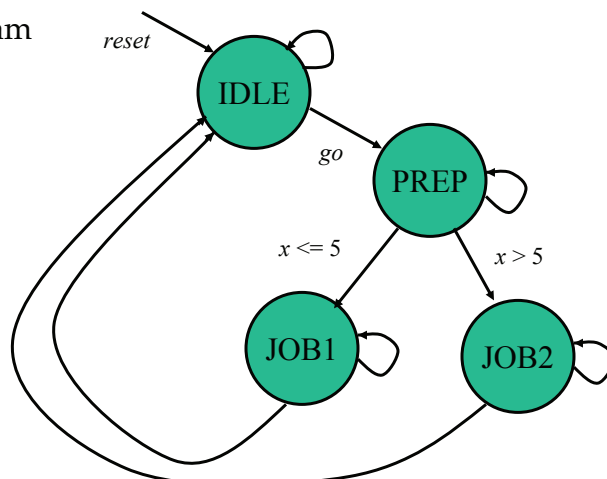

B. Baas, © 2011

EEC 281

105

Example State Machine

(untested, could have bugs—especially syntax or off-by-one-cycle bugs)

```
parameter IDLE = 2'h0; // constants in hex notation
parameter PREP = 2'h1;
parameter JOB1 = 2'h2;
parameter JOB2 = 2'h3;

reg [1:0] state, c_state; // declare both FF regs
reg [4:0] count, c_count; // and comb. logic regs

// Combinational logic for state machine
always @(state or count or go or x or reset) begin
    // defaults (place first)
    c_state = state; // default same state
    c_count = count - 5'b00001; // default count down

    // main state machine logic
    case (state) begin
        IDLE: begin
            if (go) begin
                c_state = PREP;
                c_count = 5'd10; // constant in decimal
            end
            else begin
                c_count = 0;
            end
        end

        PREP: begin
            if (count == 5'b00000) begin
                if (x <= 5) begin // goto JOB1
                    c_state = JOB1;
                    c_count = 5'd05;
                end
                else begin // goto JOB2
                    c_state = JOB2;
                    c_count = 5'd20;
                end
            end
        end // end PREP

        JOB1: begin
            if (count == 5'b00000) begin
                c_state = IDLE;
                // count will underflow to -1 but it is ok
            end
        end

        JOB2: begin
            if (count == 5'b00000) begin
                c_state = IDLE;
                // count will underflow to -1 but it is ok
            end
        end

        default: begin // good practice, but not used here
            c_state = 2'bxx; // better for testing
            c_state = IDLE; // another option
        endcase

        // reset logic (place last to override other logic)
        if (reset) begin
            c_state = IDLE;
            c_count = 5'b00000;
        end
    end // end of always block

    // Instantiates registers (flip-flops)
    always @(posedge clk) begin
        state <= #1 c_state;
        count <= #1 c_count;
    end
end
```

B. Baas, © 2011

EEC 281

106