

# **CMSC 313**

# **COMPUTER ORGANIZATION**

# **&**

# **ASSEMBLY LANGUAGE**

# **PROGRAMMING**

**Lecture 21, Fall 2014**

# TOPICS TODAY

- **Circuits for Addition**
- **Standard Logic Components**
- **Logisim Demo**



# **CIRCUITS FOR ADDITION**



## 3.5 Combinational Circuits

- Combinational logic circuits give us many useful devices.
- One of the simplest is the *half adder*, which finds the sum of two bits.
- We can gain some insight as to the construction of a half adder by looking at its truth table, shown at the right.

Inputs		Outputs	
X	Y	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

## Half Adder

---


- **Inputs:**  $A$  and  $B$
- **Outputs:**  $S$  = lower bit of  $A + B$ ,  $c_{\text{out}}$  = carry bit

$A$	$B$	$S$	$c_{\text{out}}$
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

- Using Sum-of-Products:  $S = \overline{A}B + A\overline{B}$ ,  $c_{\text{out}} = AB$ .
- Alternatively, we could use XOR:  $S = A \oplus B$ .
 
## 3.5 Combinational Circuits

- As we see, the sum can be found using the XOR operation and the carry using the AND operation.



Inputs		Outputs	
X	Y	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

## 3.5 Combinational Circuits

- We can change our half adder into to a full adder by including gates for processing the carry bit.
- The truth table for a full adder is shown at the right.

Inputs			Outputs	
X	Y	Carry In	Sum	Carry Out
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

## Full Adder

---

- **Inputs:**  $A$ ,  $B$  and  $c_{\text{in}}$
- **Outputs:**  $S$  = lower bit of  $A + B$ ,  $c_{\text{out}}$  = carry bit


$A$	$B$	$c_{\text{in}}$	$S$	$c_{\text{out}}$
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

- $S = \overline{A}\overline{B}C + \overline{A}B\overline{C} + A\overline{B}\overline{C} + ABC = A \oplus B \oplus C.$
- $c_{\text{out}} = \text{MAJ3} = AB + BC + AC.$



## 3.5 Combinational Circuits


- Here's our completed full adder.

 

Inputs			Outputs	
X	Y	Carry In	Sum	Carry Out
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1
 
## 3.5 Combinational Circuits


- Just as we combined half adders to make a full adder, full adders can be connected in series.
- The carry bit “ripples” from one adder to the next; hence, this configuration is called a *ripple-carry adder*.



**Today's systems employ more efficient adders.**
 
# Constructing Larger Adders


- A 16-bit adder can be made up of a cascade of four 4-bit ripple-carry adders.



# Full Subtractor


- Truth table and schematic symbol for a ripple-borrow subtractor:

$a_i$	$b_i$	$bor_i$	$diff_i$	$bor_{i+1}$
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

 
 
# Combined Adder/Subtractor

- A single ripple-carry adder can perform both addition and subtraction, by forming the two's complement negative for  $B$  when subtracting. (Note that  $+1$  is added at  $c_0$  for two's complement.)



# Carry-Lookahead Addition

$$s_i = \bar{a}_i \bar{b}_i c_i + \bar{a}_i b_i \bar{c}_i + a_i \bar{b}_i \bar{c}_i + a_i b_i c_i$$

$$c_{i+1} = b_i c_i + a_i c_i + a_i b_i$$

$$c_{i+1} = a_i b_i + (a_i + b_i) c_i$$

$$c_{i+1} = G_i + P_i c_i$$

- Carries are represented in terms of  $G_i$  (generate) and  $P_i$  (propagate) expressions.

$$G_i = a_i b_i \quad \text{and} \quad P_i = a_i + b_i$$

$$c_0 = 0$$


$$c_1 = G_0$$

$$c_2 = G_1 + P_1 G_0$$

$$c_3 = G_2 + P_2 G_1 + P_2 P_1 G_0$$

$$c_4 = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0$$

# Carry Lookahead Adder

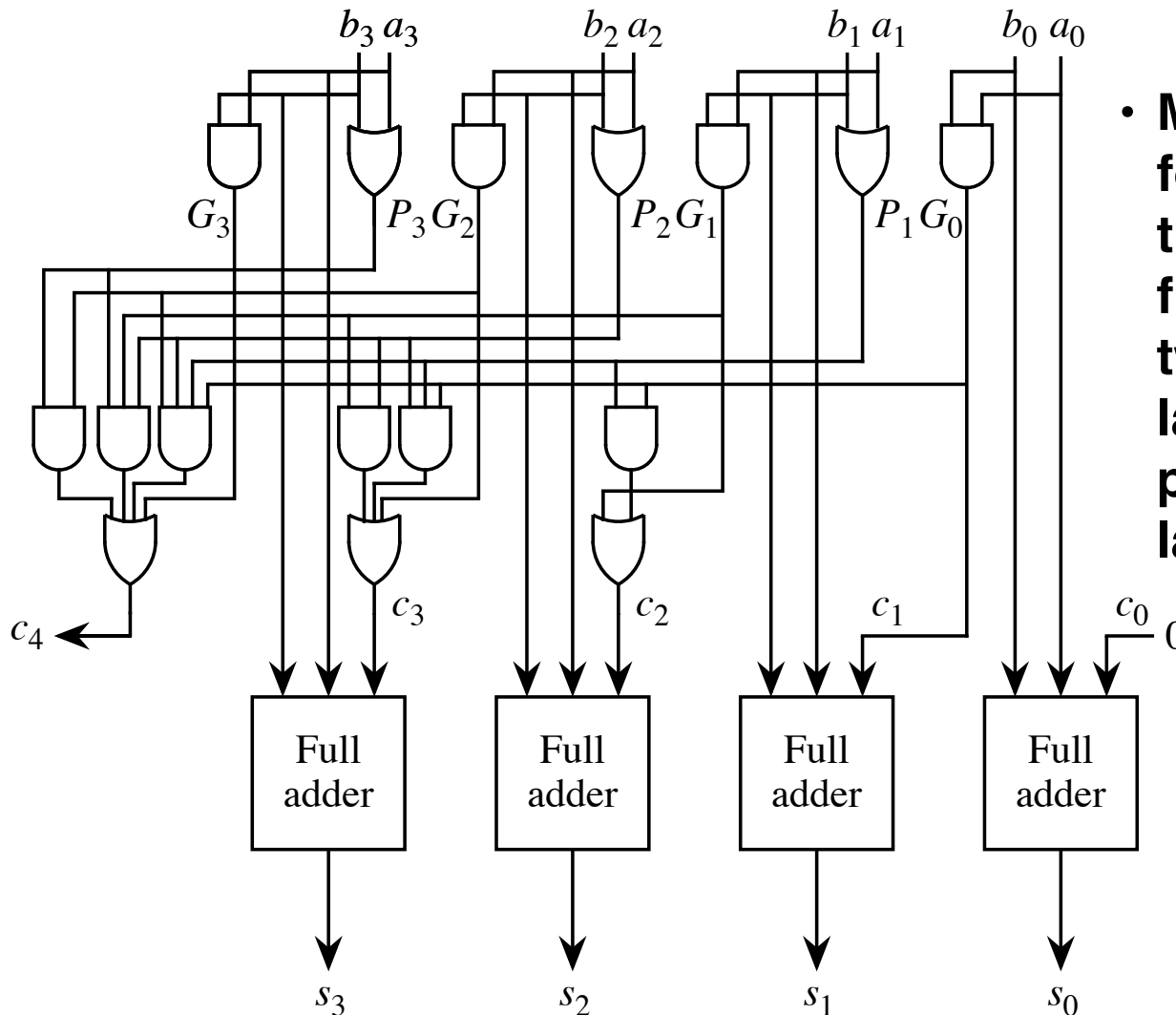

- Maximum gate delay for the carry generation is only 3. The full adders introduce two more gate delays. Worst case path is 5 gate delays.

# **STANDARD LOGIC COMPONENTS**





## 3.5 Combinational Circuits


- Decoders are another important type of combinational circuit.
- Among other things, they are useful in selecting a memory location according a binary value placed on the address lines of a memory bus.
- Address decoders with  $n$  inputs can select any of  $2^n$  locations.

**This is a block diagram for a decoder.**


 
## 3.5 Combinational Circuits


- This is what a 2-to-4 decoder looks like on the inside.



**If  $x = 0$  and  $y = 1$ ,  
which output line  
is enabled?**
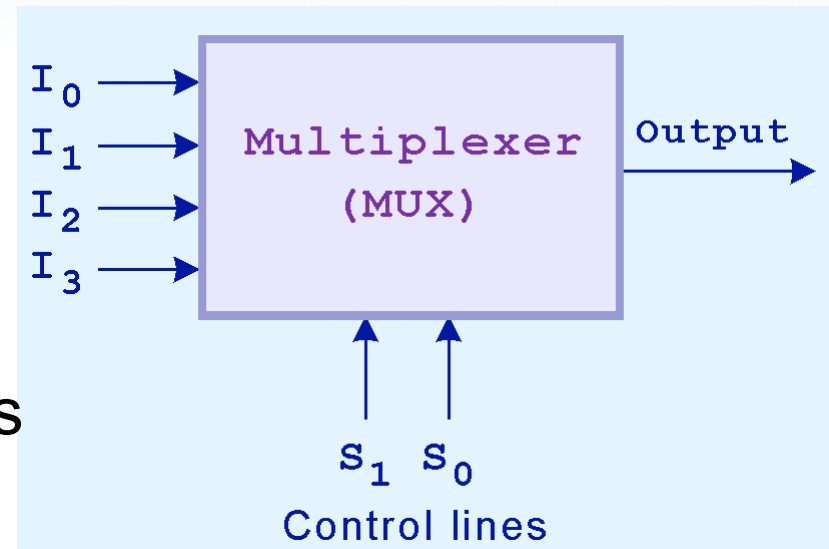
## 3.5 Combinational Circuits


- A multiplexer does just the opposite of a decoder.
- It selects a single output from several inputs.
- The particular input chosen for output is determined by the value of the multiplexer's control lines.
- To be able to select among  $n$  inputs,  $\log_2 n$  control lines are needed.



**This is a block diagram for a multiplexer.**

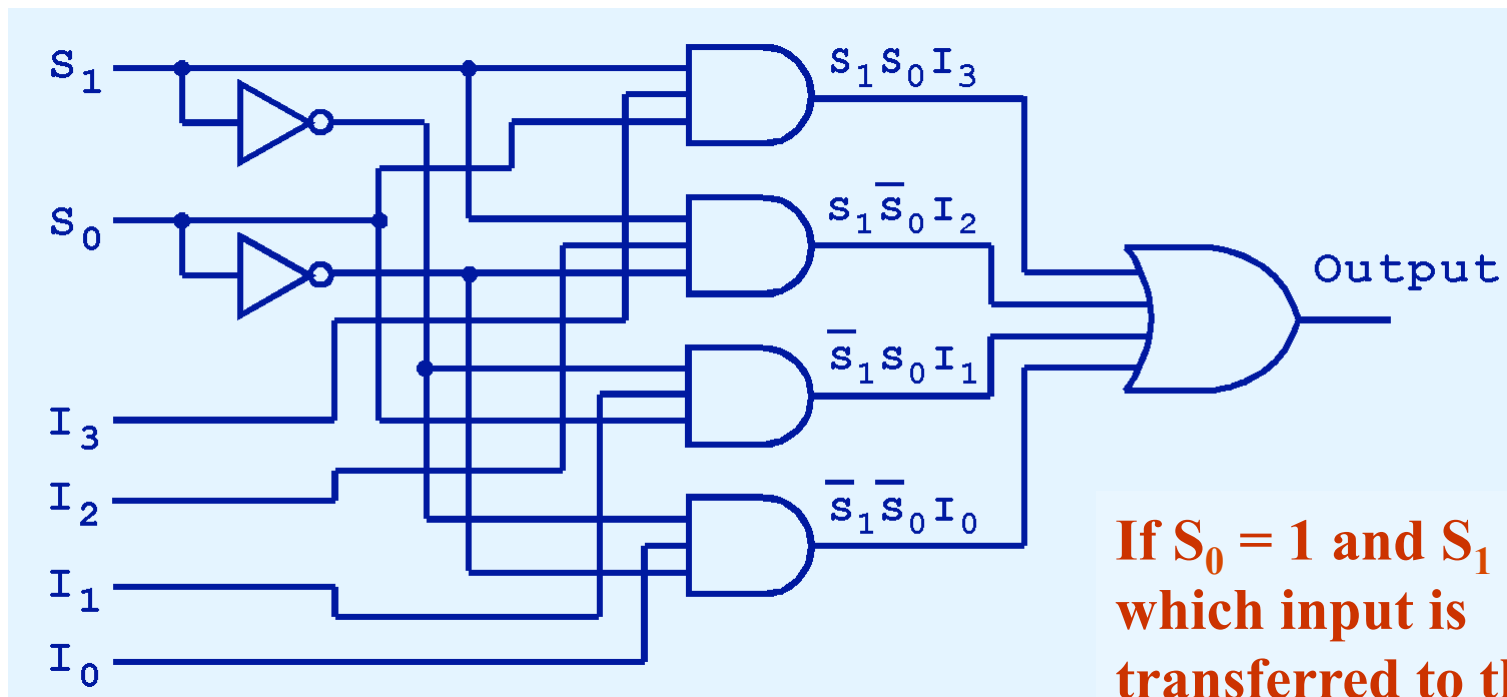
## 3.5 Combinational Circuits

- This is what a 4-to-1 multiplexer looks like on the inside.



**If  $S_0 = 1$  and  $S_1 = 0$ ,  
which input is  
transferred to the  
output?**

# Demultiplexer

 


$$F_0 = D \bar{A} \bar{B} \quad F_2 = D A \bar{B}$$

$$F_1 = D \bar{A} B \quad F_3 = D A B$$


$D$	$A$	$B$	$F_0$	$F_1$	$F_2$	$F_3$
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	0	0	0	0
0	1	1	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1

# Gate-Level Implementation of DEMUX

 
 
## 3.5 Combinational Circuits

- This shifter moves the bits of a nibble one position to the left or right.



**If  $S = 0$ , in which direction do the input bits shift?**

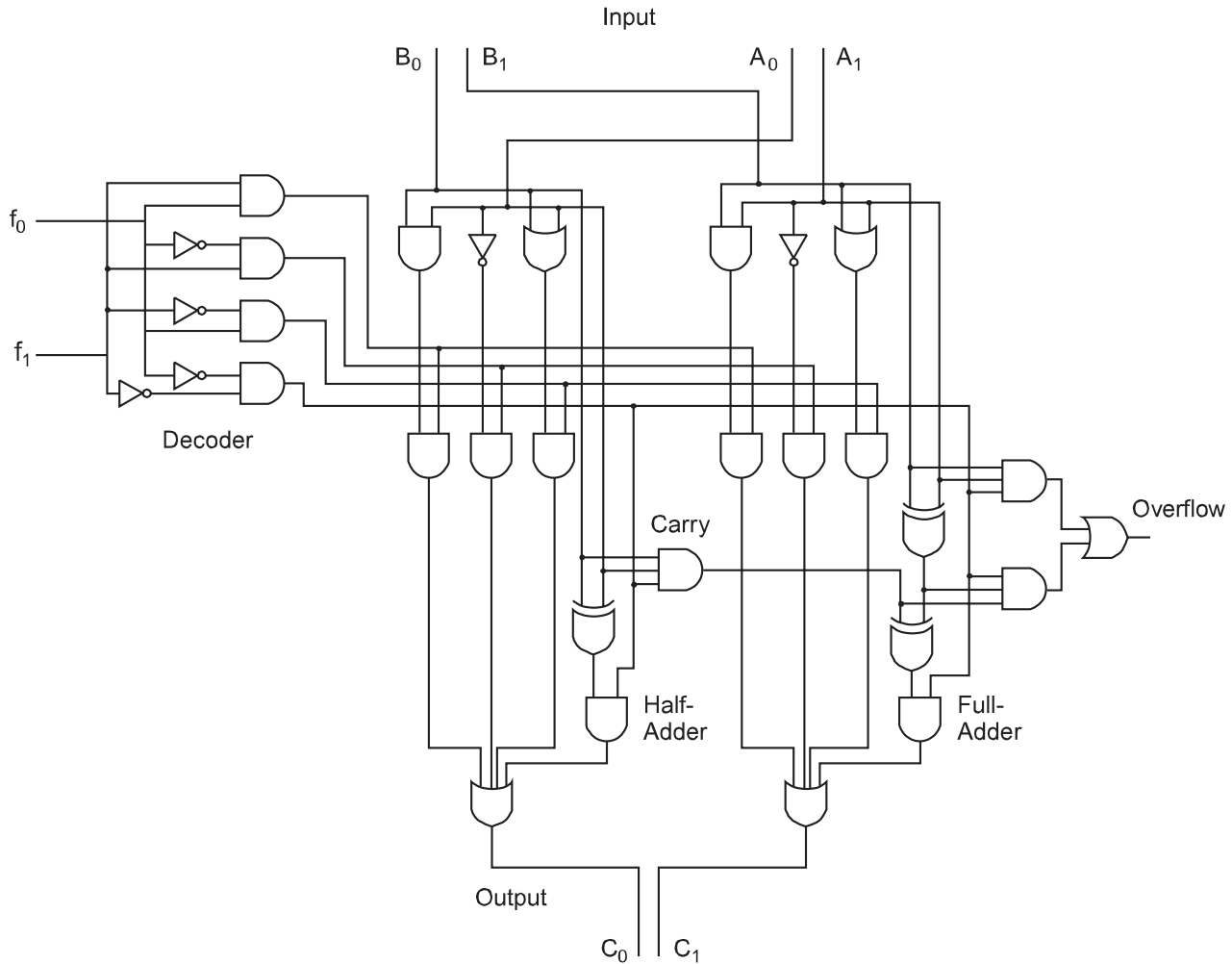


FIGURE 3.17 A Simple Two-Bit ALU



# NEXT TIME

- 2-bit ALU
- Flip-flops

